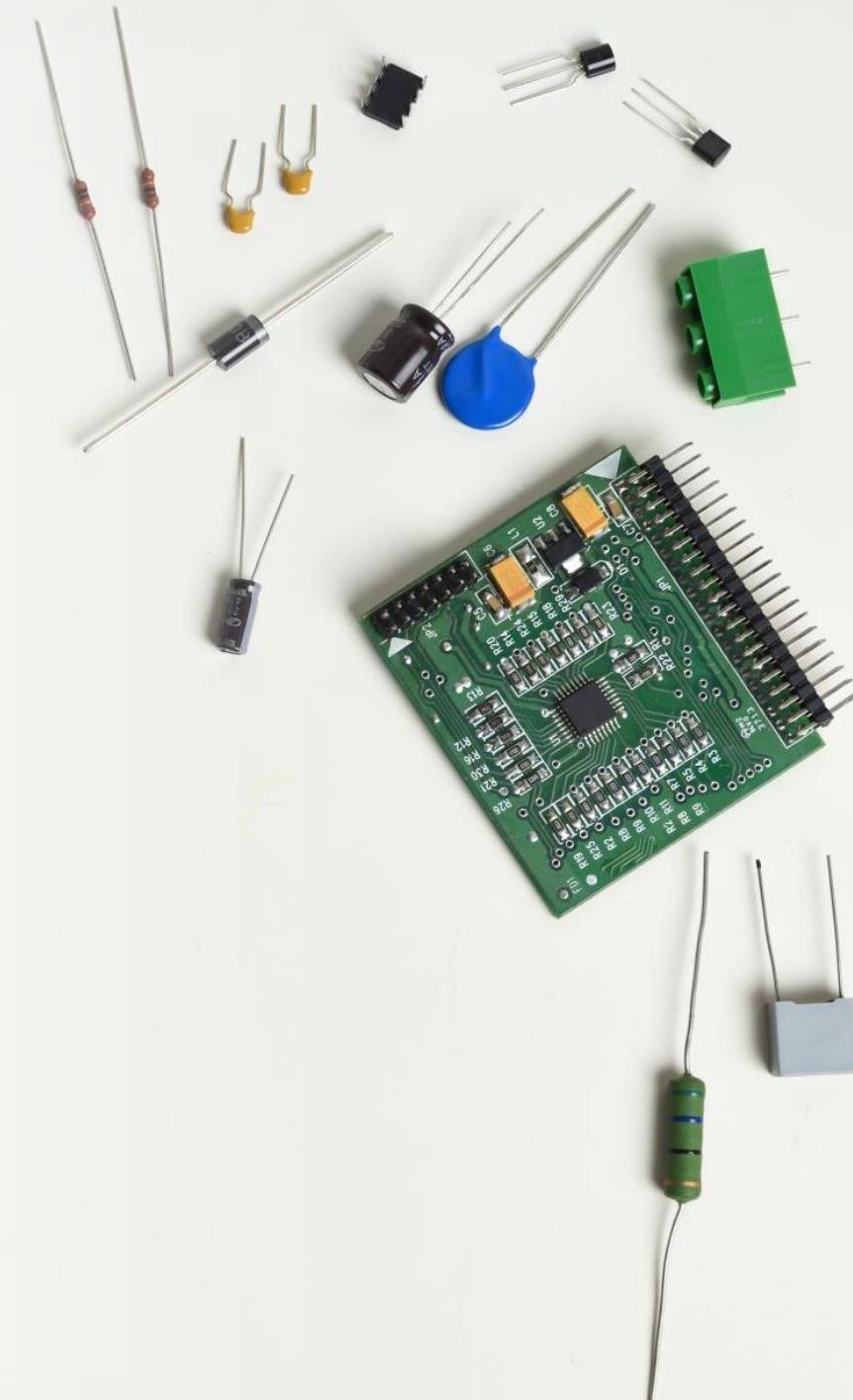



# 104010 : BASIC ELECTRONICS ENGINEERING

---

**UNIT I**  
**Introduction to Electronics**




# DC Power Supply

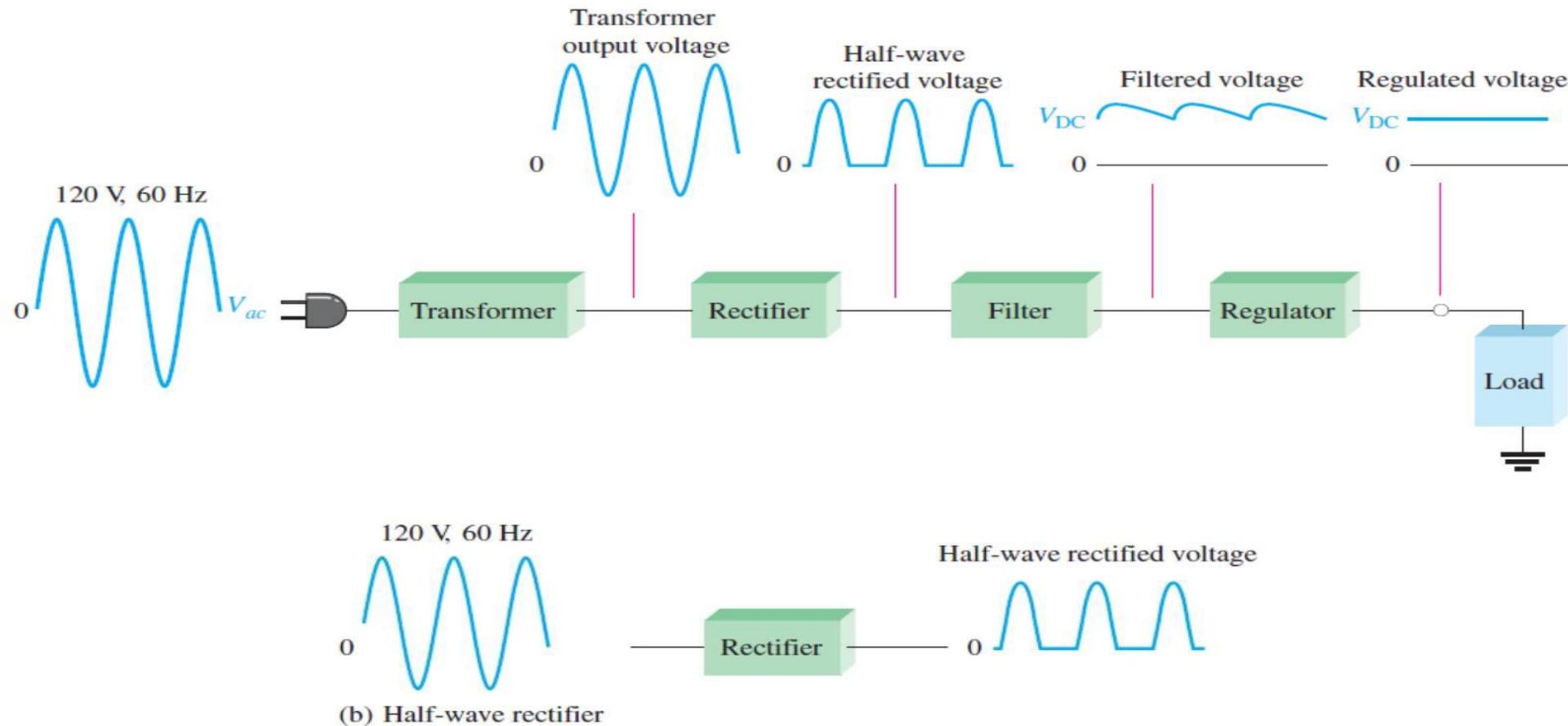


This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.
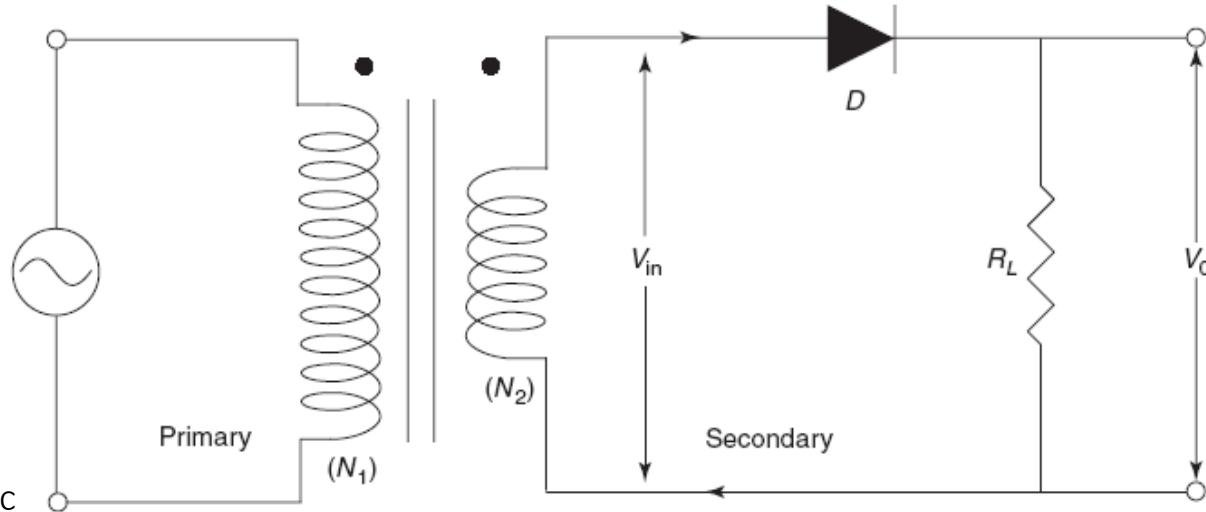
# Half Wave Rectifier


- In a half-wave rectifier, the output waveform occurs after each alternate half-cycle of the input sinusoidal signal.
- The half-wave rectifier will generate an output waveform  $v_o$ . Between the time interval  $t = 0$  to  $T/2$ , the polarity of the applied voltage  $V_i$  is such that it makes the diode forward-biased.
- As a result the diode is turned on, i.e., the forward voltage is more than the cut-in voltage of the diode.



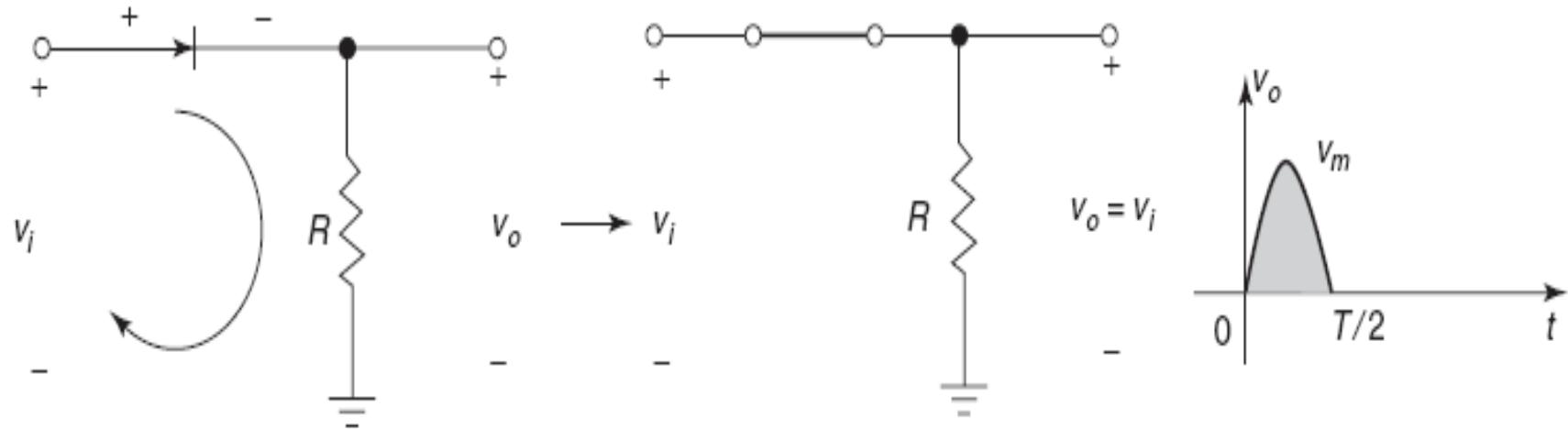This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.




### Conduction region (0 to $T/2$ )

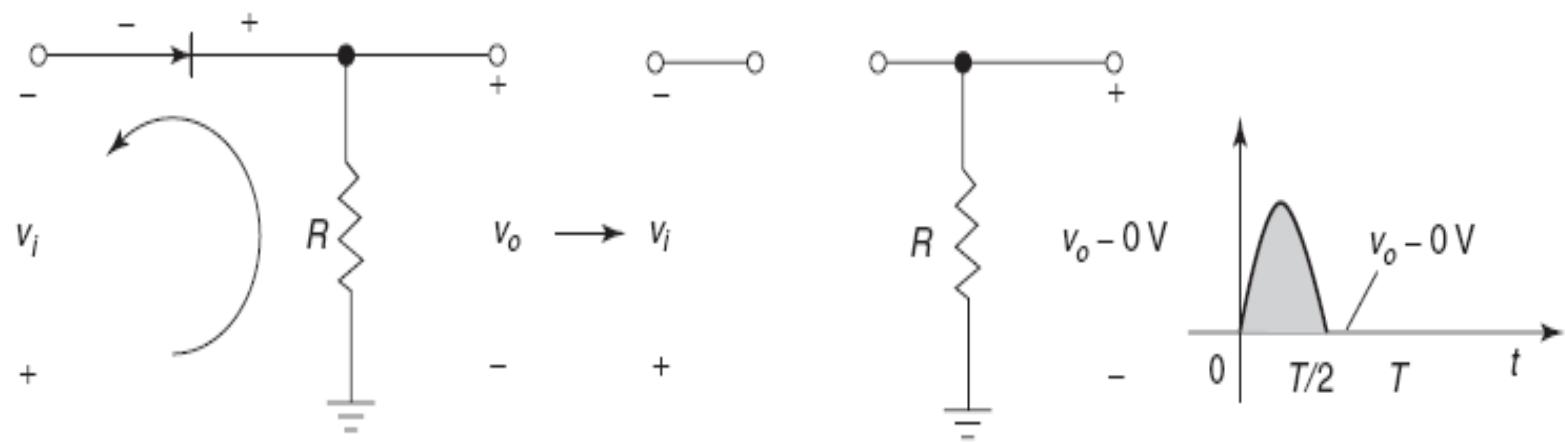
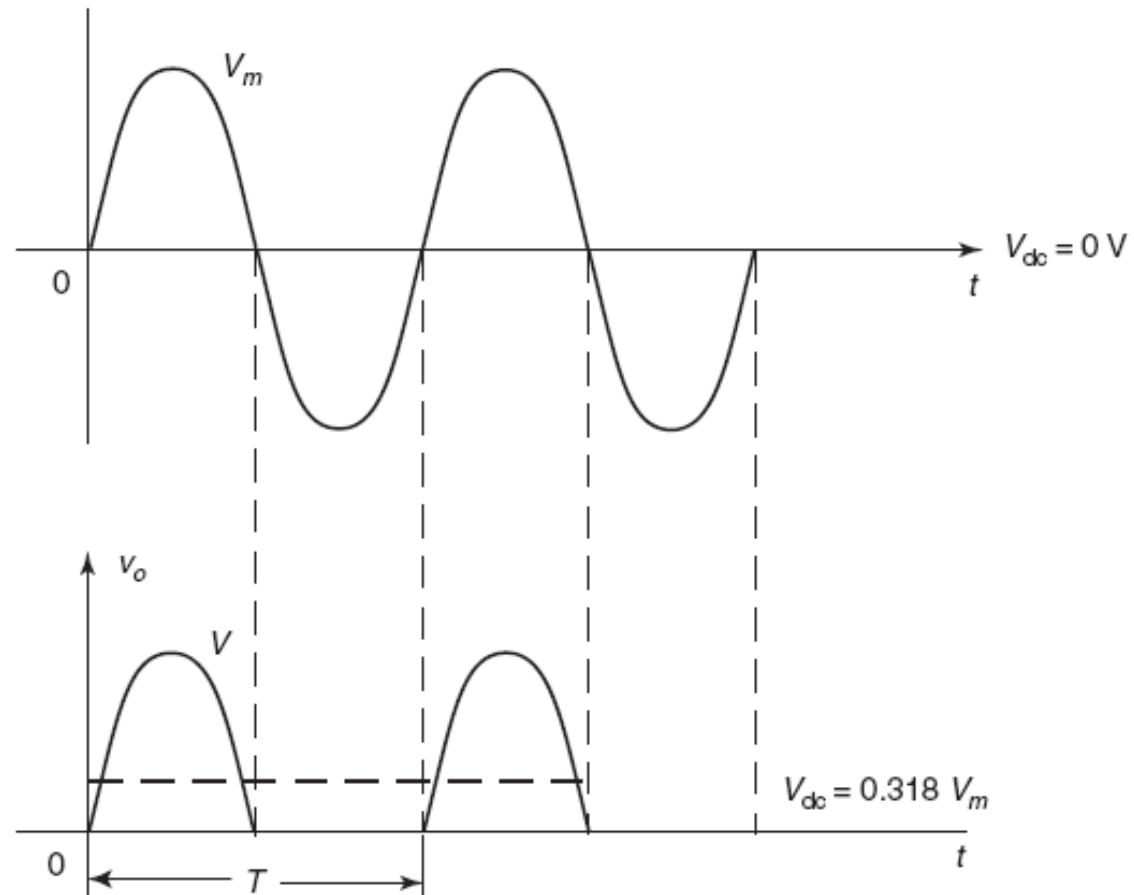
### Non-conducting region ( $T/2$ to $T$ )


This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.



### Half-wave rectified signal

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.



# Half Wave Rectifier

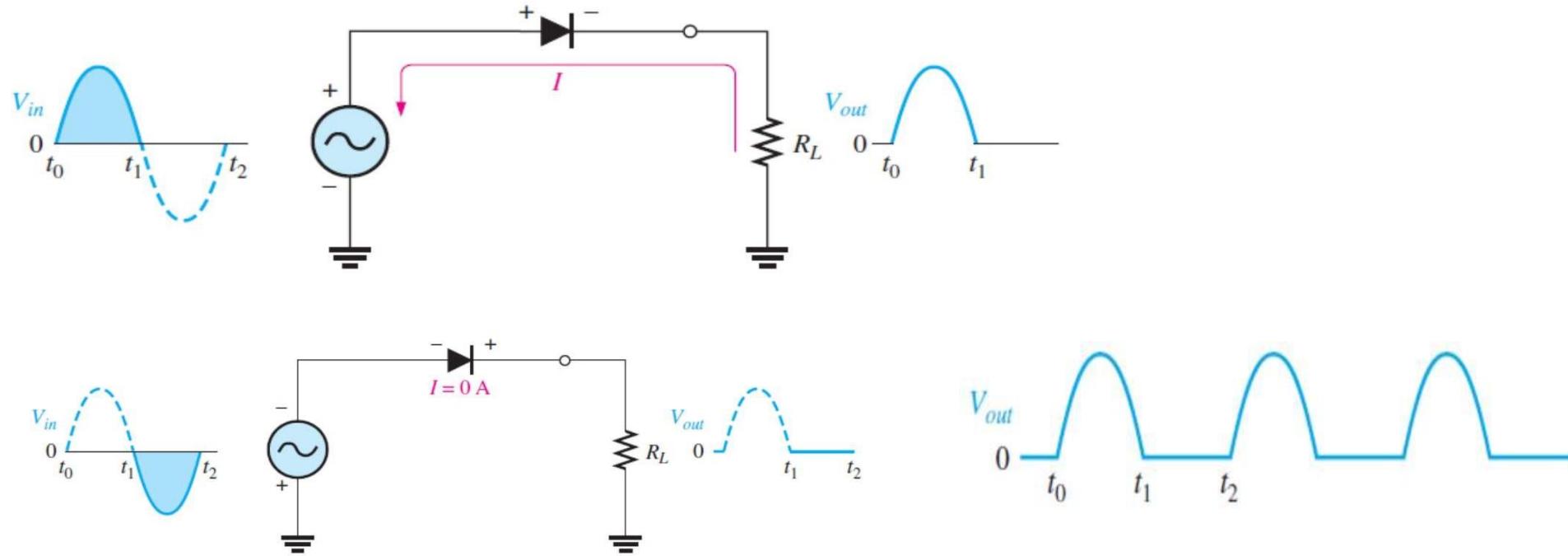


$$y(t) = \begin{cases} x(t) & x(t) \geq 0 \\ 0 & x(t) < 0 \end{cases}$$

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.

HWR:

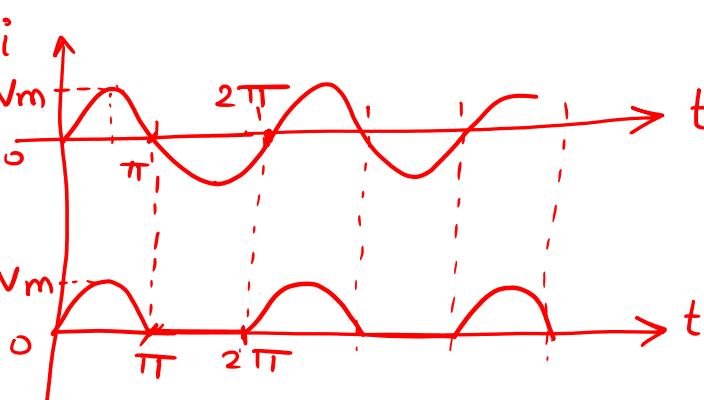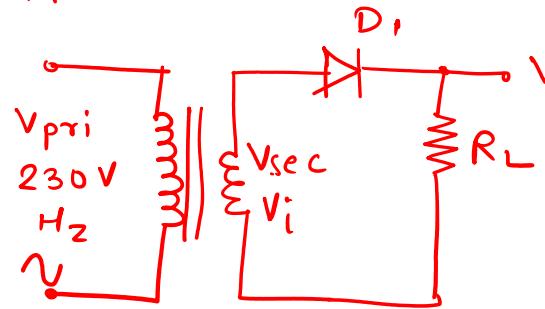

Peak value

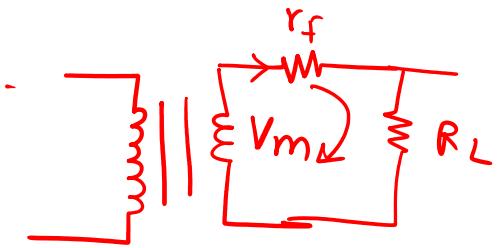

$$I_m = \frac{V_m}{r_f + R_L}$$

$R_L$  = Load resistance

$r_f$  = Resistance of diode (internal) ( $r_f \ll R_L$ )

i)  $V_m$  and  $I_m$ : Peak values of voltage and current

ii) Average Value:

$$V_{dc}/V_{avg} = \frac{\text{Area under the curve over a cycle}}{\text{Base}} = \frac{\int V_i d\theta}{\text{Base}}$$

$$V_{dc}/V_{avg} = \frac{1}{2\pi} \int_0^{2\pi} V_m \sin \theta d\theta = \frac{1}{2\pi} \left[ \int_0^{\pi} V_m \sin \theta d\theta + \int_{\pi}^{2\pi} V_m \sin \theta d\theta \right]$$

$$= \frac{1}{2\pi} \int_0^{\pi} V_m \sin \theta d\theta = \frac{V_m}{2\pi} \left[ -\cos \theta \right]_0^{\pi} = \frac{V_m}{2\pi} (-(-1-1)) = \frac{V_m}{2\pi} (2) = \frac{V_m}{\pi}$$

$$\boxed{V_{dc} = \frac{V_m}{\pi}}$$

$I_{dc} \rightarrow$

$$I_{dc} = \frac{1}{2\pi} \int_0^{2\pi} \frac{V_m}{r_f + R_L} \sin \theta d\theta = \frac{1}{2\pi} \int_0^{\pi} \frac{V_m}{r_f + R_L} \sin \theta d\theta = \frac{V_m}{2\pi(r_f + R_L)} \int_0^{\pi} \sin \theta d\theta$$

$$= \frac{V_m}{2\pi(r_f + R_L)} | -\cos \theta |_0^{\pi} = \frac{V_m}{2\pi(r_f + R_L)} (\cancel{2}) = \frac{V_m}{\pi(r_f + R_L)}$$

But,  $I_m = \frac{V_m}{r_f + R_L} \Rightarrow \boxed{I_{dc} = \frac{I_m}{\pi}} = I_{avg}$

III)  $V_{rms}$  and  $I_{rms}$ :

$$V_{rms} = \left[ \frac{1}{T} \int_0^T V_i^2 d\theta \right]^{1/2} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_m \sin \theta)^2 d\theta}$$

$$V_{rms} = \sqrt{\frac{V_m^2}{2\pi} \int_0^{2\pi} \sin^2 \theta d\theta} = V_m \sqrt{\frac{1}{2\pi} \int_0^{\pi} \left( \frac{1 - \cos 2\theta}{2} \right) d\theta}$$

$$= V_m \sqrt{\frac{1}{4\pi} \int_0^{\pi} (1 - \cos 2\theta) d\theta} = \frac{V_m}{2} \sqrt{\frac{1}{\pi} [(\pi - 0) - 0]} = \frac{V_m}{2} \sqrt{\frac{1}{\pi} (2\pi)}$$

$$\boxed{V_{rms} = \frac{V_m}{2}}$$

$$; \quad \boxed{I_{rms} = \frac{I_m}{2}}$$

IV) Rectifier Efficiency ( $\eta$ ):

$$\eta = \frac{\text{d.c. o/p power}}{\text{a.c. i/p power}} = \frac{P_{dc}}{P_{ac}}$$

$$P_{dc} = (I_{dc})^2 R_L = \frac{I_m^2}{\pi^2} R_L$$

$$P_{ac} = (I_{rms})^2 (r_f + R_L) = \frac{I_m^2}{4} (r_f + R_L)$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \frac{\cancel{I_m^2}/\pi^2 \cdot R_L}{\cancel{I_m^2}/4 (r_f + R_L)}$$

$$\therefore \eta = \frac{4R_L}{\pi^2(r_f + R_L)} = \frac{4/\pi^2}{(1 + r_f/R_L)}$$

$$= \frac{0.406}{(1 + r_f/R_L)}$$

↪ if  $r_f \ll R_L$  ;  $1 + \frac{r_f}{R_L} \approx 1$

$$\therefore \eta = 0.406 \times 100$$

$$\boxed{\therefore \eta = 40.6\%}$$

V) Form Factor (FF):

$$FF = \frac{\text{rms value}}{\text{average value}}$$

$$= \frac{I_m/2}{\cancel{I_m}/\pi}$$

$$= \frac{\pi}{2}$$

$$\boxed{\therefore FF = 1.57}$$

vi) Ripple Factor (R.F.) ( $r$ ) :

$$r = \frac{\text{rms value of ac component}}{\text{Value of dc component}} = \frac{I_{ac}}{I_{dc}}$$

Now, the effective value of total load current is,

$$I_{rms} = \sqrt{I_{ac}^2 + I_{dc}^2} \Rightarrow I_{ac} = \sqrt{I_{rms}^2 - I_{dc}^2}$$

$$\therefore r = \frac{I_{ac}}{I_{dc}} = \frac{\sqrt{I_{rms}^2 - I_{dc}^2}}{I_{dc}} = \frac{1}{I_{dc}} \sqrt{I_{rms}^2 - I_{dc}^2}$$

$$= \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1} = \sqrt{\left(\frac{Im/2}{Im/\pi}\right)^2 - 1} = \sqrt{\frac{\pi^2}{4} - 1} \quad \boxed{\therefore RF = r = 1.21}$$

vii) Peak Inverse Voltage (PIV) :

$$\boxed{PIV = V_m}$$

# Average Value of the Output Voltage

- Average value of a Signal

$$\frac{1}{T} \int_0^T x(t) dt$$

- Output Signal of HW Rectifier

$$x(t) = \begin{cases} \sin(2\pi f_0 t) & 0 \leq t \leq \frac{T}{2} \\ 0 & \frac{T}{2} \leq t \leq T \end{cases}$$

# Comparison of Rectifiers

- **Average Voltage:**

DC Component  $\frac{1}{T} \int_0^T x(t) dt$

- **RMS Voltage**

The RMS value is the square root of the mean (average) value of the squared function of the instantaneous values.


$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T V_m^2 \cos^2(\omega t) dt}$$

- **Ripple factor ( $\gamma$ ):**

Defined as the ratio of the root mean square (rms) value of the **ripple** voltage to the absolute value of the DC component of the output voltage, usually expressed as a percentage. Measure of the Purity of DC
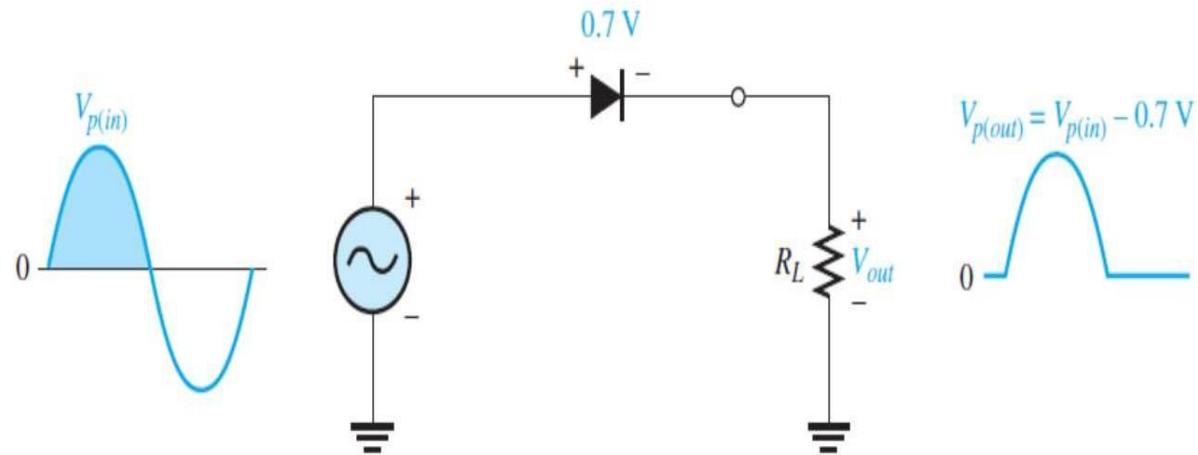
# Effect of Barrier Potential

$$V_{p(out)} = V_{p(in)} - 0.7 \text{ V}$$




This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.

# Peak Inverse Voltage


- The **peak inverse voltage (PIV)** equals the peak value of the input voltage, and the diode must be capable of withstanding this amount of repetitive reverse voltage
- The maximum value of reverse voltage, designated as PIV, occurs at the peak of each negative alternation of the input voltage when the diode is reverse-biased
- A diode should be rated at least 20% higher than the PIV

$$\text{PIV} = V_{p(in)}$$

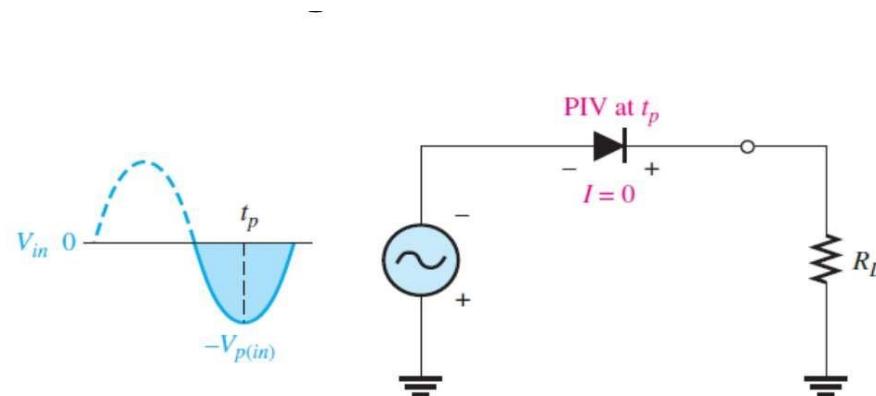

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.

# Transformer Coupling

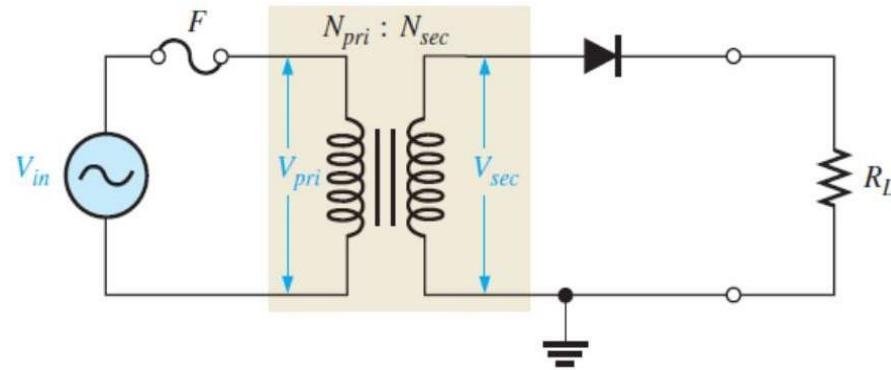

- Transformer coupling provides two advantages
- First, it allows the source voltage to be stepped down as needed.
- Second, the ac source is electrically isolated from the rectifier, thus preventing a shock hazard in the secondary circuit
- $n = \text{"the number of turns in the secondary (Nsec) divided by the number of turns in the primary (Npri)."}$

$$V_{sec} = nV_{pri}$$

$$V_{p(out)} = V_{p(sec)} - 0.7\text{ V}$$


$$\text{PIV} = V_{p(sec)}$$

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.


# Full Wave Rectifier

The full-wave rectifier can be classified into two distinct types.

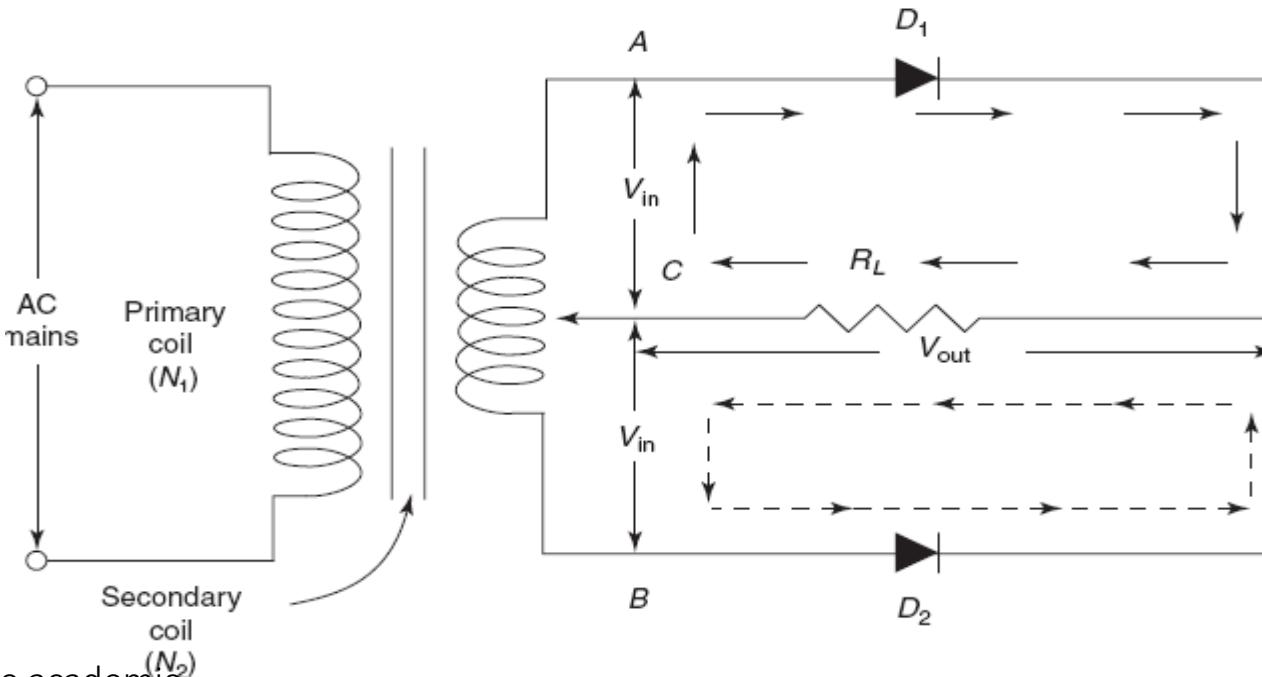(i) Centre-tapped transformer full-wave rectifier:- It comprises of two half-wave circuits, connected in such a manner that conduction takes place through one diode during one half of the power cycle and through the other diode during the second half of the cycle.



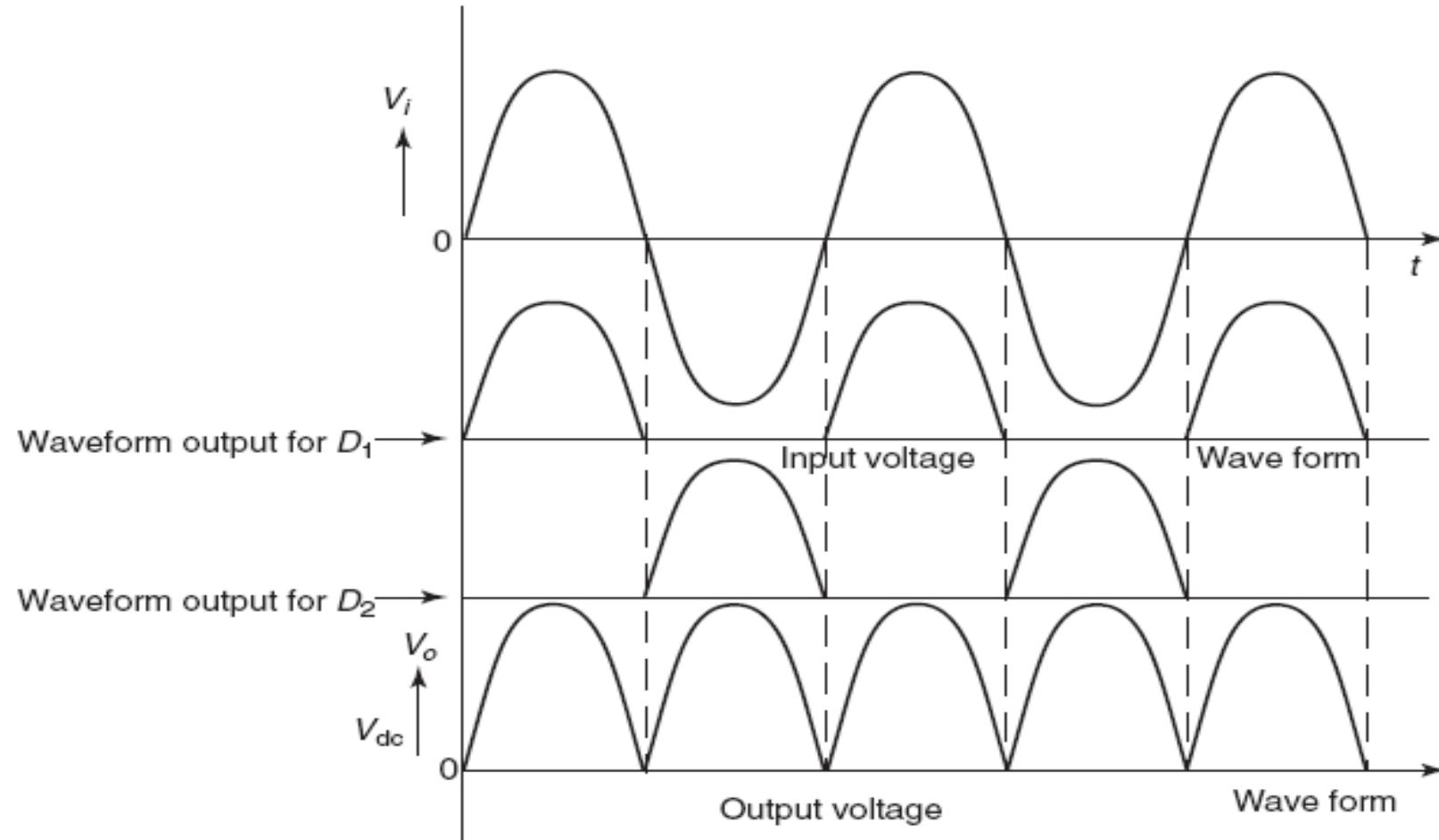
This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.



## Waveform for full-wave rectifier

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.

# Peak Inverse Voltage

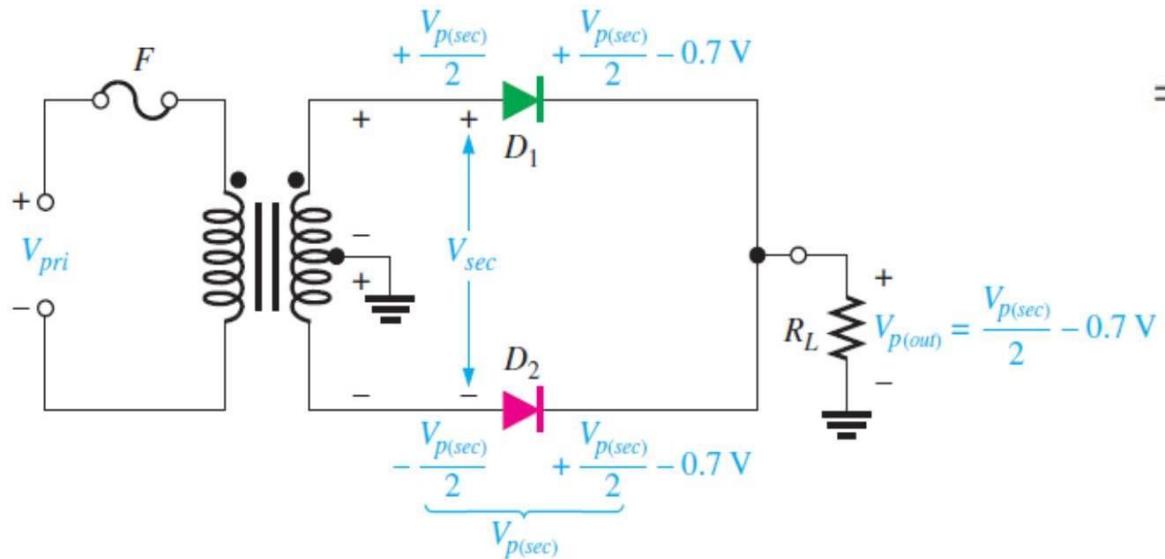

$$\begin{aligned} \text{PIV} &= \left( \frac{V_{p(sec)}}{2} - 0.7 \text{ V} \right) - \left( -\frac{V_{p(sec)}}{2} \right) = \frac{V_{p(sec)}}{2} + \frac{V_{p(sec)}}{2} - 0.7 \text{ V} \\ &= V_{p(sec)} - 0.7 \text{ V} \end{aligned}$$

$$V_{p(out)} = V_{p(sec)} / 2 - 0.7 \text{ V}$$


$$V_{p(sec)} = 2V_{p(out)} + 1.4 \text{ V}$$

$$\text{PIV} = 2V_{p(out)} + 0.7 \text{ V}$$

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.


# Full Wave Rectifier

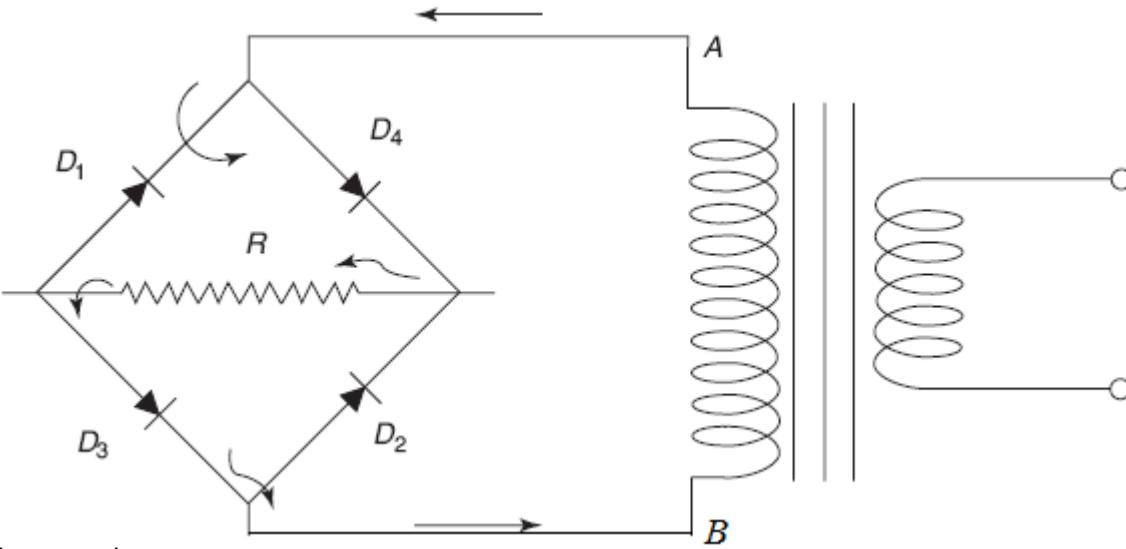(ii) Bridge type full-wave rectifier:- The most important disadvantage of the centre-tapped rectifier is that it brings in the use of a heavy transformer with three terminals at its output, i.e., a centre-tapped transformer. The centre tapping may not be perfect in most cases. This problem can be solved by designing another circuit with four diodes and a simple transformer. This is called a bridge rectifier.




This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.

# Bridge Full Wave Rectifier

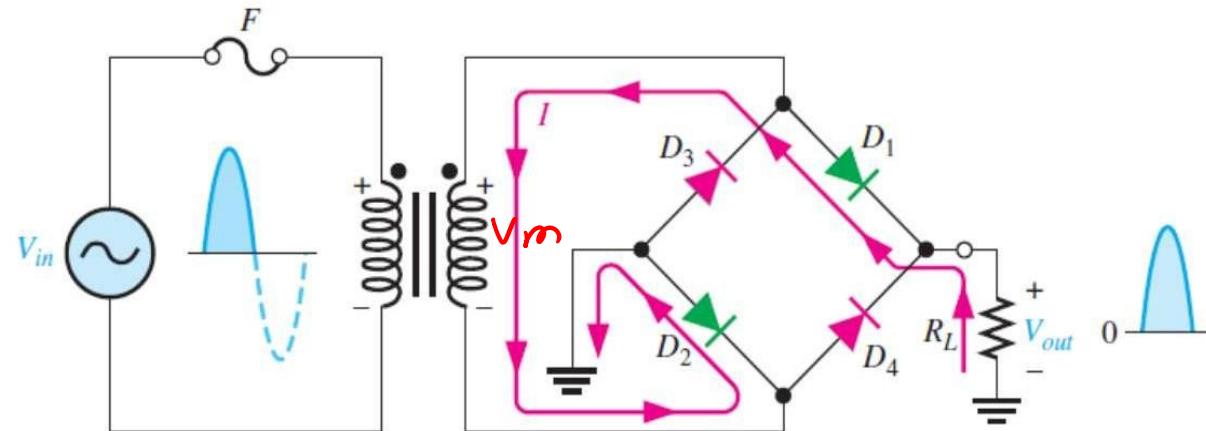


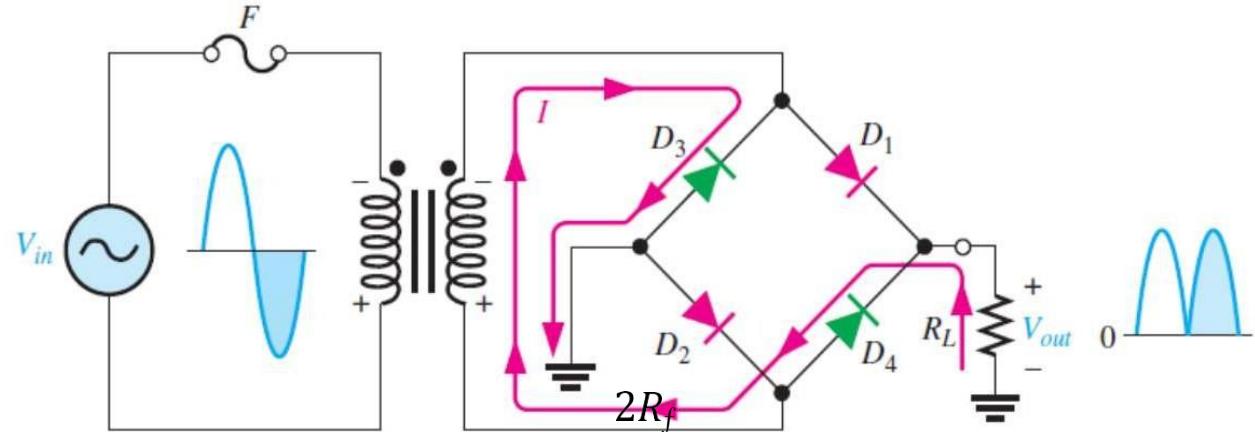(a) During the positive half-cycle of the input,  $D_1$  and  $D_2$  are forward-biased and conduct current.  $D_3$  and  $D_4$  are reverse-biased.




(b) During the negative half-cycle of the input,  $D_3$  and  $D_4$  are forward-biased and conduct current.  $D_1$  and  $D_2$  are reverse-biased.

# Bridge Full Wave Rectifier

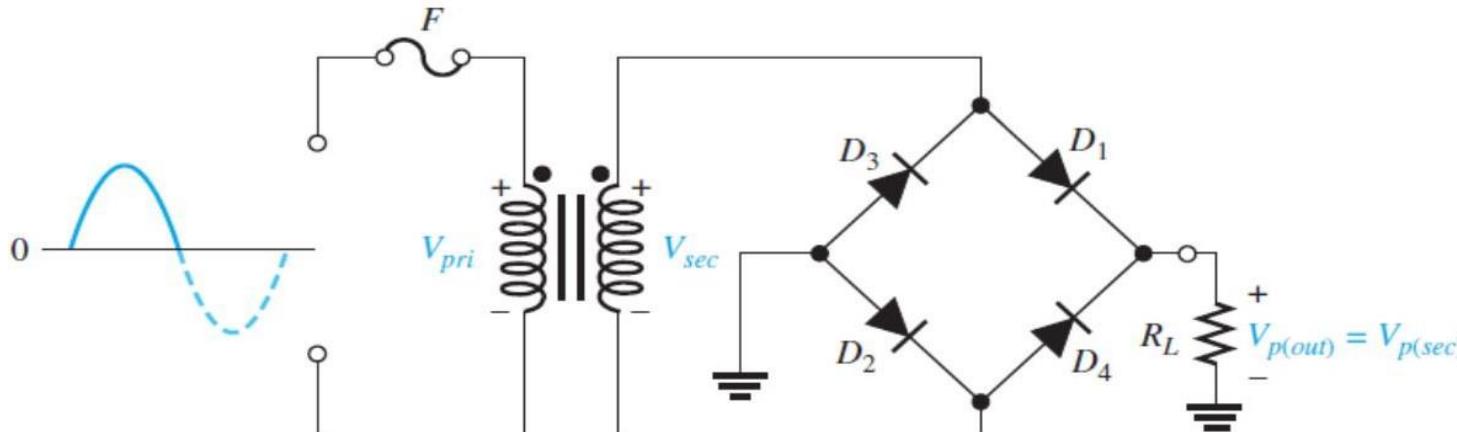

(a) Ideal diodes

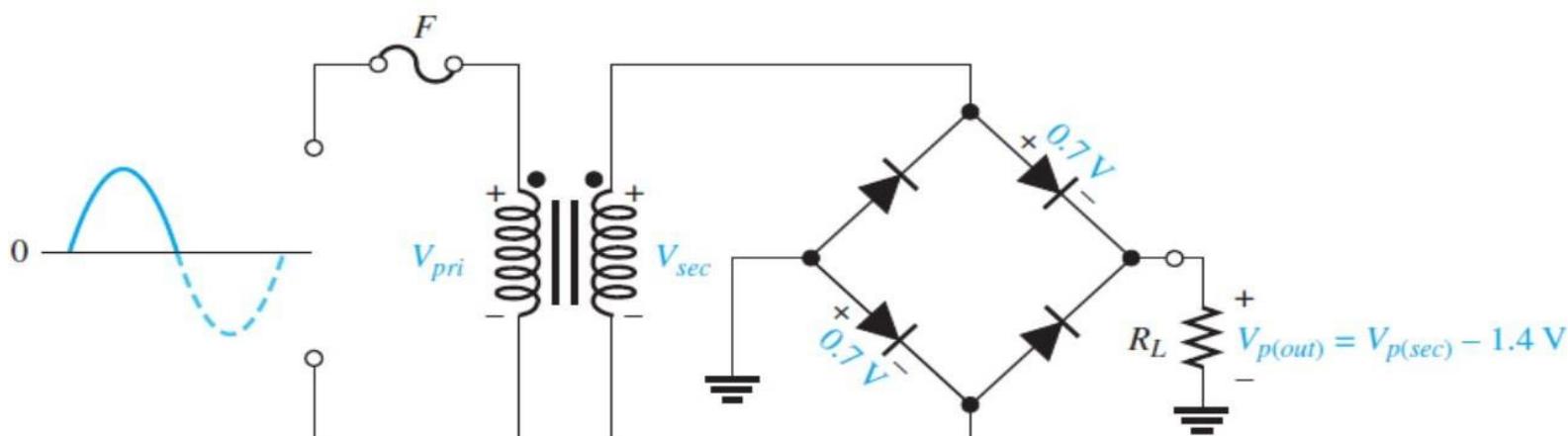

(b) Practical diodes (Diode drops included)

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.

## **Advantages of a Bridge Rectifier**

- (i) In the bridge circuit a transformer without a centre tap is used.
- (ii) The bridge circuit requires a smaller transformer as compared to a full-wave rectifier giving the identical rectified dc output voltage.
- (iii) For the same dc output voltage, the PIV rating of a diode in a bridge rectifier is half of that for a full -wave circuit.
- (iv) The bridge circuit is more appropriate for high-voltage applications, thus, making the circuit compact.

## Disadvantages of a Bridge Rectifier

- (i) Two or more diodes are required in case of a bridge rectifier, as a full-wave rectifier uses two diodes whereas a bridge rectifier uses four diodes.
- (ii) The amount of power dissipated in a bridge circuit is higher as compared to a full-wave rectifier. Hence, the bridge rectifier is not efficient as far as low voltages are concerned.

## Parameters of Full Wave Rectifier:

$V_m$  and  $I_m$  : Peak values.

1)  $V_{dc}$  or  $V_{avg}$


$$V_{dc} = \frac{\text{Area under the curve}}{\text{Base}} \\ = \frac{\int_0^{2\pi} V_m \sin \omega \theta d\theta}{2\pi}$$

$$V_{dc} = \frac{1}{\pi} \left[ \int_0^{\pi} V_m \sin \omega \theta d\theta \right] = \frac{V_m}{\pi} \int_0^{\pi} \sin \omega \theta d\theta \Rightarrow V_{dc} \text{ or } V_{avg} = \frac{2V_m}{\pi}$$

$$I_{dc} = \frac{2I_m}{\pi}$$

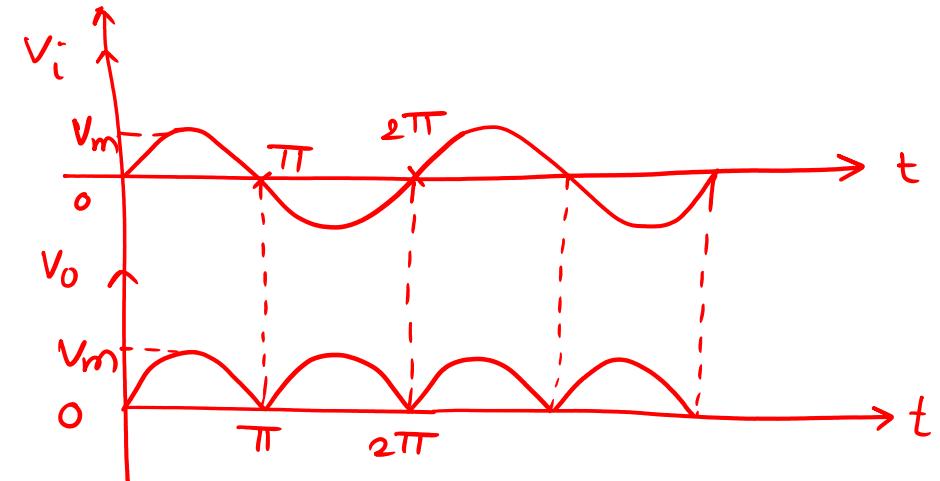2)  $V_{rms}$  and  $I_{rms}$

$$V_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_m \sin \omega \theta)^2 d\theta} = \frac{V_m}{\sqrt{2}}$$



$$\therefore V_{rms} = V_m / \sqrt{2}$$

$$\& I_{rms} = I_m / \sqrt{2}$$

### 3) Rectifier Efficiency ( $\eta$ ):

$$\eta = \frac{P_{dc}}{P_{ac}}$$

$$\rightarrow P_{dc} = (I_{DC})^2 R_L = \left(\frac{2Im}{\pi}\right)^2 R_L$$

$$P_{ac} = (I_{rms})^2 (r_f + R_L) = \left(\frac{Im}{\sqrt{2}}\right)^2 (R_L + r_f) \quad \therefore \eta = \frac{8}{\pi^2}$$

$$\begin{aligned} \therefore \eta &= \frac{P_{dc}}{P_{ac}} = \frac{\frac{4Im^2}{\pi^2} R_L}{\frac{Im^2(r_f + R_L)}{2}} \\ &= \frac{8}{\pi^2} \left( \frac{R_L}{r_f + R_L} \right) \\ &= \frac{8/\pi^2}{1 + r_f/R_L} \end{aligned}$$

If  $r_f \ll R_L$ ,

$\frac{r_f}{R_L} \rightarrow \text{Negligible}$

$$\therefore \eta = 81.2\%$$

### 4) Form Factor:

$$F.F. = \frac{\text{rms value}}{\text{average value}}$$

$$= \frac{I_{rms}}{I_{avg}}$$

$$= \frac{Im/\sqrt{2}}{2Im/\pi} = 1.11 \quad \therefore F.F. = 1.11$$

## 5) Ripple Factor:

$$R.F. (\gamma) = \frac{I_{ac}}{I_{dc}}$$

$$I_{ac} = \sqrt{I_{rms}^2 - I_{dc}^2}$$

$$\therefore \mu = \frac{\sqrt{I_{rms}^2 - I_{dc}^2}}{I_{dc}}$$

$$= \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}$$

$$= \sqrt{\left(\frac{I_m/\sqrt{2}}{2 I_m/\pi}\right)^2 - 1}$$

$$= \sqrt{\frac{\pi^2}{8} - 1}$$

$$\therefore \gamma = 0.483$$

For HWR,

$$PIV = V_m = V_{psec}$$


For CTFWR,

$$\begin{aligned} PIV &= 2V_m \\ &= 2\left(\frac{V_{psec}}{2}\right) \end{aligned}$$

For BR,

$$\begin{aligned} PIV &= V_m \\ &= V_{psec} \end{aligned}$$

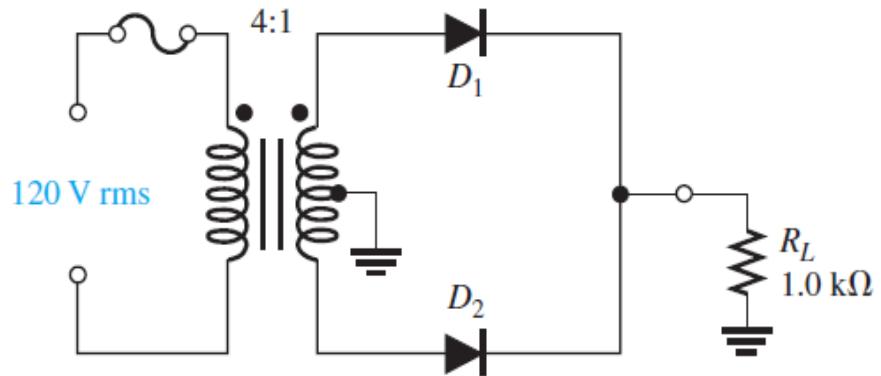Determine the DC and RMS voltage across the load resistance considering the ideal diodes.



$$V_{\text{pri}} = 120 \text{ Vrms}$$

$$\therefore V_{\text{sec}} = \frac{120}{4} = 30 \text{ Vrms}$$

$$\therefore V_m \text{ at sec} = 30\sqrt{2} = 42.4 \text{ V}$$

$$V_{\text{DC}} = \frac{2V_m}{\pi} = 27.01 \text{ V}$$

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}} = 30 \text{ V}$$

$$I_m = \frac{V_m}{R_L}$$


$$I_{\text{dc}} = \frac{2I_m}{\pi} = \frac{2V_m}{\pi R_L}$$

$$I_m = \frac{V_m}{r_f + R_L}$$

$$I_{\text{DC}} \rightarrow V_{\text{DC}}$$

$$I_{\text{dc}} \cdot R_L = \frac{2V_m}{\pi R_L} \cdot R_L = \frac{2V_m}{\pi}$$

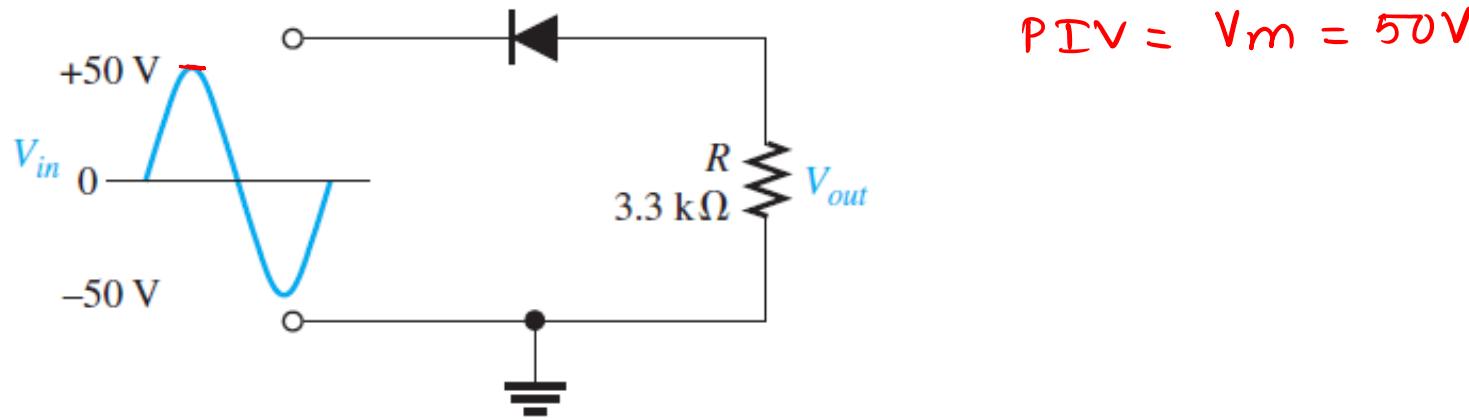What is the Peak Inverse Voltage across the Diode in the following Circuit? Consider the diode to be Ideal.




Peak voltage appearing at the primary of the transformer with 10:1 turns ratio, is 220V, what would be the Peak Inverse Voltage for the diodes used in Centre Trapped Full wave Rectifier?

$$V_{p(\text{pri})} = 220V \quad ; \text{ Turns ratio} = 10:1$$

$$V_{p(\text{sec})} = \frac{220}{10} = 22V$$

$$PIV = 2 \cdot \left( \frac{V_{p(\text{sec})}}{2} \right) = 22V$$

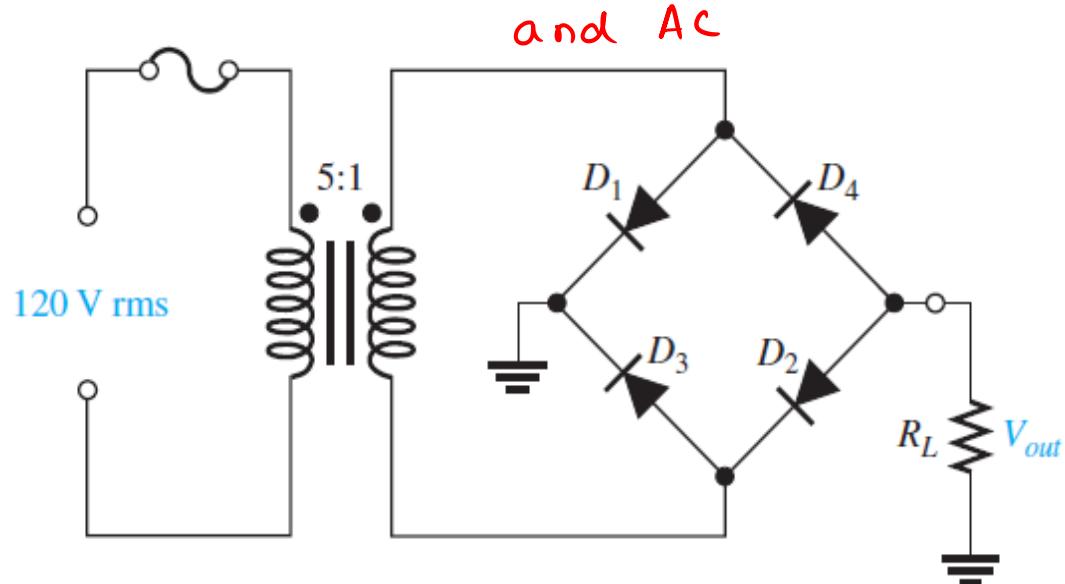Determine the DC power delivered to the load for the load resistance of  $1\text{k}\Omega$ .



$$\rightarrow P_{dc} = (I_{dc})^2 R_L$$

$$= \frac{(V_{dc})^2}{R_L}$$

$$= \frac{(21.61)^2}{1 \times 10^3}$$

$$\therefore P_{dc} = 0.466 \text{ W}$$

$$V_{dc} = \frac{2V_m}{\pi} = 21.61 \text{ V}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} = 24 \text{ V}$$

$$V_{pri} = 120 \text{ V rms}$$

$$V_{sec} = \frac{120}{5} = 24 \text{ V rms}$$

$$\therefore V_m = 24\sqrt{2} \\ = 33.94 \text{ V}$$

$$P_{ac} = (I_{rms})^2 (R_L)$$

$$= \frac{(V_{rms})^2}{R_L}$$

$$= \frac{(24)^2}{1 \times 10^3}$$

$$\therefore P_{ac} = 0.576 \text{ W}$$

# Comparison of HWR and FWR

SI.No	Parameter	Type of the rectifier		
		Halfwave	Fullwave	Bridge
1.	Number of diodes	1	2	4
2.	$V_{dc}$	$V_m/\pi$	$2V_m/\pi$	$2V_m/\pi$
3.	Peak inverse voltage	$V_m$	$2V_m$	$V_m$
4.	Ripple factor	1.21	0.48	0.48
5.	Rectifier efficiency	40.6%	81.2%	81.2%
6.	Transformer Utilization factor	0.287	0.693	0.812
7.	Form factor	1.57	1.11	1.11

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.

# Acknowledgements

1. Electronic Devices, Thomas L. Floyd
2. Web Resources

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.

**Thank You..**