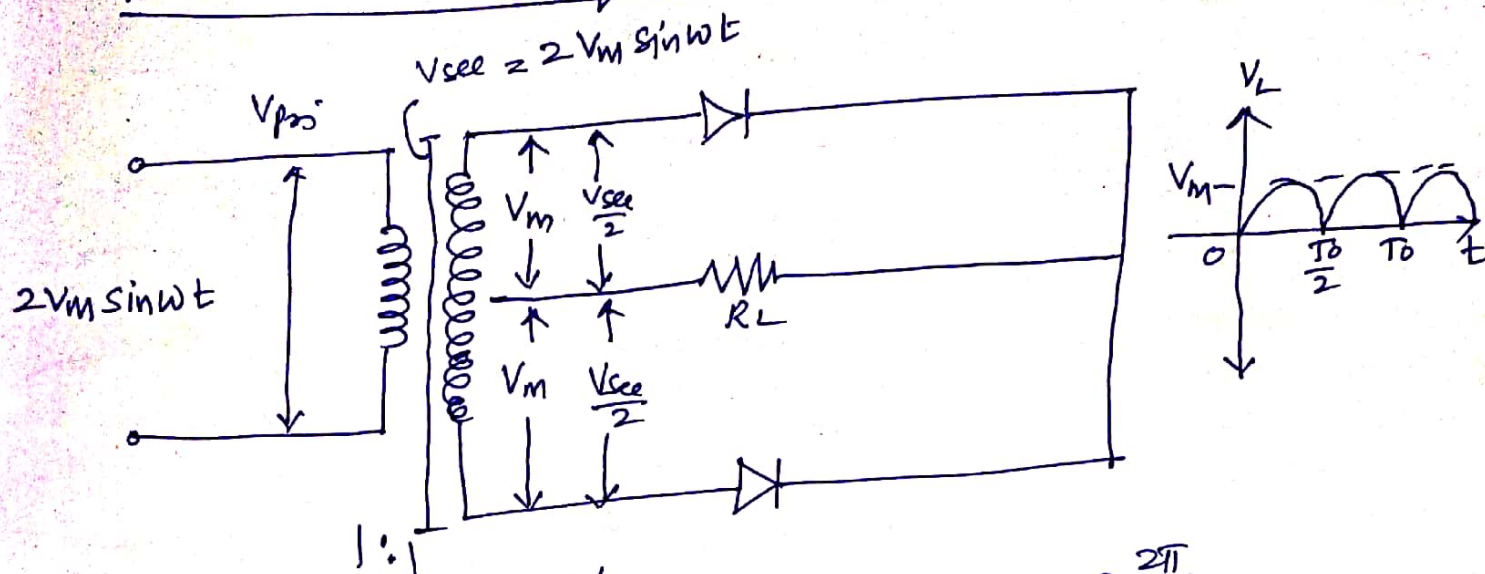


# Centre tapped Full wave Rectifier



$$V_{avg} = \frac{1}{T_0/2} \int_0^{T_0/2} V_m \sin \omega t dt$$

$$= \frac{2}{T_0} \cdot V_m \cdot \left[ -\cos \frac{2\pi}{T_0} t \right]_0^{T_0/2} \times \frac{T_0}{2\pi}$$

$$= \frac{2V_m}{T_0} \left[ -\cos \frac{2\pi}{T_0} \times \frac{T_0}{2} - \left( -\cos \frac{2\pi}{T_0} (0) \right) \right] \times \frac{T_0}{2\pi}$$

$$= \frac{2V_m}{T_0} \left[ 2 \right] \frac{T_0}{2\pi} = \frac{2V_m}{\pi}$$

$$V_{avg} = \frac{2V_m}{\pi}$$

~~Primary~~

$$V_{sec} = V_m \sin \omega t$$

$$V_{avg} = \frac{V_m}{\pi}$$

$$V_{rms} = \sqrt{\frac{1}{T_0/2} \int_0^{T_0/2} V_m^2 \sin^2 \omega t dt}$$


$$= \sqrt{\frac{2}{T_0} \cdot V_m^2 \cdot \int_0^{T_0/2} \frac{1 - \cos \frac{4\pi}{T_0} t}{2} dt}$$

$$= \sqrt{\frac{2}{T_0} \cdot \frac{V_m^2}{2} \left\{ \left[ t \right]_0^{T_0/2} - \left[ \sin \frac{4\pi}{T_0} t \right]_0^{T_0/2} \times \frac{T_0}{4\pi} \right\}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

(1)
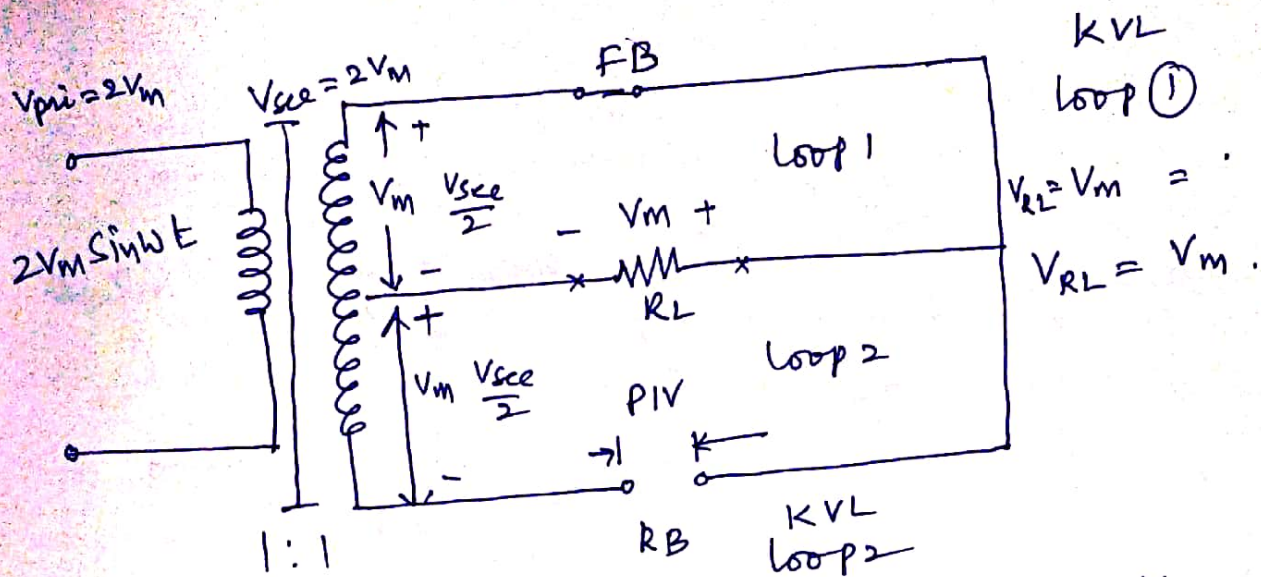
# Peak Inverse voltage of Full wave Rectifier



$$PIV = V_m + V_{RL} = \frac{V_{sec}}{2} + \frac{V_{sec}}{2} = 2V_m = V_{sec}$$

$$PIV = 2V_m$$



Efficiency  $\eta = \frac{P_{ac}}{P_{dc}} = \frac{V_{avg} \cdot I_{avg}}{V_{rms} \cdot I_{rms}} = \frac{V_{avg}^2 / R_L}{V_{rms}^2 / R_L} =$

$$= \frac{4V_m^2}{\pi^2} \times \frac{2}{V_m^2} = \frac{8}{\pi^2} = 0.81$$

$\eta = 81\%$



# Bridge Rectifier

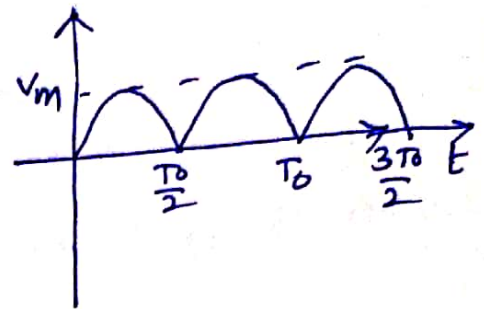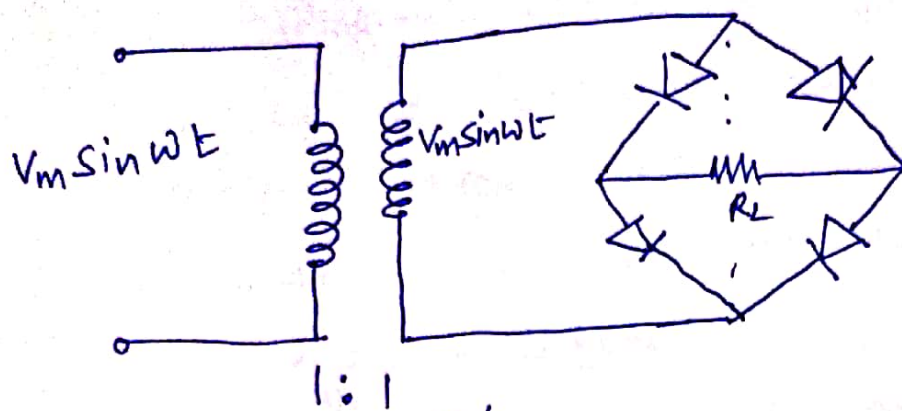


$$V_{avg} = \frac{1}{T_0/2} \int_0^{T_0/2} V_m \sin \frac{2\pi}{T_0} t = \frac{2V_m}{\pi}$$

$$I_{dc} = \frac{2I_m}{\pi}$$

$$V_{rms} = \sqrt{\frac{1}{T_0/2} \int_0^{T_0/2} V_m^2 \sin^2 \frac{2\pi}{T_0} t} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$PIV = V_m$$

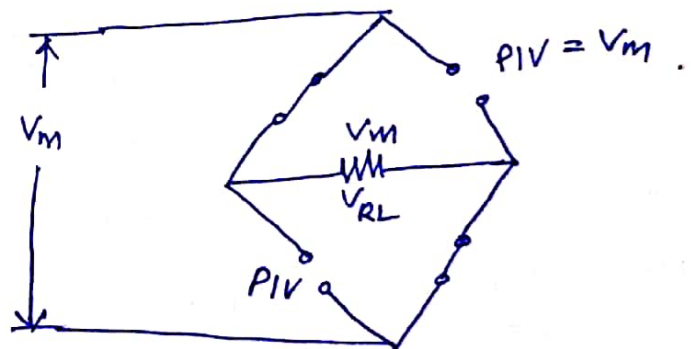

# Basic Electronics Engineering


## Numerical Questions

SPPU  
① For a full wave Rectifier applied input voltage is  $5 \sin \omega t$ . calculate average output voltage, RMS voltage and PIV of diode used for both centre tapped and Bridge rectifiers

(i) Centre tapped Full wave Rectifier :

$$I/p = 5 \sin \omega t$$

$$2V_m = 5$$

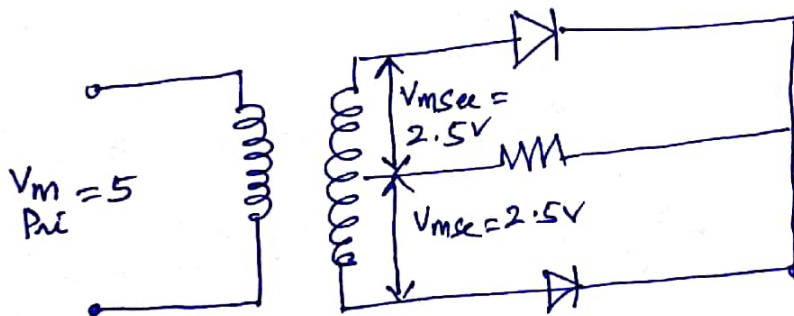

$$V_{avg} = \frac{2V_{msec}}{\pi} = \frac{5}{\pi} = 1.59V$$

$$V_{rms} = \frac{V_{msec}}{\sqrt{2}} = \frac{2.5}{\sqrt{2}} = 1.7677$$

$$PIV = \frac{V_{msec}}{2} + \frac{V_{msec}}{2} = V_{msec} = 2.5V$$

$$PIV = 5V$$

OR Consider  
g/p as

$$2V_m = 5$$

$$V_{avg} = \frac{5}{\pi}$$

$$V_{rms} =$$

(ii) Bridge Rectifier  $\Rightarrow V_m = 5$

$$V_{avg} = \frac{2V_m}{\pi} = \frac{10}{\pi} = 3.18$$

$$V_{rms} = \frac{5}{\sqrt{2}} = 3.5355$$


$$PIV = 5V$$

④



Q2 For the half wave Rectifier circuit of following figure, the resistance of the transformer secondary is  $5\Omega$ , forward resistance of the diode  $R_F = 50\Omega$  and the load resistance is  $1k\Omega$ . Calculate the following

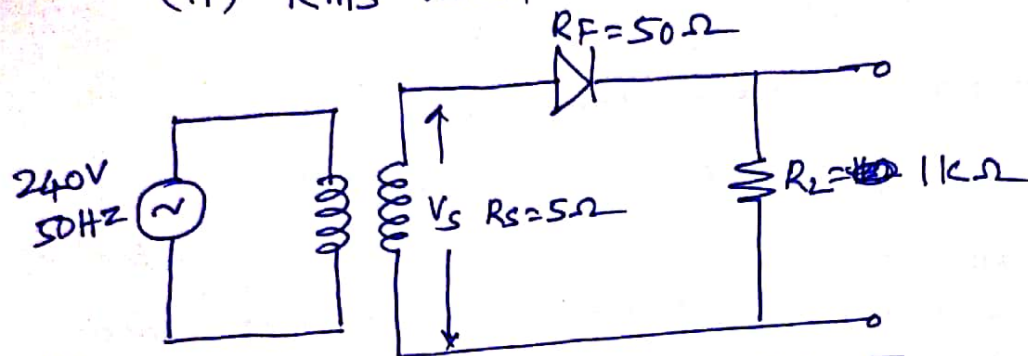- (i) Average load current and load voltage
- (ii) RMS load current and load voltage



Given Primary

$$V_{rms} = 240$$

$$V_m = 240 \times \sqrt{2}$$

4:1

$$V_{rms \text{ Secondary}} = \frac{240\sqrt{2}}{4} = 60\sqrt{2} = 84.85V$$

$$V_{rms \text{ Secondary}} = \frac{240}{4}$$

$I_m$  &  $I_{rms}$  are loop currents

$$I_m = \frac{V_m}{R_s + R_F + R_L} = \frac{84.85}{55} = 80.49 \text{ mA}$$

$$V_{rms} = \frac{V_m}{2} ; I_{rms} = \frac{I_m}{2} \quad \text{for Half wave Rectifier}$$

$$I_{rms} = 40.24 \text{ mA}$$

$$I_{dc} = \frac{I_m}{\pi} = \frac{80.49}{\pi} = 25.62 \text{ mA}$$

$$\text{RMS voltage Across load} = I_{rms} \times R_L = 40.24 \text{ mA} \times 1k\Omega$$

$$V_{rms L} = 40.24 \text{ V}$$

$$\text{Average / DC voltage Across load} = 25.62 \text{ mA} \times 1k\Omega = 25.62 \text{ V}$$

$$\star (i) V_{avg} = 25.62 \text{ V} ; I_{vg} = 25.62 \text{ mA}$$

$$\star (ii) V_{rms} = 40.24 \text{ V} ; I_{rms} = 40.24 \text{ mA}$$

(5)

Q3 A bridge rectifier is applied with the input from a step down transformer having turns ratio 8:1 and input 230V, 50Hz. If the load is  $2k\Omega$ , diode forward resistance is  $1\Omega$ , Secondary (series source) resistance is  $10\Omega$

Calculate (i)  $I_{dc}$  (Average current) and  $V_{dc}$  (Average voltage) Across load

(ii)  $V_{rms}$  and  $I_{rms}$  Across load

(iii) Rectifier Efficiency

Given

$$V_{rms} \text{ primary} = 230V$$

$$V_{rms} \text{ secondary} = \frac{230}{8}$$

$$R_L = 2k$$

$$R_S = 10\Omega$$

$$R_f = 1\Omega$$

$$\rightarrow V_m \text{ secondary} = \frac{230}{8} \times \sqrt{2} = 40.65V$$

$$\rightarrow I_m = \frac{V_{msec}}{2R_f + R_L + R_S} = \frac{40.65}{2012} = 20.2mA$$

$$\cancel{V_{avg}} \rightarrow V_{dc} = \frac{2V_m}{\pi} = \frac{2 \times 40.65}{\pi} = \cancel{51.87V}$$

$$I_{dc} = \frac{2I_m}{\pi} = \frac{2 \times 20.2}{\pi} = 12.85mA$$

$$\rightarrow I_{dc} = 12.85mA$$

$$\rightarrow V_{dc} = I_{dc} \times R_L = 12.85mA \times 2k\Omega = 40.4V$$

$$\rightarrow I_{rms} = \frac{I_m}{\sqrt{2}} = 14.28mA$$

$$\rightarrow V_{rms} = 28.56V$$

$$\rightarrow \text{Efficiency} = \frac{(12.85)^2 \times (10^3)^2 \times R_L}{(14.28 \times 10^3)^2} = 80.9\%$$

(6)



Q4: A full wave rectifier is fed from a transformer with a centre tap. The rms voltage from one end to centre tap at secondary is 30V. If the forward diode resistance is  $2\Omega$  and that of Half Part Secondary resistance is  $8\Omega$  calculate the following for ~~load~~  $1K\Omega$  load

- (i)  $I_{dc}$ ,  $I_{rms}$   $R_L = 1K$   
 $R_f = 2\Omega$   
 $R_s = 8\Omega$   
 (ii)  $V_{dc}$ ,  $V_{rms}$  across the load  
 (iii) Power available at secondary and Power delivered to the load  
 (iv) Rectifier Efficiency.

Given:  $\frac{V_{rms_{sec}}}{2} = 30V$   
 ~~$\frac{V_{sec}}{2}$~~

$V_{rms_{sec}} = 30 \times 2 = 60V$

$V_{m_{sec}} = \frac{60 \times \sqrt{2}}{2} = 60 \times \sqrt{2}$

$I_m = \frac{60 \times \sqrt{2}}{R_f + R_s + R_L} = \frac{84.85}{2 + 8 + 1000} = \frac{84.85}{1010}$

$I_m = 84.01mA$

$I_{dc} = \frac{2I_m}{\pi} = 53.48mA$

Load

$V_{dc} = 53.48mA \times 1K$

$V_{dc} = 53.48V$

$I_{rms} = \frac{I_m}{\sqrt{2}} = 59.57mA$

$I_{rms} = 59.57mA$

$V_{rms \text{ across load}} = 59.57mA \times 1K\Omega = 59.4$

$V_{rmsL} = 59.4V$

Efficiency =  $\frac{P_{dc}}{P_{ac}} = \frac{\text{Power delivered to load}}{\text{Power at secondary}} =$   
 $= \frac{(53.48)^2 \times (10^3)^2 \times 1000}{(59.57 \times 10^3)^2 (1010) \times 1000} = \frac{79.80\%}{8.84\%}$

(7)