

Half Wave Rectifier

1. Average Voltage


Indicates the dc content in the rectifier output

$$V_{avg} = \frac{1}{T_0} \int_0^{T_0} V_{out}(t) dt$$

$$V_{avg} = \frac{1}{T_0} \left\{ \int_0^{\frac{T_0}{2}} V_m \sin\left(\frac{2\pi}{T_0} t\right) dt + \int_{\frac{T_0}{2}}^{T_0} (0) dt \right\}$$

$$\begin{aligned} V_{avg} &= \frac{1}{T_0} \cdot \frac{T_0}{2\pi} V_m \left[-\cos\left(\frac{2\pi}{T_0} t\right) \right]_0^{T_0/2} \\ &= \frac{V_m}{2\pi} \left[\left[-\cos\left(\frac{2\pi}{T_0} \cdot \frac{T_0}{2}\right) - (-\cos(0)) \right] \right] \quad \cos\pi = -1 \\ &= \frac{V_m}{2\pi} \left[-(-1) + 1 \right] = \frac{V_m}{2\pi} \times 2 = \frac{V_m}{\pi} \end{aligned}$$

$$V_{avg} = V_{dc} = \frac{V_m}{\pi}$$

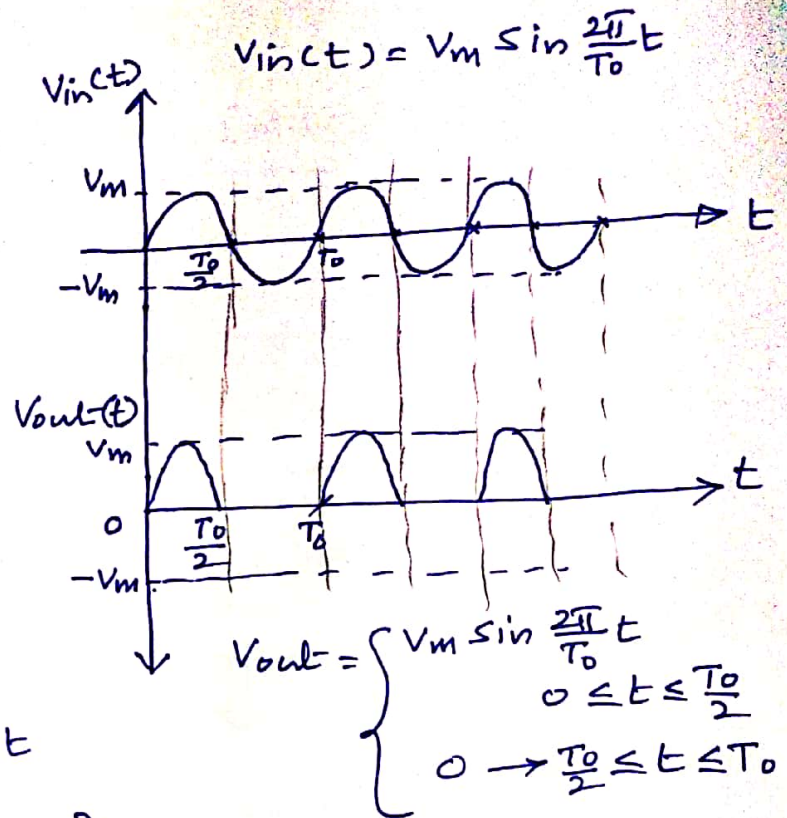

Half Wave Rectifier

1. Average Voltage


Indicates the dc content in the rectifier output

$$V_{avg} = \frac{1}{T_0} \int_0^{T_0} V_{out}(t) dt$$

$$V_{avg} = \frac{1}{T_0} \left\{ \int_0^{\frac{T_0}{2}} V_m \sin\left(\frac{2\pi}{T_0} t\right) dt + \int_{\frac{T_0}{2}}^{T_0} (0) dt \right\}$$

$$\begin{aligned} V_{avg} &= \frac{1}{T_0} \cdot \frac{T_0}{2\pi} V_m \left[-\cos\left(\frac{2\pi}{T_0} t\right) \right]_0^{T_0/2} \\ &= \frac{V_m}{2\pi} \left[\left[-\cos\left(\frac{2\pi}{T_0} \cdot \frac{T_0}{2}\right) - (-\cos\left(\frac{2\pi}{T_0} (0)\right)) \right] \right] \quad \cos\pi = -1 \\ &= \frac{V_m}{2\pi} \left[-(-1) + 1 \right] = \frac{V_m}{2\pi} \times 2 = \frac{V_m}{\pi} \end{aligned}$$

$$V_{avg} = V_{dc} = \frac{V_m}{\pi}$$

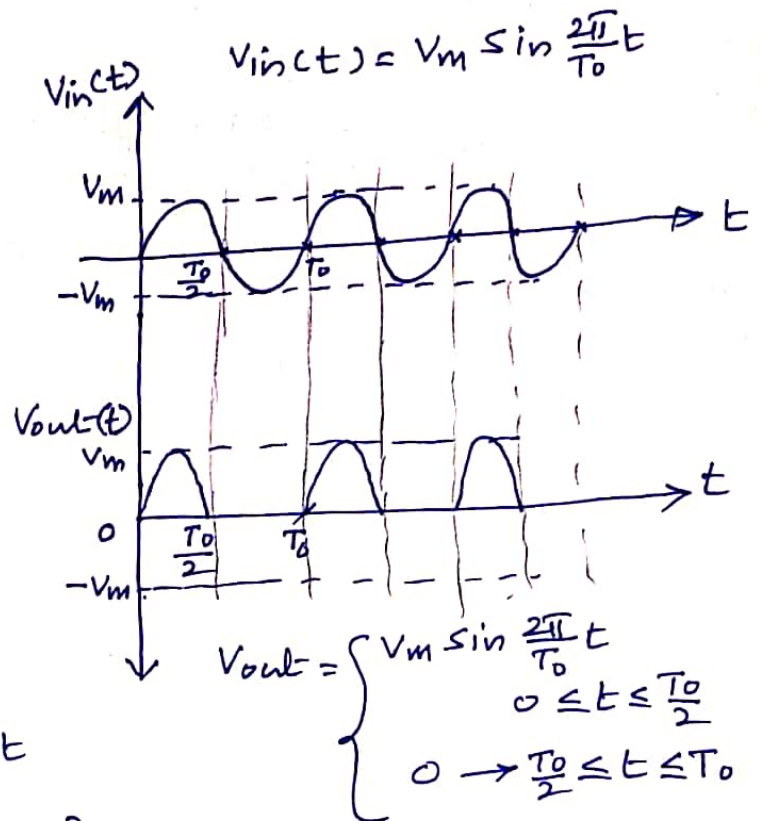

Q. 2. ~~Q. 2. Root~~

2. Root Mean Square Voltage (RMS)

Indicates the AC component

$$V_{rms} = \sqrt{\frac{1}{T_0} \int_0^{T_0} V_{out}^2(t) dt}$$

$$V_{rms} = \sqrt{\frac{1}{T_0} \int_0^{T_0/2} V_m^2 \sin^2\left(\frac{2\pi}{T_0} t\right) dt + \underbrace{\int_{T_0/2}^{T_0} (0) dt}_{\text{Zero}}}$$

$$\int_0^{T_0/2} \frac{V_m^2}{2} (1 - \cos[2(\frac{2\pi}{T_0})t]) dt$$

$$\frac{V_m^2}{2} \left[\left[t \right]_0^{T_0/2} + \left(\sin \frac{4\pi}{T_0} t \right) \times \frac{T_0}{4\pi} \right]_0^{T_0/2}$$

$$\frac{V_m^2}{2} \left[\frac{T_0}{2} - \underbrace{\sin \frac{4\pi}{T_0} \cdot \frac{T_0}{2}}_{\sin 2\pi = 0} + \underbrace{\sin(0)}_0 \right]$$

$$\frac{V_m^2}{2} \cdot \frac{T_0}{2}$$

$$V_{rms} = \sqrt{\frac{1}{T_0} \cdot \frac{V_m^2}{2} \cdot \frac{T_0}{2}} = \frac{V_m}{2}$$

$$V_{rms} = V_{ac} = \frac{V_m}{2}$$

3. Ripple factor : Measure of Purity of DC output
Indicates the • Ripple in output
with reference to V_{dc} .

$$R.F = \sqrt{\frac{V_{ac}^2 - V_{dc}^2}{V_{dc}^2}}$$

$$= \sqrt{\frac{V_{rms}^2 - V_{avg}^2}{V_{avg}^2}}$$

$$= \sqrt{\frac{\frac{V_m^2}{4} - \frac{V_m^2}{\pi^2}}{\frac{V_m^2}{\pi^2}}}$$

$$= \sqrt{\pi^2 \left(\frac{1}{4} - \frac{1}{\pi^2} \right)}$$

$$= \sqrt{\frac{\pi^2 - 4}{4}} = \underline{\underline{1.2114}}$$


Ripple factor for Half wave Rectifier = 1.2114

4. Efficiency of Half wave Rectifier

$$\eta = \frac{\text{DC output Power}}{\text{Ac Input Power}} = \frac{P_{DC}}{P_{AC}}$$

$$P_{DC} = \frac{V_m^2}{\pi^2} / R_L = V_{dc}^2 / R_L$$

$$V_{dc} = \frac{V_m}{\pi^2}$$

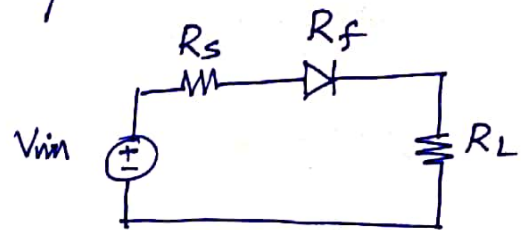

$$P_{AC} = V_{dc}^2 / R_L + R_f + R_s$$

$$P_{AC} = \frac{V_{rms}^2}{R_L} = \frac{V_m^2}{4 R_L}$$

$R_f = R_s = 0$
For an Ideal
Source &
Diode

$$\eta = \frac{\frac{V_m^2}{\pi^2} \times \frac{1}{R_L}}{\frac{V_m^2}{4 R_L}} = \frac{4}{\pi^2} = 0.4053$$

Efficiency in Percentage = 40.53

Half wave Rectifier

5. Transformer Utilization factor

$$TVF = \frac{\text{DC Power output}}{\text{Effective Voltage Ampere Rating of Transformer}}$$

Effective VA Rating of transformer is the average value of transformer primary and secondary VAs.

$$(1) \text{ Rated voltage} = \frac{V_m}{\sqrt{2}}$$

$$\text{Rated current} = \frac{I_m}{2}$$

$$TVF = \frac{V_{DC}^2 / R_L}{\frac{V_m}{\sqrt{2}} \times \frac{I_m}{2}}$$

$$= \frac{\frac{V_m^2}{\pi^2 R_L}}{\frac{V_m}{2\sqrt{2}} \frac{V_m}{R_L + R_f + R_s}}$$


$$= \frac{\frac{V_m^2}{\pi^2 R_L}}{\frac{V_m^2}{2\sqrt{2} R_L}} = \frac{2\sqrt{2}}{\pi^2}$$

$$\cancel{R_s} R_f = R_s = 0$$

$$TVF = 0.286$$

$$TVF = 28.6 \%$$

Full Wave Rectifier

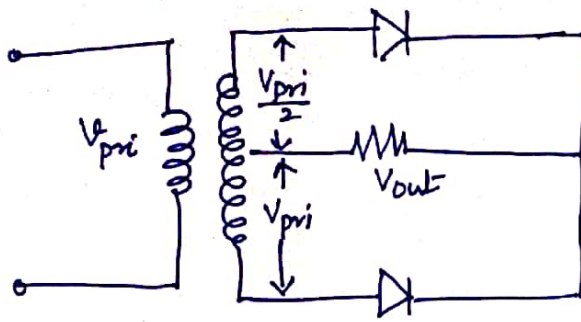

$$V_{pri} = 2V_m \sin\left(\frac{2\pi}{T_0} t\right)$$

$$V_{out} = V_m \sin\left(\frac{2\pi}{T_0} t\right) \quad 0 \leq t \leq \frac{T_0}{2}$$

①


$$V_{avg} = \frac{1}{\frac{T_0}{2}} \int_0^{T_0/2} V_m \sin\left(\frac{2\pi}{T_0} t\right) dt$$

$$V_{avg} = \frac{2}{T_0} \cdot V_m \cdot \frac{T_0}{2\pi} \left[-\cos \frac{2\pi}{T_0} t \right]_0^{T_0/2}$$

$$= \frac{V_m}{\pi} \left[-\cos \frac{2\pi}{T_0} \cdot \frac{T_0}{2} - \left[-\cos(0) \right] \right]$$

$$= \frac{V_m}{\pi} \left[-(-1) + 1 \right] = \frac{2V_m}{\pi}$$

$$V_{avg} = \frac{2V_m}{\pi}$$

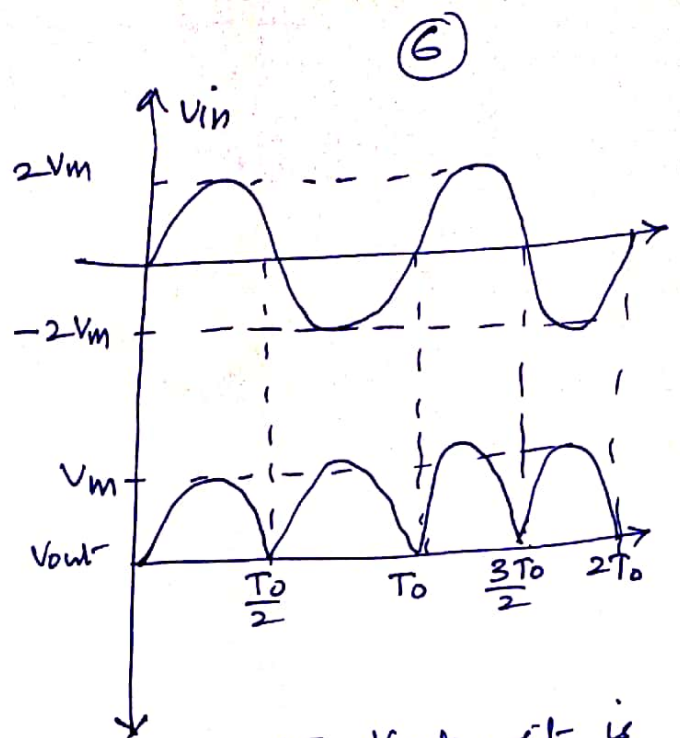

Observe the V_{out} , it is same for every half cycle (it is repeating for every $T_0/2$)

(7)

RMS of FW

(2)

$$V_{rms} = \sqrt{\frac{1}{T_0/2} \int_0^{T_0/2} V_m^2 \sin^2\left(\frac{2\pi}{T_0}t\right) dt}$$

$$V_{rms} = \sqrt{\frac{2}{T_0} \cdot V_m^2 \cdot \left[\frac{1}{2} \int_0^{T_0/2} 1 - \cos\left(\frac{4\pi}{T_0}t\right) dt \right]}$$

$$= \sqrt{\frac{2}{T_0} V_m^2 \cdot \frac{1}{2} \left(\frac{T_0}{2} - 0 \right)}$$

$$= \sqrt{\frac{V_m^2}{2}} = \frac{V_m}{\sqrt{2}}$$

(3) Ripple factor

$$RF = \frac{\sqrt{V_{ac}^2 - V_{dc}^2}}{V_{dc}}$$

$$= \frac{\sqrt{\frac{V_m^2}{2} - \frac{4V_m^2}{\pi^2}}}{\frac{2V_m}{\pi}} = \frac{\sqrt{\frac{1}{2} - \frac{4}{\pi^2}}}{\frac{2}{\pi}} = 0.4834$$

(4) Rectifier Efficiency = $\frac{P_{dc}}{P_{ac}}$

$$P_{ac} = \frac{V_{ac(rms)}^2}{R_L} \quad P_{dc} = \frac{V_{dc(avg)}^2}{R_L} = \frac{4V_m^2}{\pi^2 R_L}$$

$$= \frac{V_m^2}{2R_L}$$

$$\eta = \frac{\frac{4V_m^2}{\pi^2 R_L}}{\frac{V_m^2}{2R_L}} = \frac{8}{\pi^2} = ~~81.06~~ 0.8106$$

$$\eta \text{ in Percentage} = 0.8106 \times 100 = 81.06\%$$