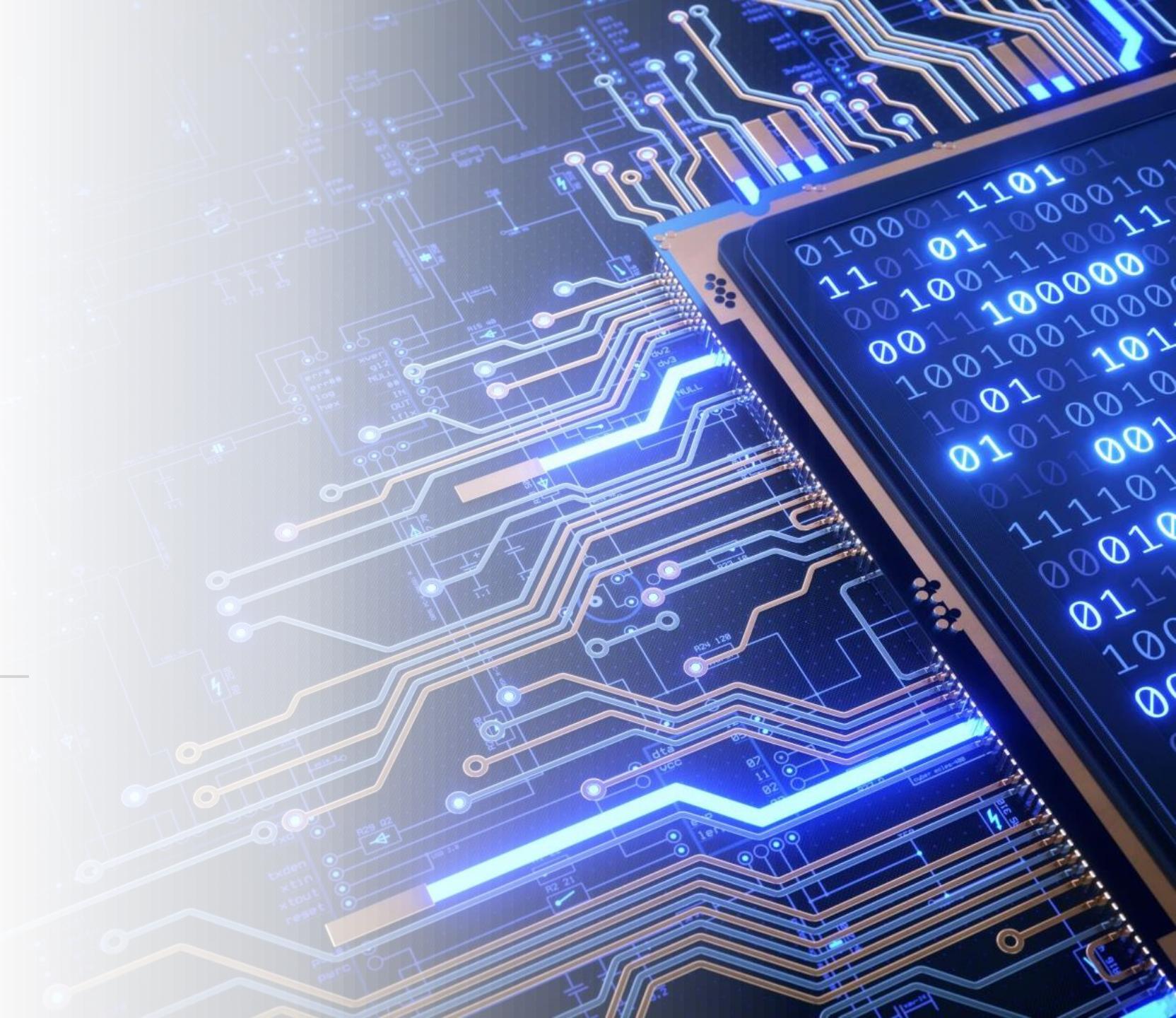


# Operational Amplifier (OP-AMP)



# Operational Amplifier


An **Operational Amplifier** (often **op-amp** or **opamp**) is a DC coupled high-gain electronic voltage amplifier with a differential input and usually, a single-ended output.

multiple stages connected in cascade




- Op-amp is basically a multistage amplifier which uses several amplifier stages interconnected to each other in a complicated manner.
- The amplifier can be configured to perform a variety of operations such as amplification, addition, subtraction, differentiation and integration. Hence the name is **operational amplifier (OP-AMP)**.  
→ IC 741 → 8 pin IC
- The integrated Op-amp offers all the advantages of monolithic integrated circuits such as small size, high reliability, reduced cost, less power consumption.  
↓  
• IC 741 is extremely popular and is used in a variety of applications.

# Pin Configuration of OP-AMP IC 741

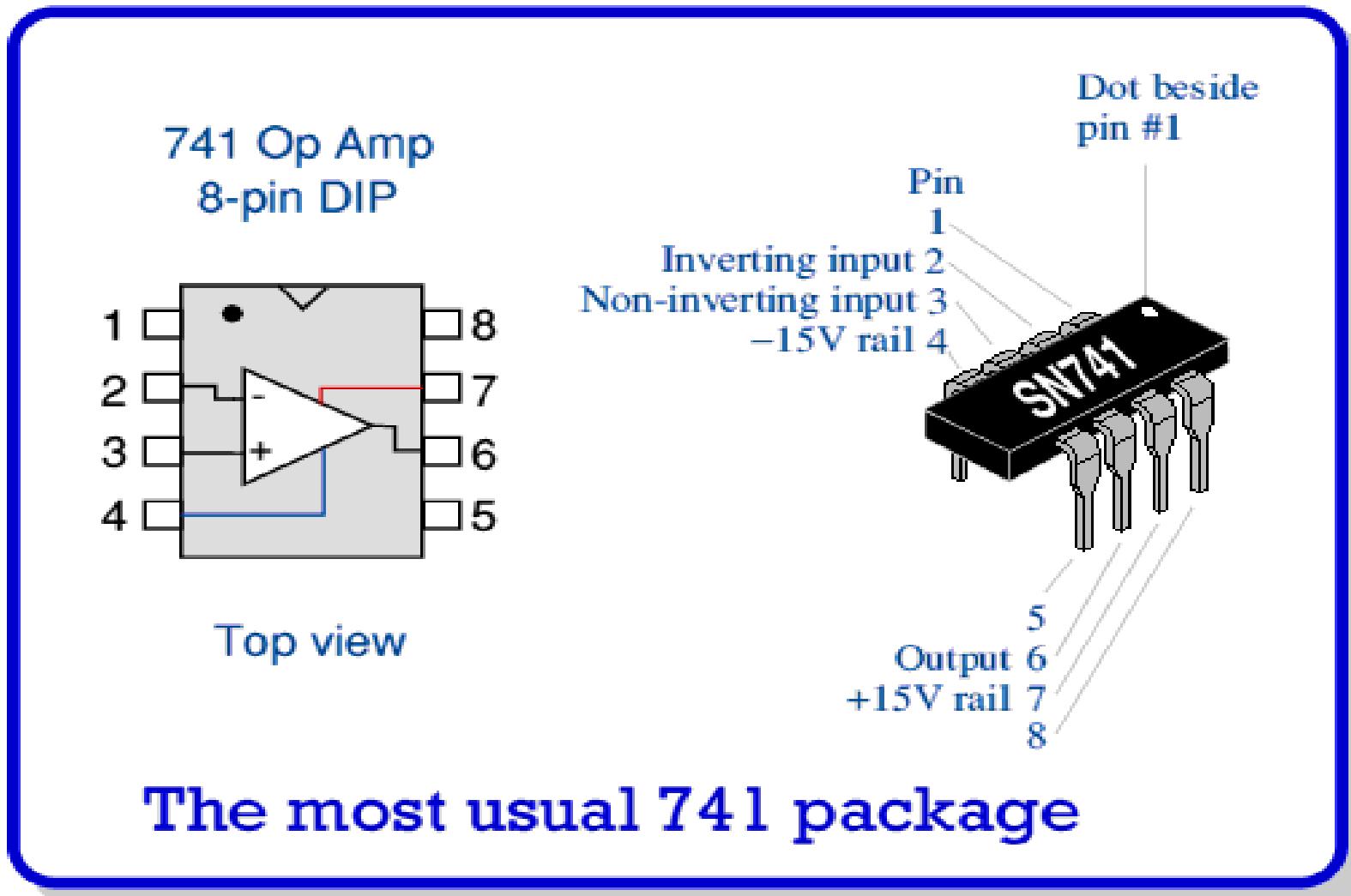


The most usual 741 package

# Symbol and Terminal

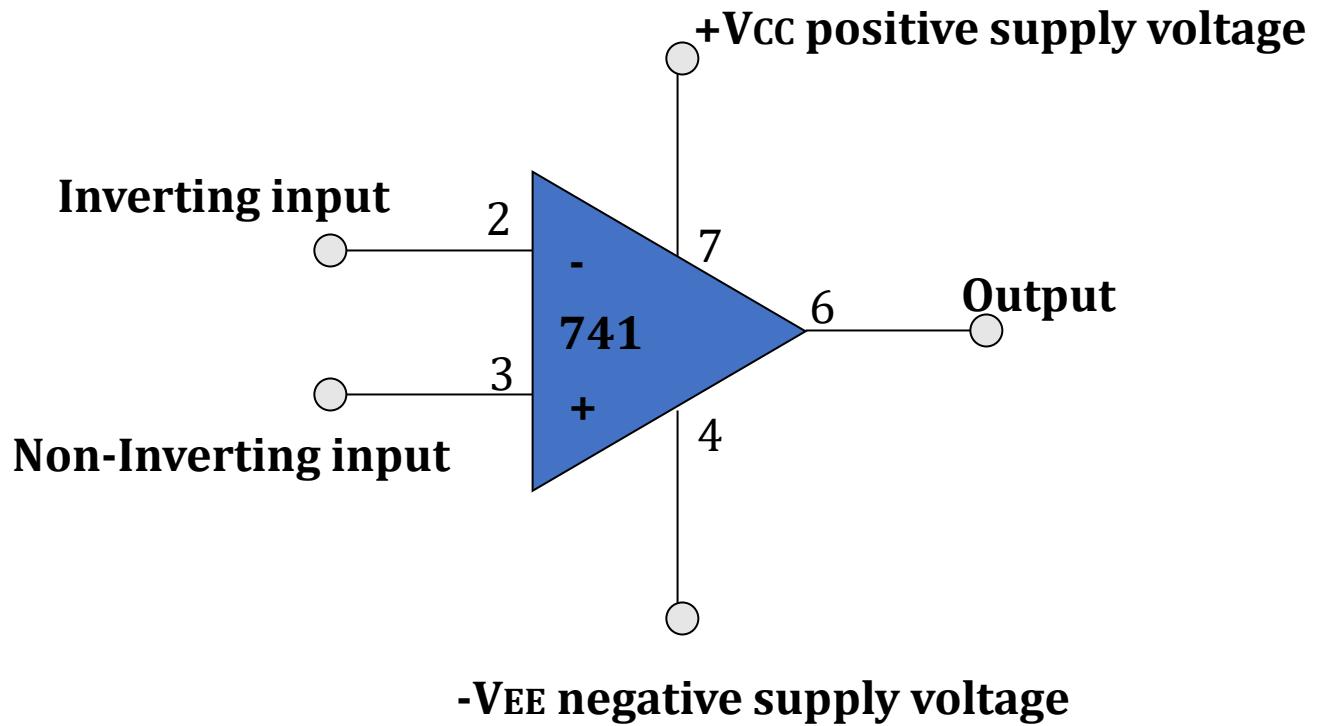

The **Operational Amplifier (op amp)** was **invented** in the 40's. Bell Labs filed a patent in 1941 and many consider the first practical **op amp** to be the vacuum tube K2-W **invented** in 1952 by George Philbrick.

Symbol :

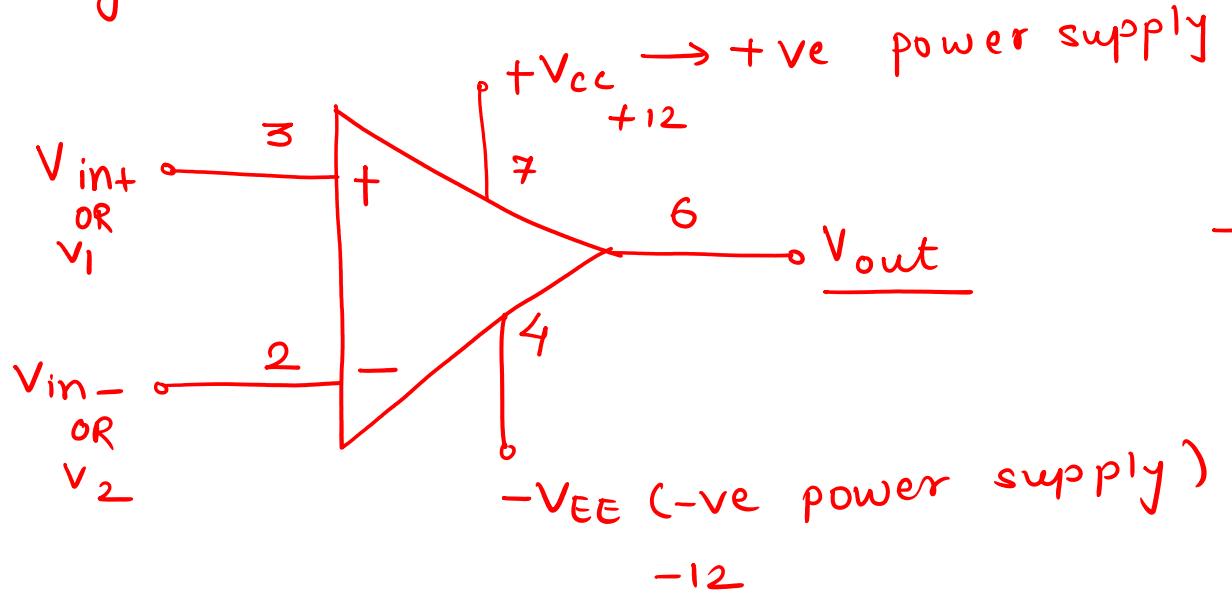


$$\rightarrow V_{out} = A (V_{int} - V_{in-}) \\ = A (v_1 - v_2)$$

5V      3V


$V_{int}$  : Non-inverting i/p

$V_{in-}$  : Inverting i/p

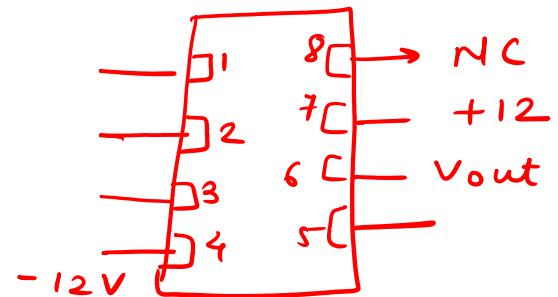


Pin 1 and 5 : offset null .


# Op-amp Symbols and Packages.

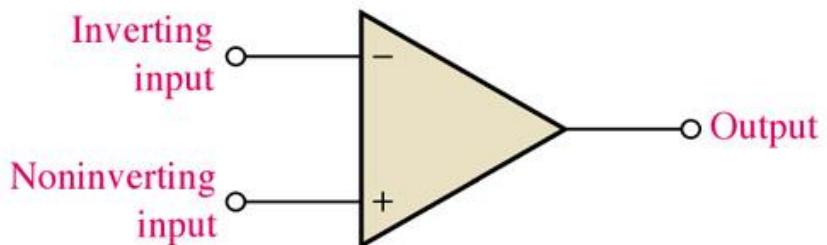


(a) Symbol

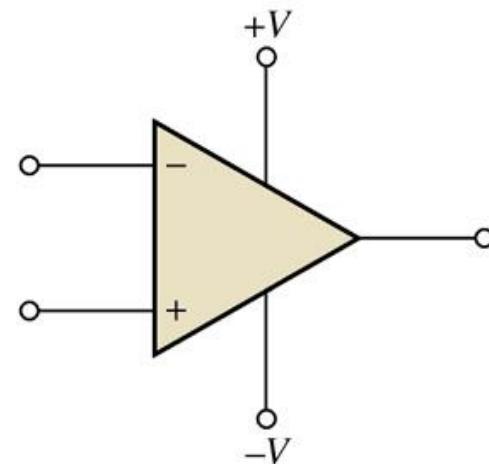


(b) Symbol with dc supply connections

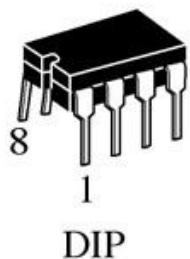

DIP

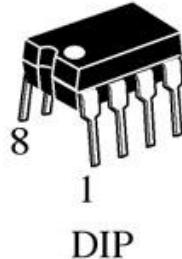

DIP

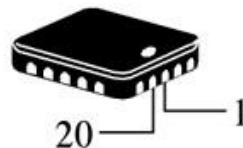

SMT




SMT

(c) Typical packages. Pin 1 is indicated by a notch or dot on dual-in-line (DIP) and surface-mount technology (SMT) packages, as shown.

# **Manufactures of OP-AMP IC 741**

- The manufactures of Op-amp ICs are companies like Fairchild, National semiconductor, Motorola, Texas Instruments and Signetics.
- The identifying initials for some other companies are as follows:
  1. National semiconductors : LM 741
  2. Motorola : MC 741
  3. RCA : CA 741
  4. Texas instruments : SN 52741
  5. Signetics : N 5741

# Block Diagram of a Typical OP-AMP

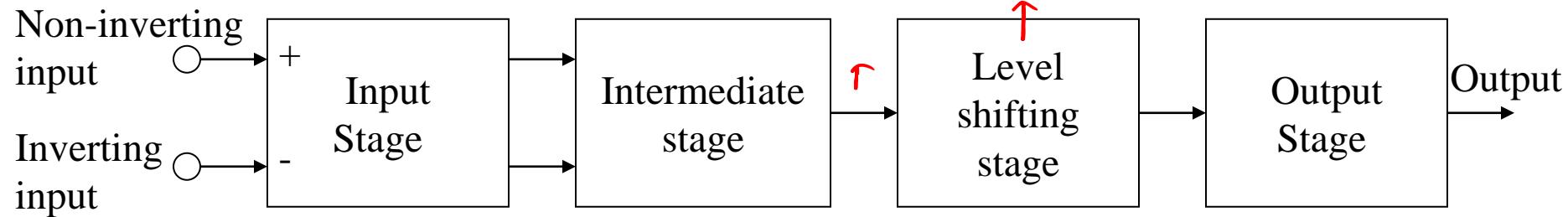

Dual input  
Balanced  
Output  
Differential  
amplifier

Dual input  
unbalanced →  
Output  
Differential  
amplifier  
single ended .


Emitter follower  
Using constant  
Current source

common  
collector

Complementary  
Symmetry  
Push-pull  
amplifier

provide  
low  
o/p  
impedance


providing  
constant  
current

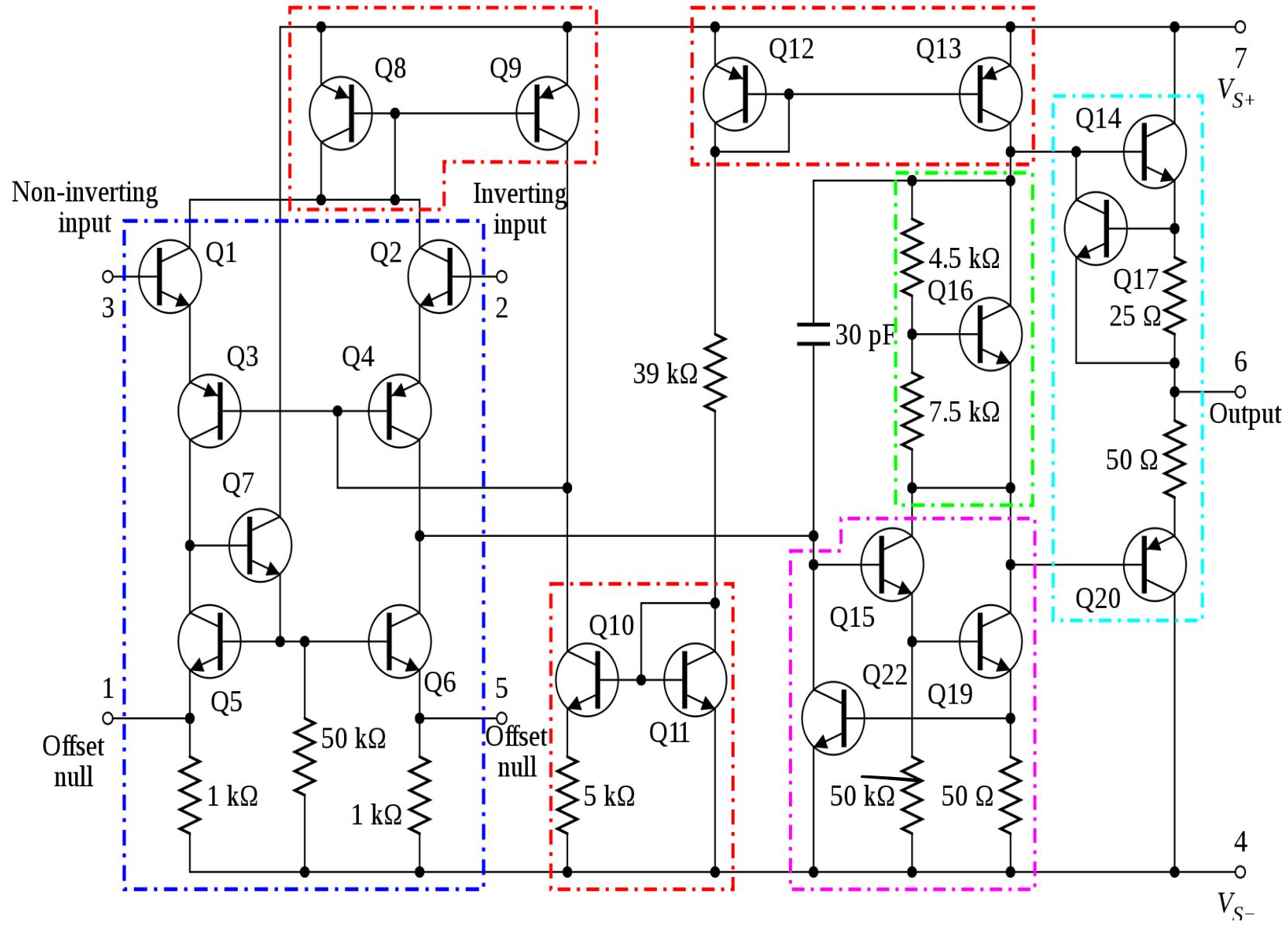


This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.
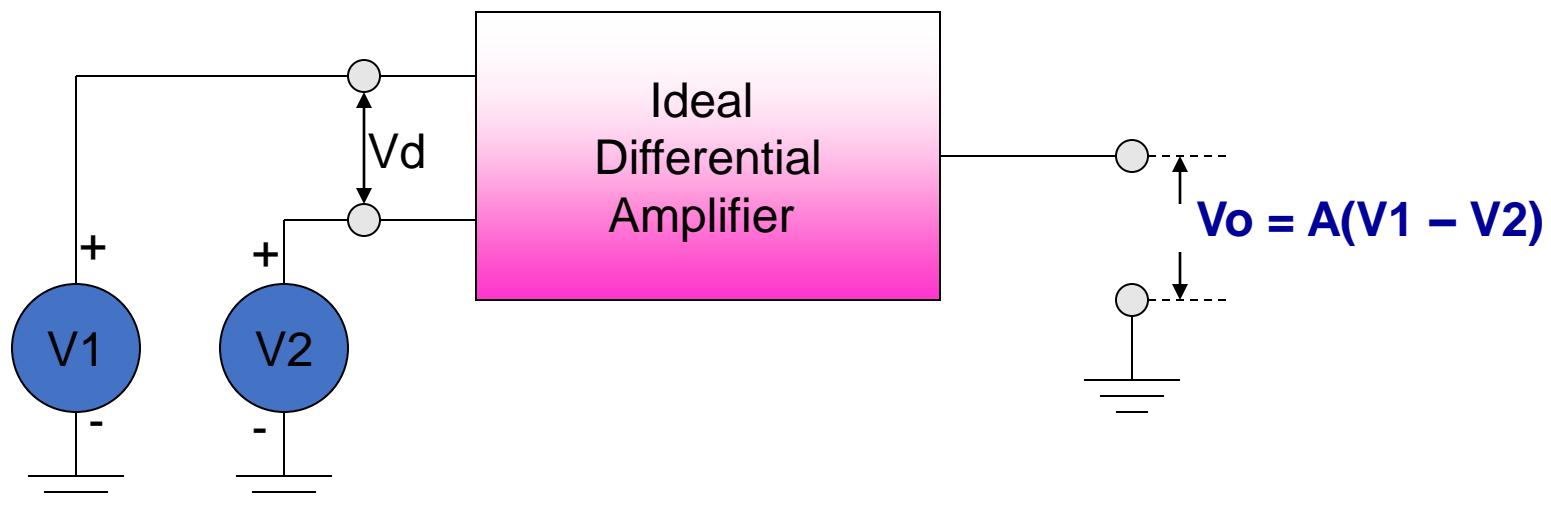
## Ideal Differential Amplifier

- An ideal differential amplifier is expected to amplify the differential signal present between its two inputs.
- It is also the basic stage of an integrated Op-amp with differential input.



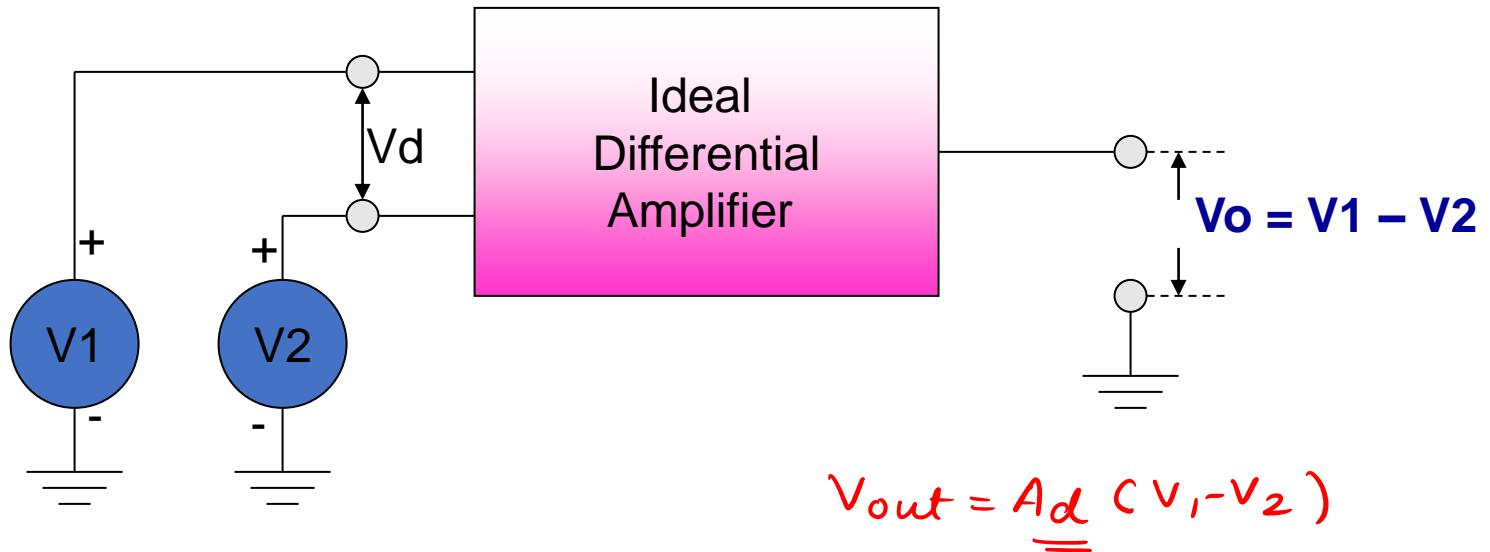

### Differential Gain -

- $V_o = \underline{A_d} ( V_1 - V_2 )$ , where  $A_d$  is called as the differential gain.
- The differential gain can be defined as the gain with which the differential amplifier amplifies the differential signal.

$$V_o = A_d V_d$$


$$\text{as, } V_d = V_1 - V_2$$

$$\text{Gain } A_d = V_o / V_d$$

$$A_d (\text{dB}) = 10 \log_{10} [ V_o / V_d ]$$

$$A_d (\text{dB}) = 10 \log_{10} \left( \frac{V_o}{\underline{V_d}} \right)$$

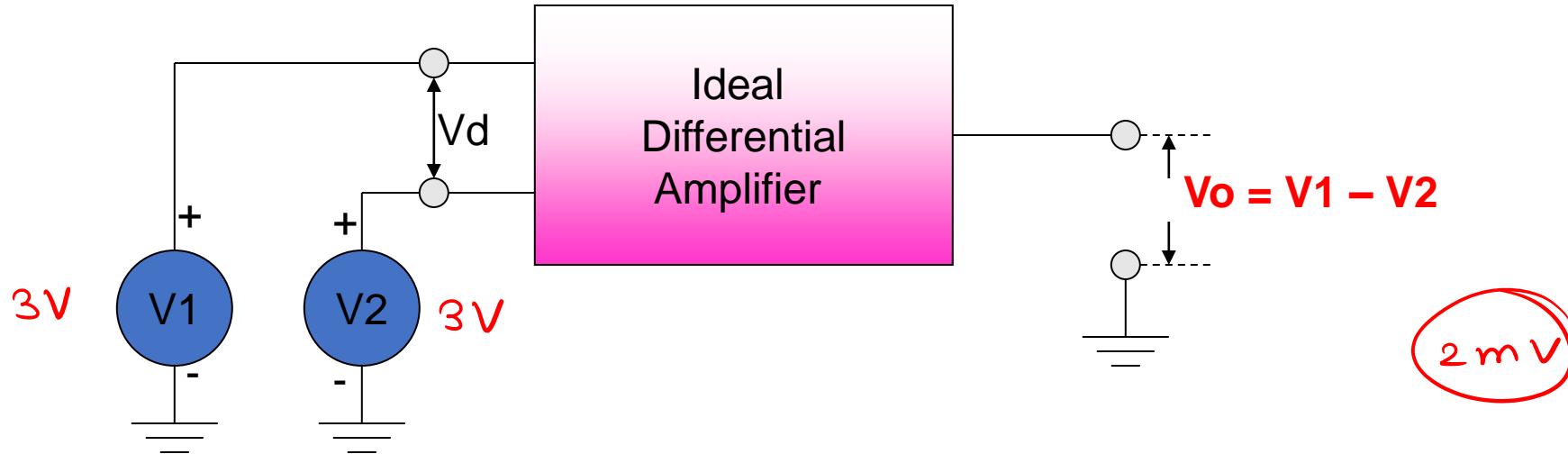
$$= 10 \log_{10} \left( \frac{V_o}{V_1 - V_2} \right)$$




## Common Mode Signal $(V_1 = V_2 = V)$

- A common signal to both the input terminals ( i.e.  $V_1=V_2=V$ ) is called as common mode signal.
- The output voltage produced by an ideal differential amplifier is zero for the common mode signal.



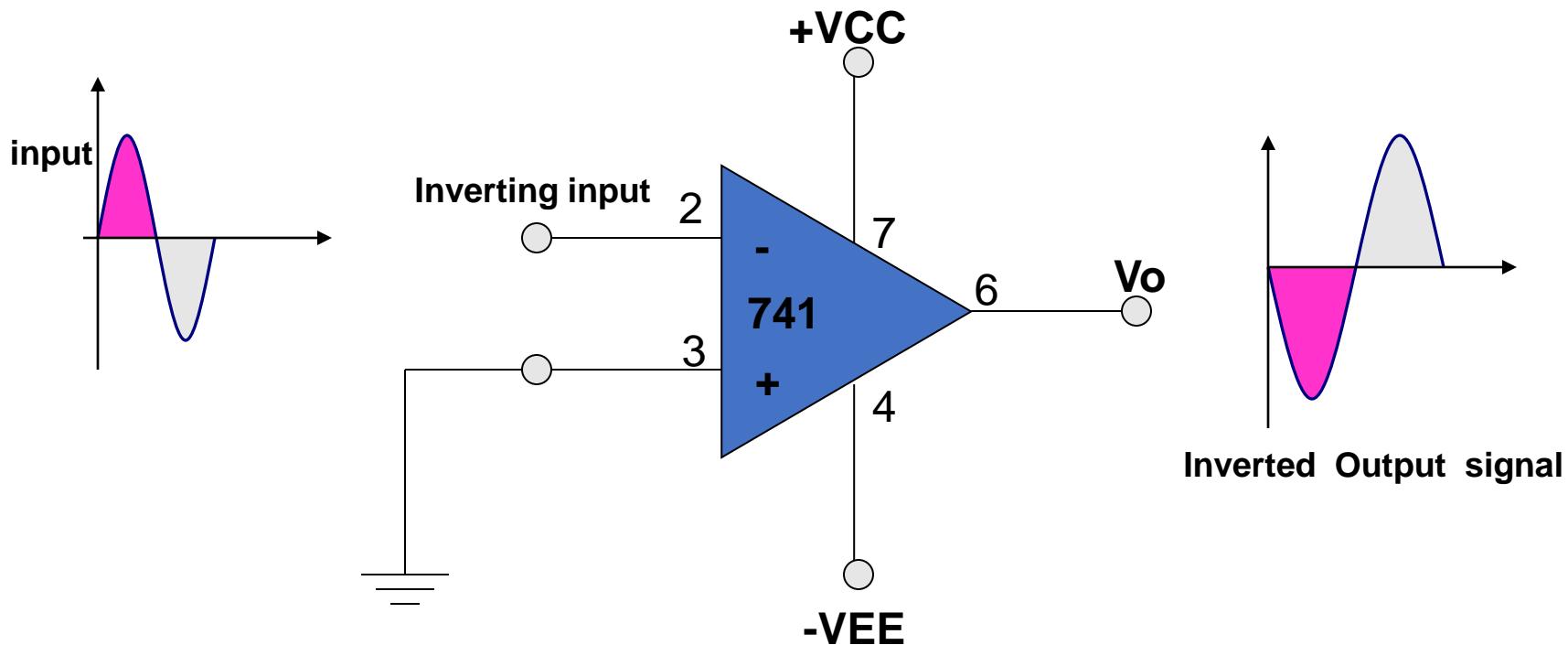
**Input and output signals  $180^\circ$  phase shift when the input signal is applied to the inverting (-) terminal.**



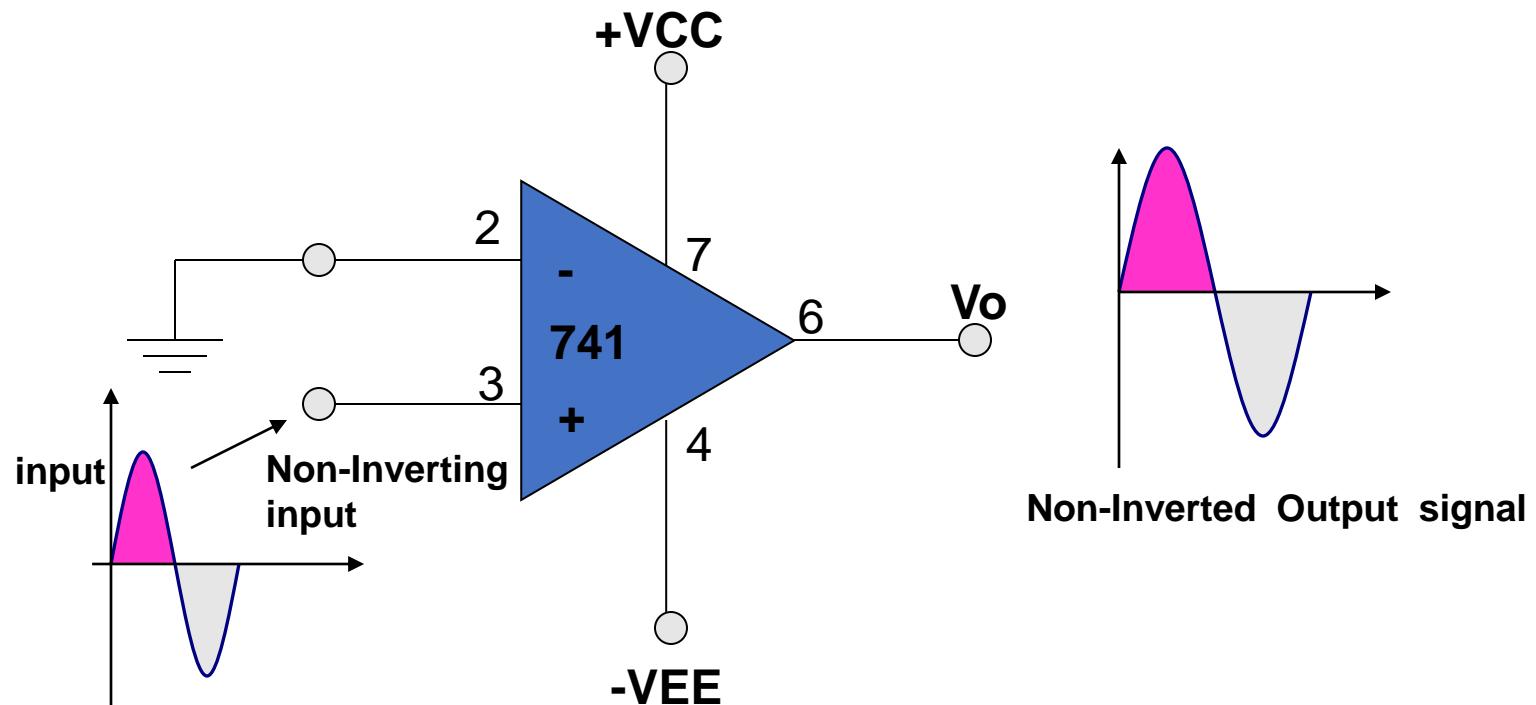**Input and output signals  $0^{\circ}$  phase shift when the input signal is applied to the Non-inverting (+) terminal.**



# Equivalent Circuit of an OP-AMP

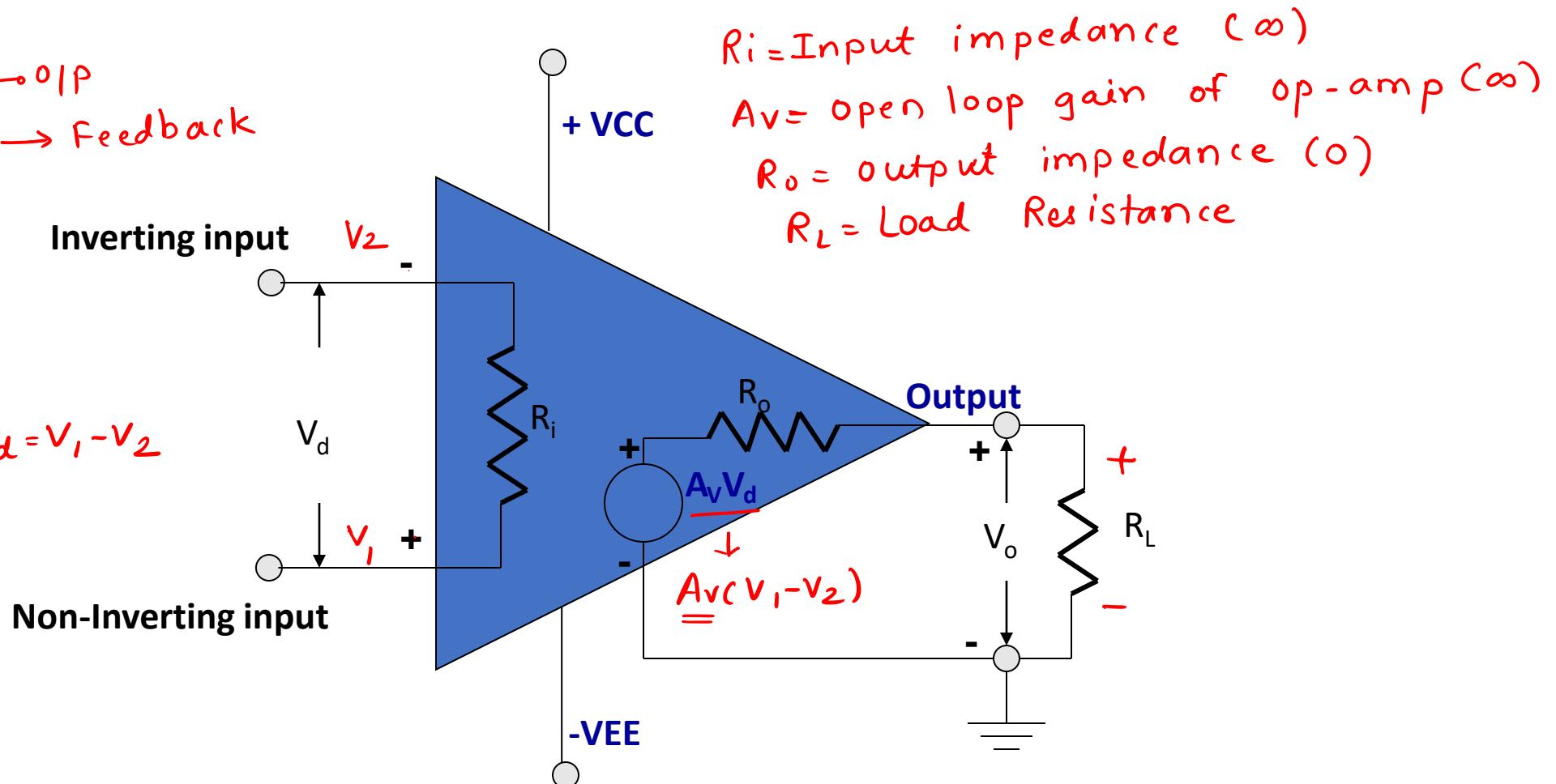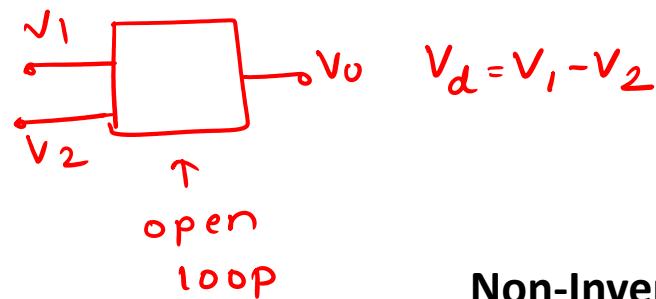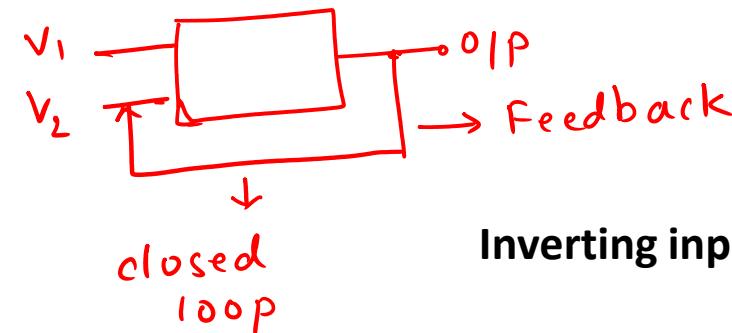


$$A_d = 2 \times 10^3$$

$$A_c = 10$$

$$CMRR = \frac{A_d}{A_c}$$

$$= 200$$

$$= 46 \text{ dB}.$$

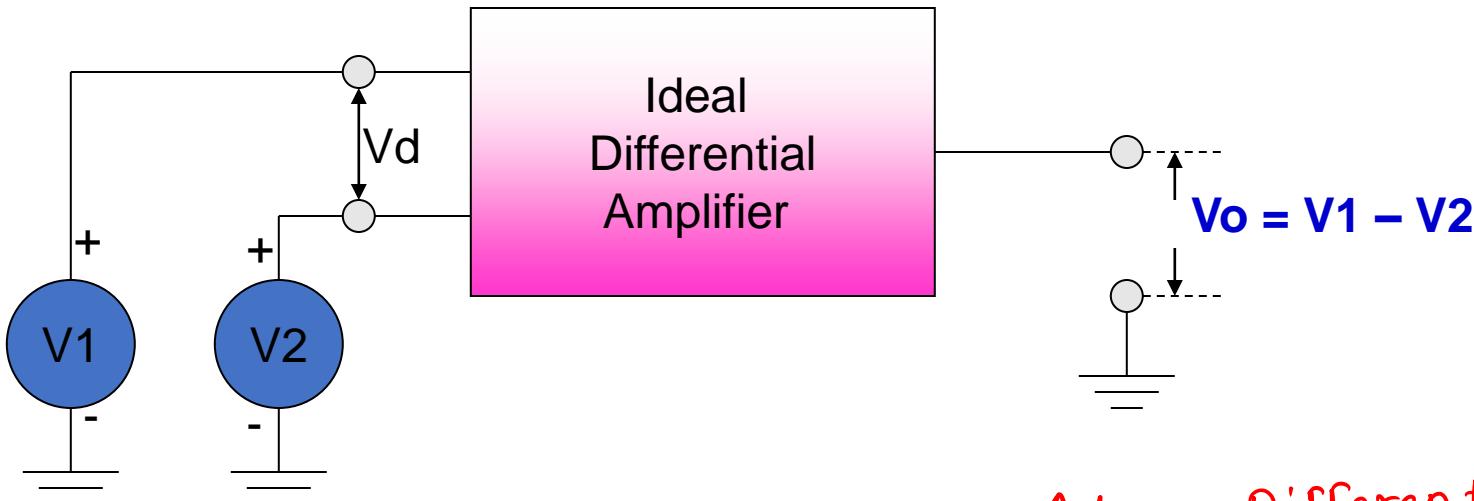


## Common Mode Rejection Ratio (CMRR)

$$CMRR = \frac{A_d}{A_c} = \frac{\text{Differential Gain}}{\text{Common mode gain}} = \rho$$

- Common mode rejection ratio (CMRR) is the ability of a differential amplifier to reject the common mode signal successfully.
- CMRR is defined as the ratio of differential gain  $A_d$  and common mode gain  $A_c$ . It is denoted by letter “ $\rho$ ”.
- $CMRR = \rho = |A_d / A_c|$
- Ideally CMRR should be infinite and practically it should be as high as possible.

$$CMRR = 20 \log_{10} \left( \frac{A_d}{A_c} \right) \text{ (dB)}$$

# The Ideal OP-AMP

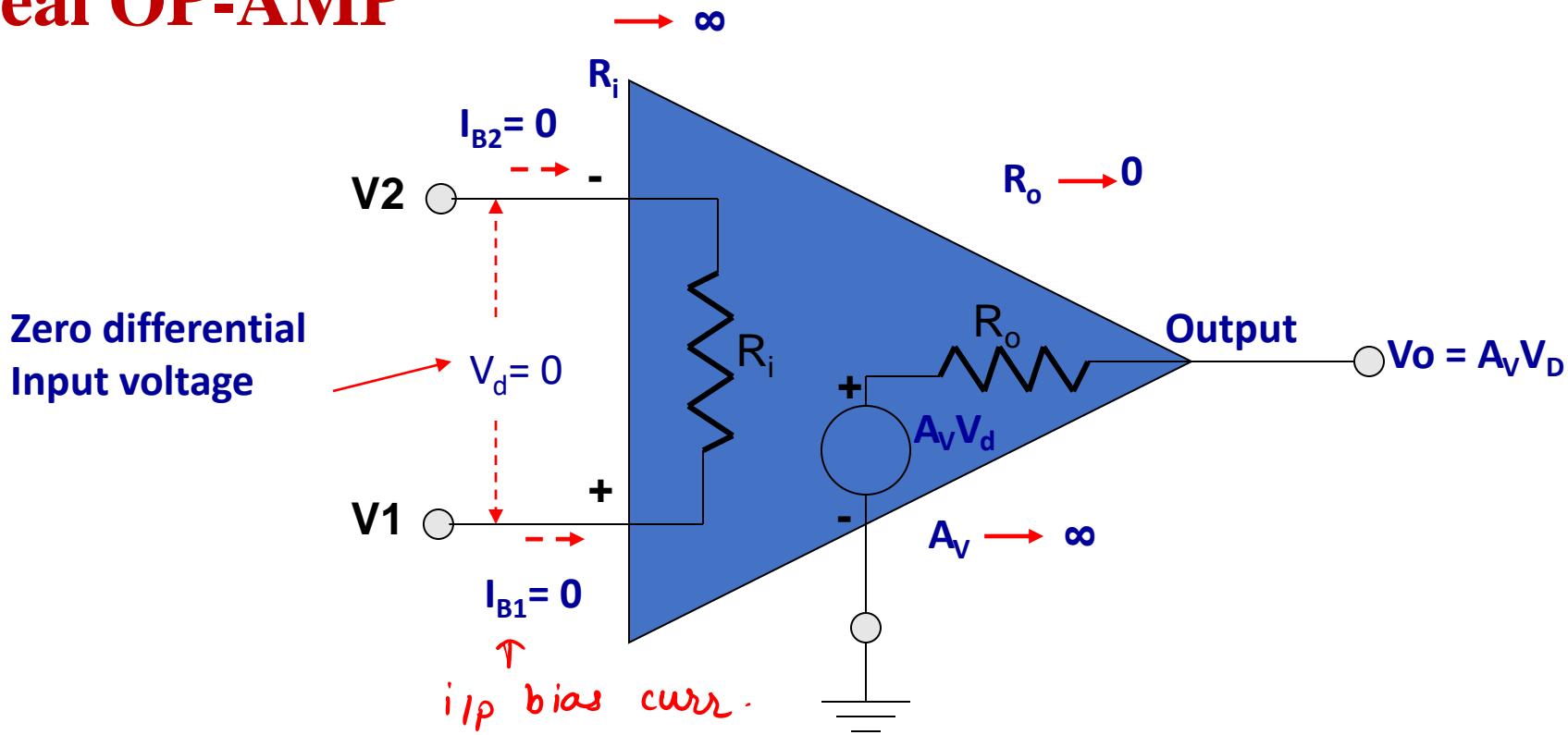

## Important characteristics of Op-Amp

1. Infinite voltage gain ( $\underline{A_v} \rightarrow \infty$ )


$$741 \rightarrow 2 \times 10^5$$

The open loop gain of an ideal OP-AMP is denoted by  $\underline{A_v}$ . It is the differential voltage gain and its value for an ideal OP-AMP is infinite.

$$\underline{V_o} = \underline{A_v} \underline{V_d}$$

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.

# The Ideal OP-AMP

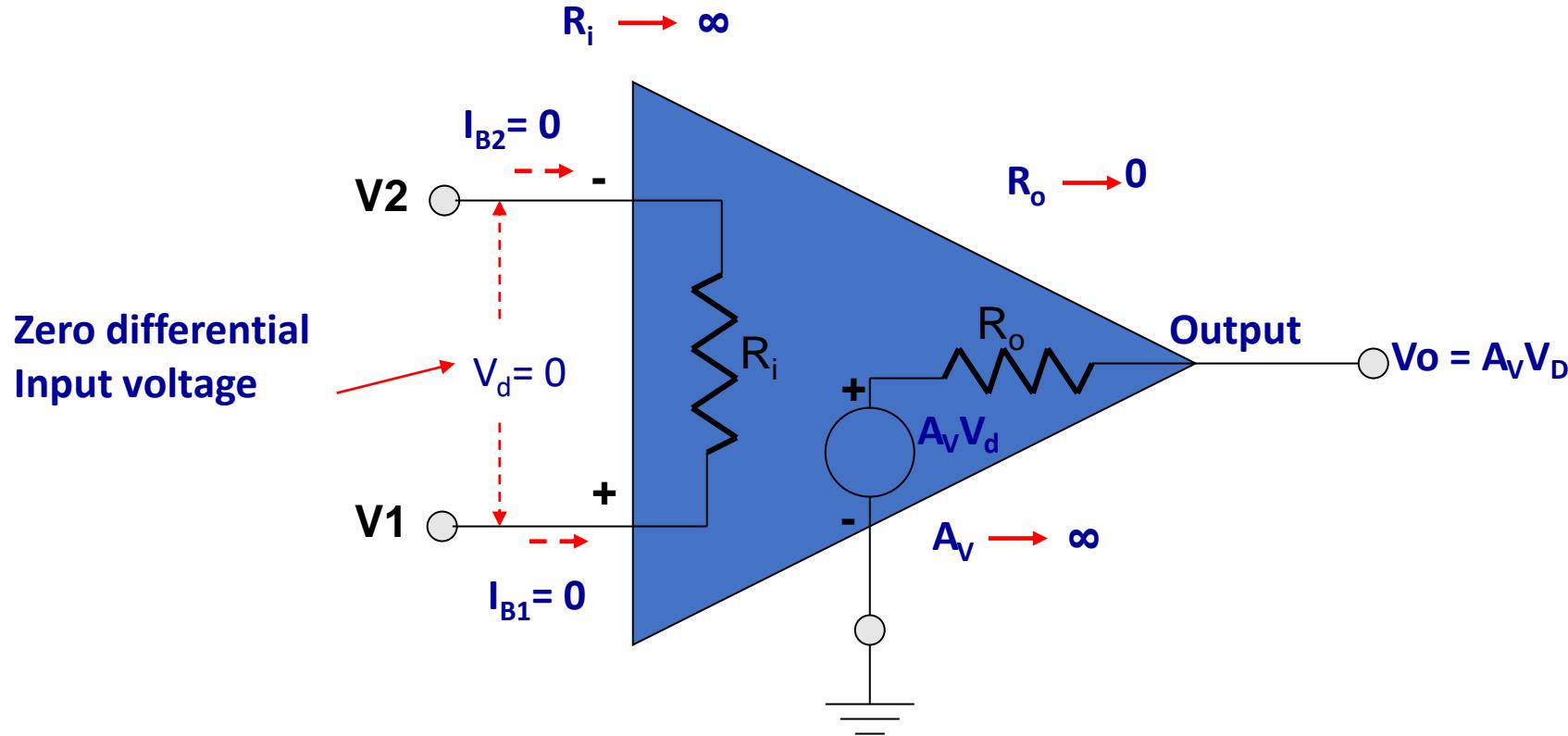


## 2. Infinite Input Resistance ( $R_i \rightarrow \infty$ )

- The input resistance  $R_i$  of an ideal OP-amp is infinite.
- Due to this, the current flowing in each input terminal will be zero.  $I_{B1} = 0$      $I_{B2} = 0$
- Due to infinite input resistance, almost any source can drive it and there is no loading of the source.

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.


# The Ideal OP-AMP

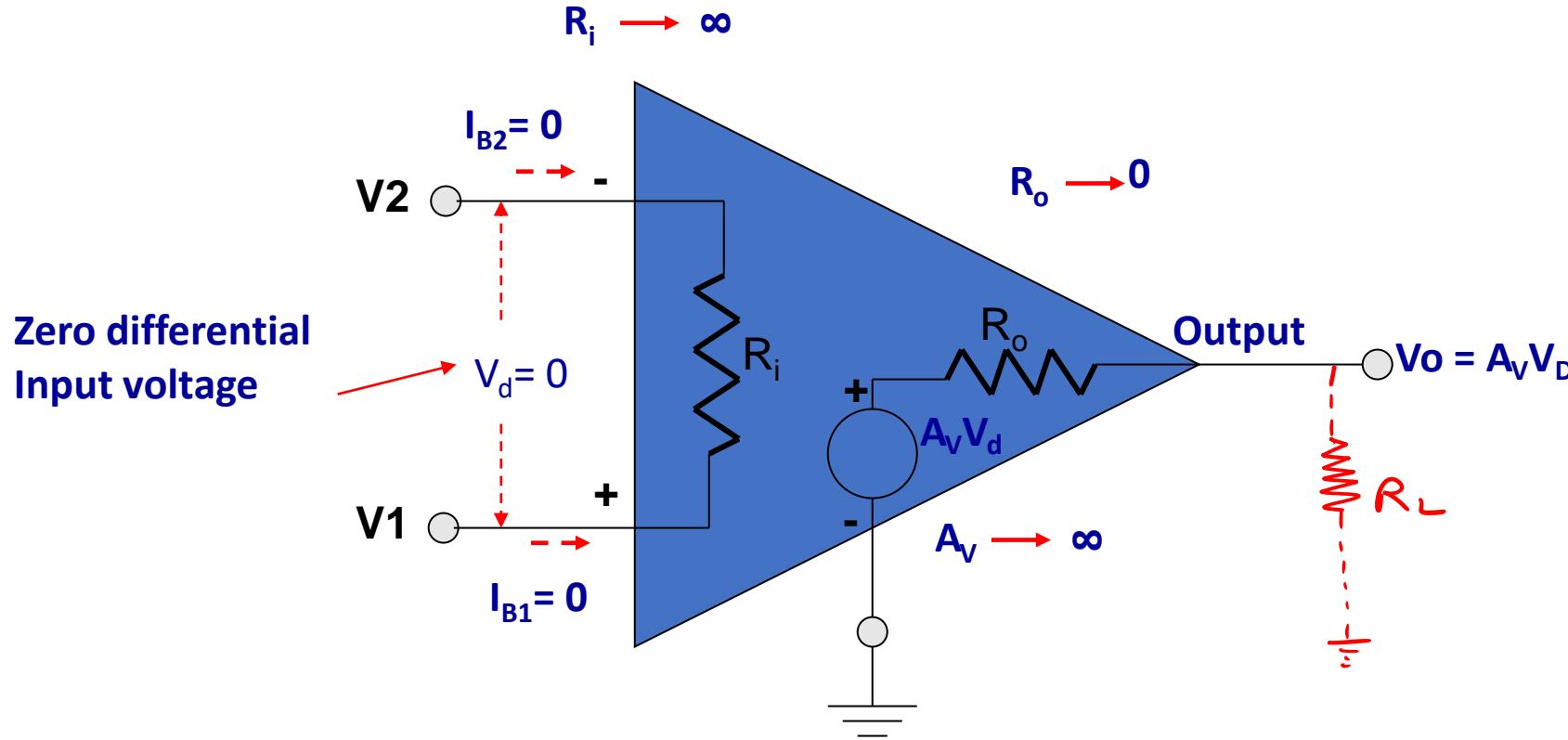

### 3. Zero Output Resistance ( $R_o = 0$ )

- The output resistance  $R_o$  of an ideal OP-amp is zero.
- Due to this, the ideal Op-amp can handle infinite number of other devices.

# The Ideal OP-AMP

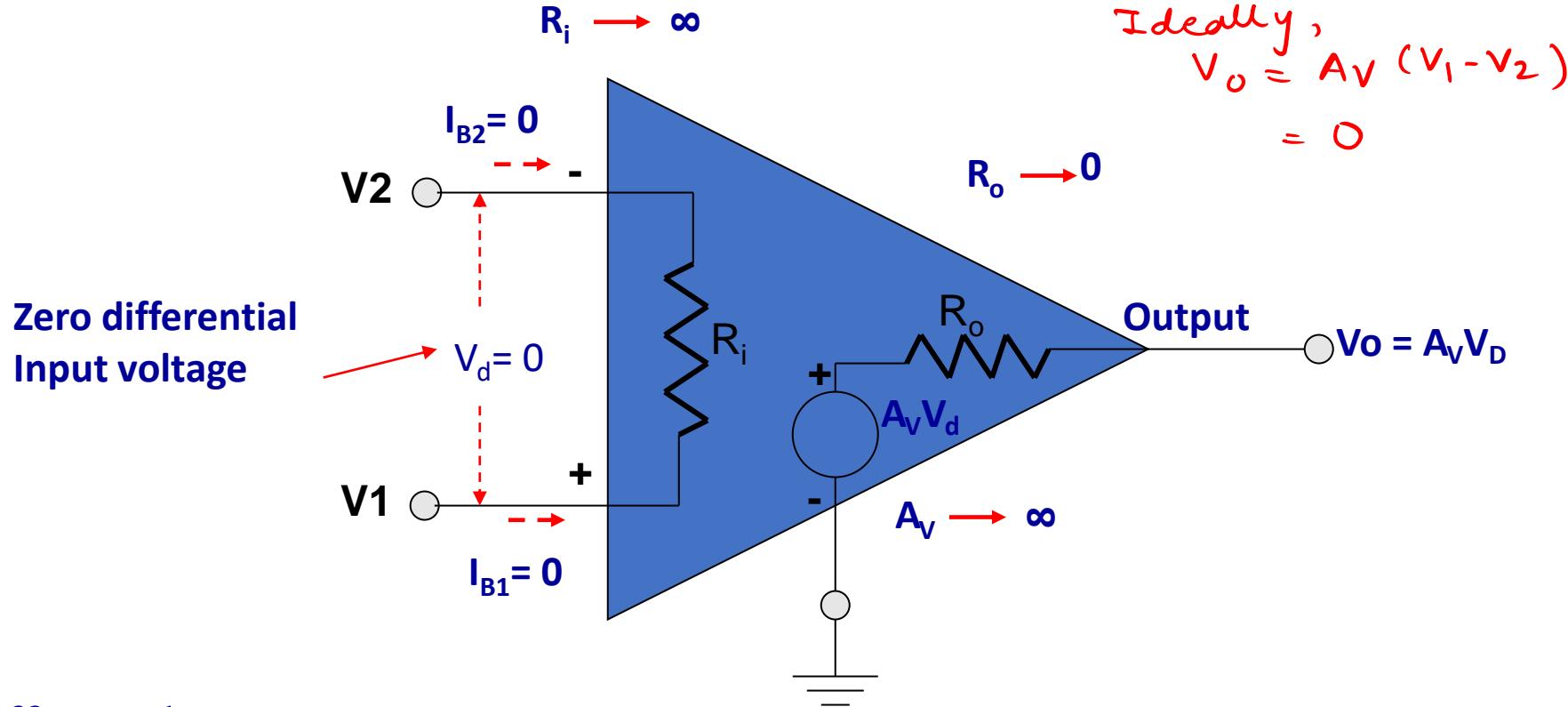


## 4. Zero offset voltage

( $\mu$ V / mV)

- In practical Op-amps a small output voltage is present even though both the inputs  $V_1$  and  $V_2$  are having a zero value. ( $V_1 = V_2 = 0$ )
- This voltage is called as the offset voltage. For ideal Op-amp the offset voltage is zero.
- That means output voltage is zero when input voltage is zero.


# The Ideal OP-AMP

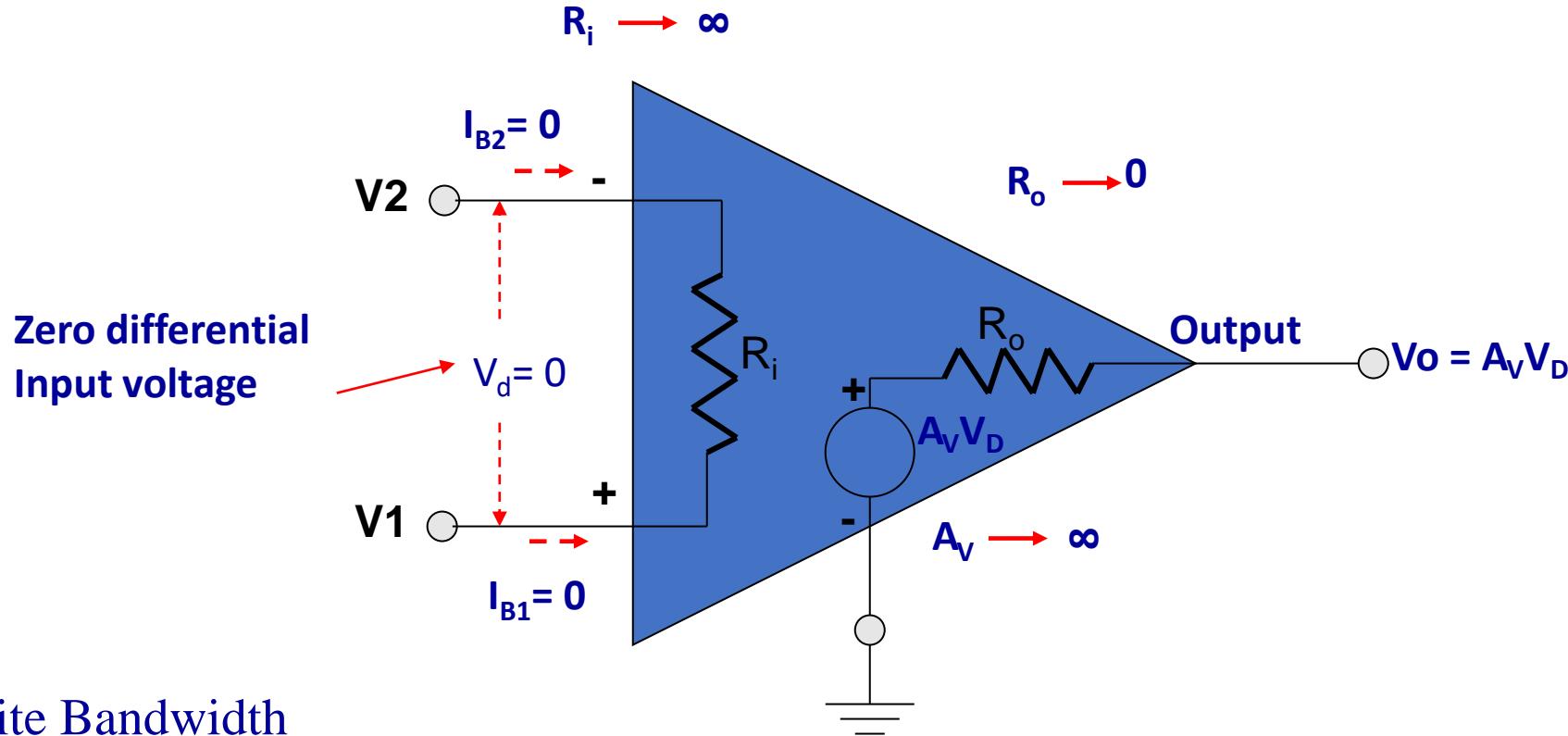

## 5. Infinite Bandwidth

- Bandwidth of an amplifier is the range of frequencies over which all the signal frequencies are amplified almost equally.
- The bandwidth of an ideal Op-amp is infinite. So, it can amplify any frequency from zero to infinite hertz.
- Thus, the gain of an ideal amplifier is constant from zero to infinite hertz.

# The Ideal OP-AMP

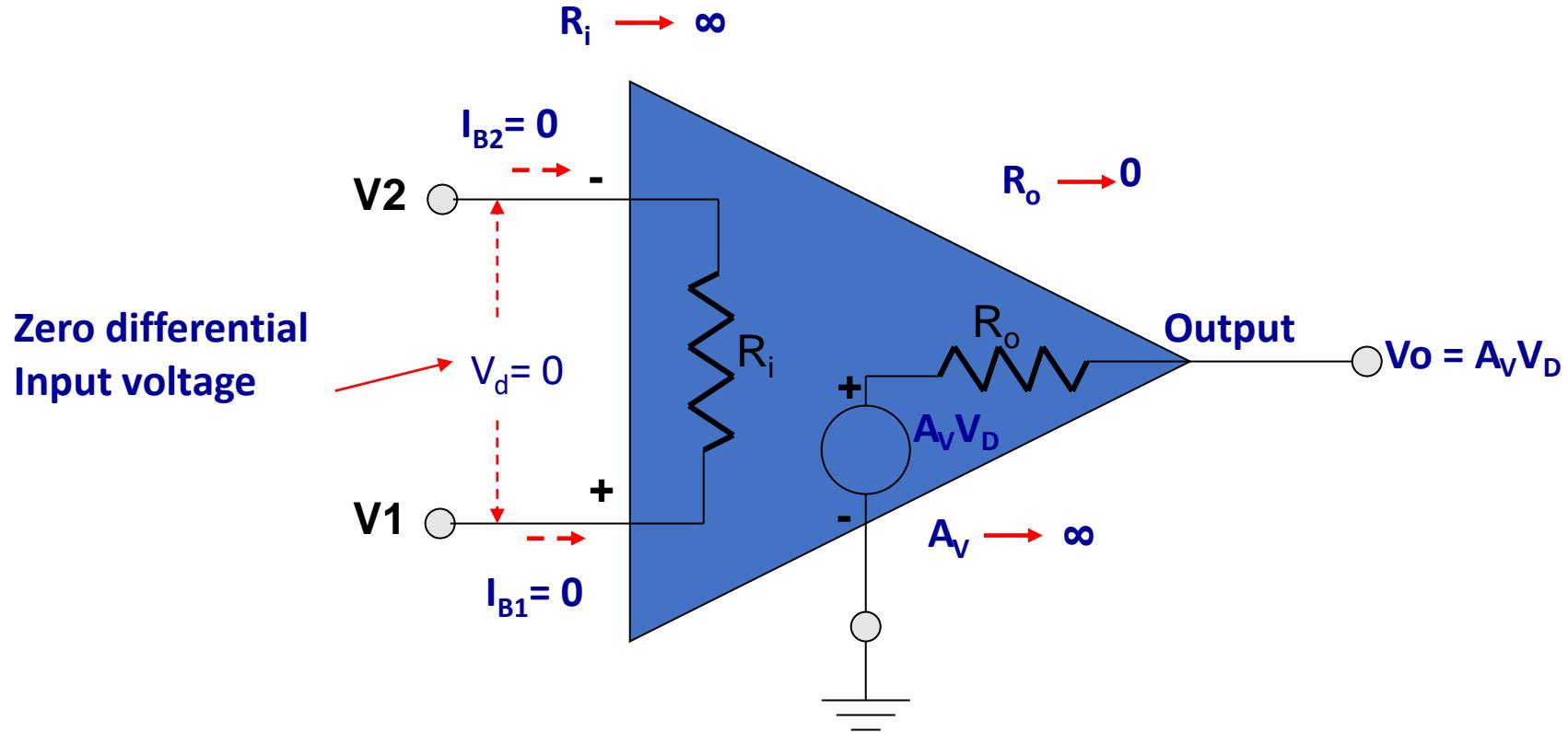

## 6. Infinite CMRR

- For an Op-amp, the common mode rejection ratio (CMRR) is defined as the ratio of differential gain to common mode gain.
- CMRR is infinite for the ideal Op-amp.

# The Ideal OP-AMP


$$V_1 = 5V$$

$$V_2 = 3V$$

$$\rightarrow V_1 = 7V$$

$$V_2 = 5V$$

Zero differential  
Input voltage

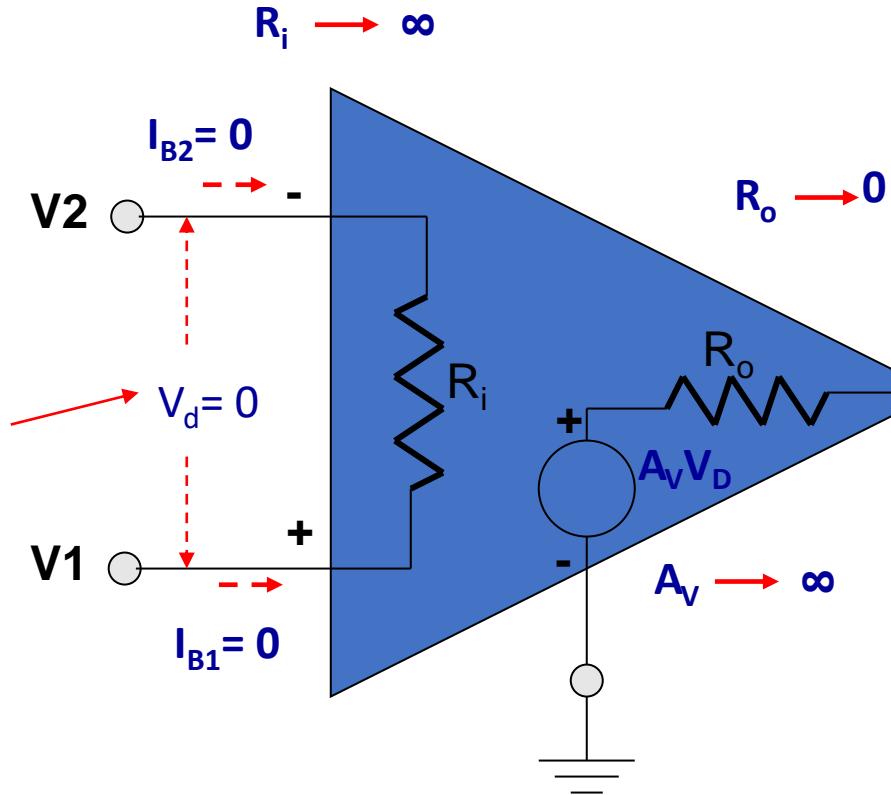

$$\text{slew rate} = \frac{dV_{out}}{dt} \quad (\frac{V}{\mu\text{sec}})$$

$$dt \rightarrow 0$$

$$\text{slew rate} = \infty.$$

$dV_{out} = \text{change in}$   
 $\text{o/p vtg}$


$$V_o = A_v V_D$$

$dt = \text{time required}$
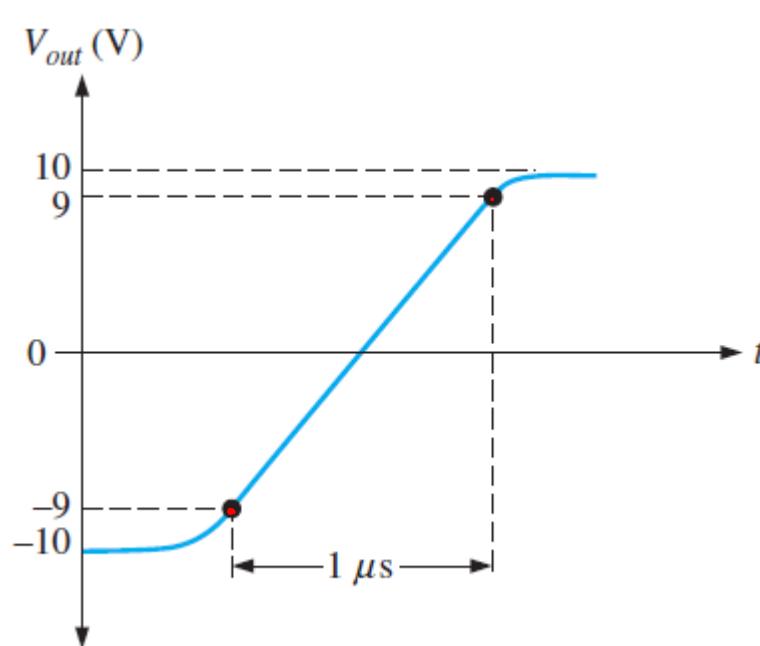
## 7. Infinite Slew Rate


- The slew rate of an ideal Op-amp is infinite so that the output voltage changes occur simultaneously with the input voltage changes.

The output voltage of a certain op-amp appears as shown in Figure in response to a step input. Determine the slew rate.



$$\begin{aligned}\rightarrow \text{slew rate} &= \frac{dV}{dt} \\ &= \frac{g - (-g)}{1 \mu\text{sec}} \\ &= \frac{18\text{V}}{1 \mu\text{sec}} \\ \text{slew rate} &= 18 \text{ V}/\mu\text{sec}\end{aligned}$$

# The Ideal OP-AMP

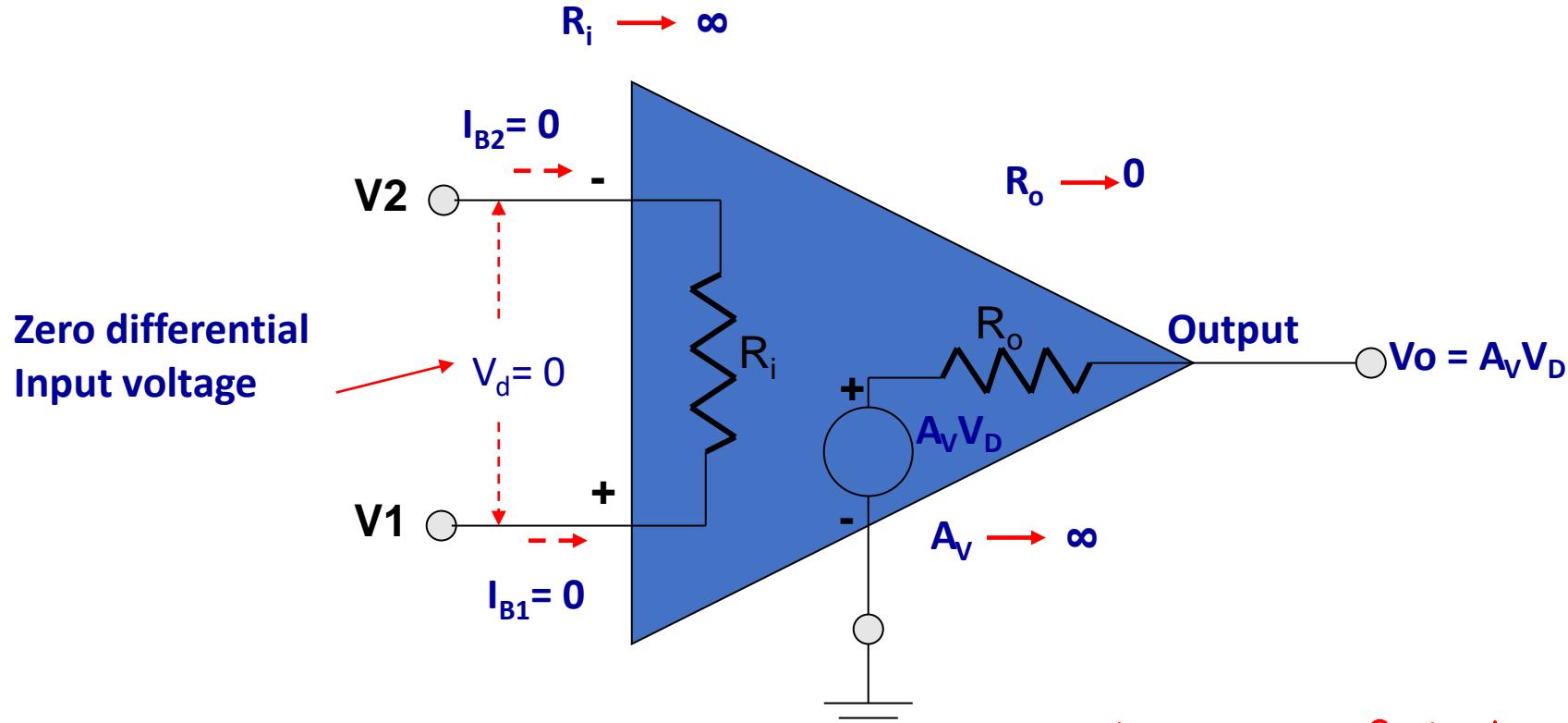

8. Zero power supply rejection ratio (PSRR). (SVRR - Supply Voltage Rejection Ratio)


- PSSR is a parameter which specifies the degree of the dependence of the Op-amp output on the changes in power supply.
- For an ideal Op-amp, PSRR = 0. That means, the output voltage does not change due to fluctuation in supply voltage.

# The Ideal OP-AMP

Input Offset Voltage ( $V_{io}$ ) ( Ideally,  $V_{io} = 0$  )

- It is the voltage which must be applied between two input terminals of op-amp to zero or null the output. (  $V_{out} = 0$  )
- It may be positive or negative.
- For a 741C OPAMP the maximum value of  $V_{io}$  is 6mV. It means a voltage  $\pm 6$  mV is required to one of the input to reduce the output offset voltage to zero.
- The smaller the input offset voltage the better the differential amplifier, because its transistors are more closely matched.

$$V_{io} = V_{dc1} - V_{dc2}$$

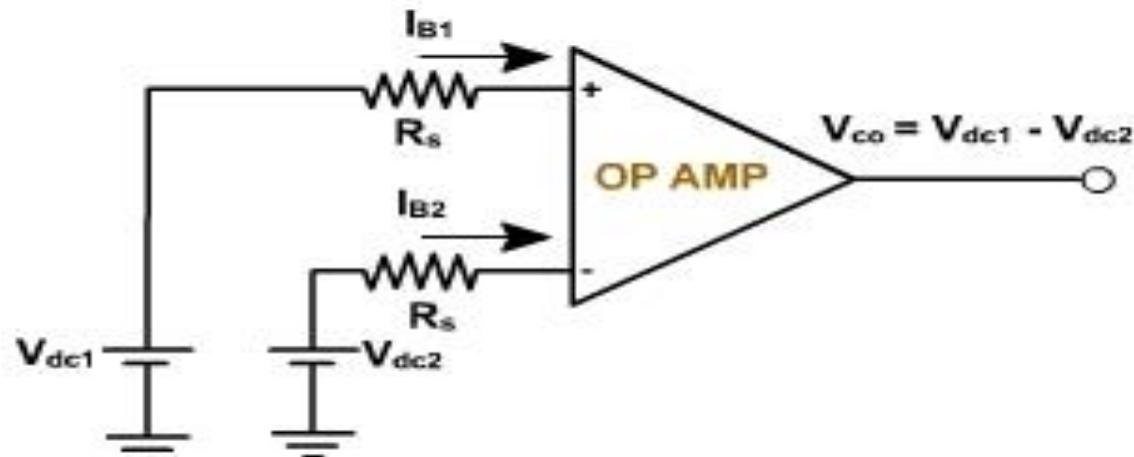

# The Ideal OP-AMP

$I_{B1}$  } input currents to op-amp  
 $I_{B2}$

## Input Offset Current ( $I_{io}$ ):

- It is the algebraic difference between the currents into the inverting and non-inverting terminals.


$$I_{io} = |I_{B1} - I_{B2}|$$

- The  $I_{io}$  for the 741C is 200nA maximum.
- As the matching between two input terminals is improved, the difference between  $I_{B1}$  and  $I_{B2}$  becomes smaller, i.e. the  $I_{io}$  value decreases further.
- For a precision OPAMP 741C,  $I_{io}$  is 6 nA.

Ideally,  $I_{io} = 0$

$$I_{B1} = 0$$

$$I_{B2} = 0$$

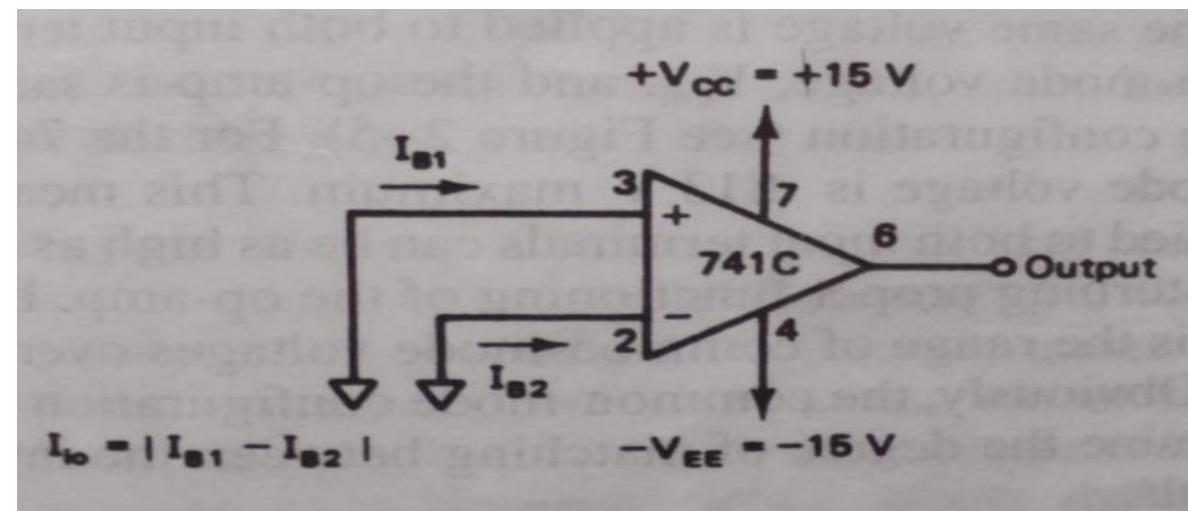

# The Ideal OP-AMP

## Input Bias Current ( $I_B$ ):

- The input bias current  $I_B$  is the average of the current entering the input terminals of amplifier i.e.


$$I_B = (I_{B1} + I_{B2}) / 2$$

- For 741C  $I_{B(\max)} = \underline{700 \text{ nA}}$  and for precision 741C  $I_B = \pm \underline{7 \text{ nA}}$
- The input bias current is the dc current required by the inputs of the amplifier to properly operate the first stage.

# Important Characteristics of OP-AMP IC 741

Sr. No.	Characteristics	Value for IC 741	Ideal value
1	Input resistance $R_i$	$2 \text{ M}\Omega$	$\infty$
2	Output resistance $R_o$	$75 \Omega$	0
3	Voltage gain $A_v$	$2 \times 10^5$	$\infty$
4	Bandwidth BW	1 MHz	$\infty$
5	CMRR	90 dB	$\infty$
6	Slew rate S	$0.5 \text{ V}/\mu\text{s}$	$\infty$
7	Input offset voltage	2 mV	0
8	PSRR	$150 \mu\text{V}/\text{V}$	0
9	Input bias current	50 nA	0
10	Input offset current	6 nA	0


# Pin Description of IC 741

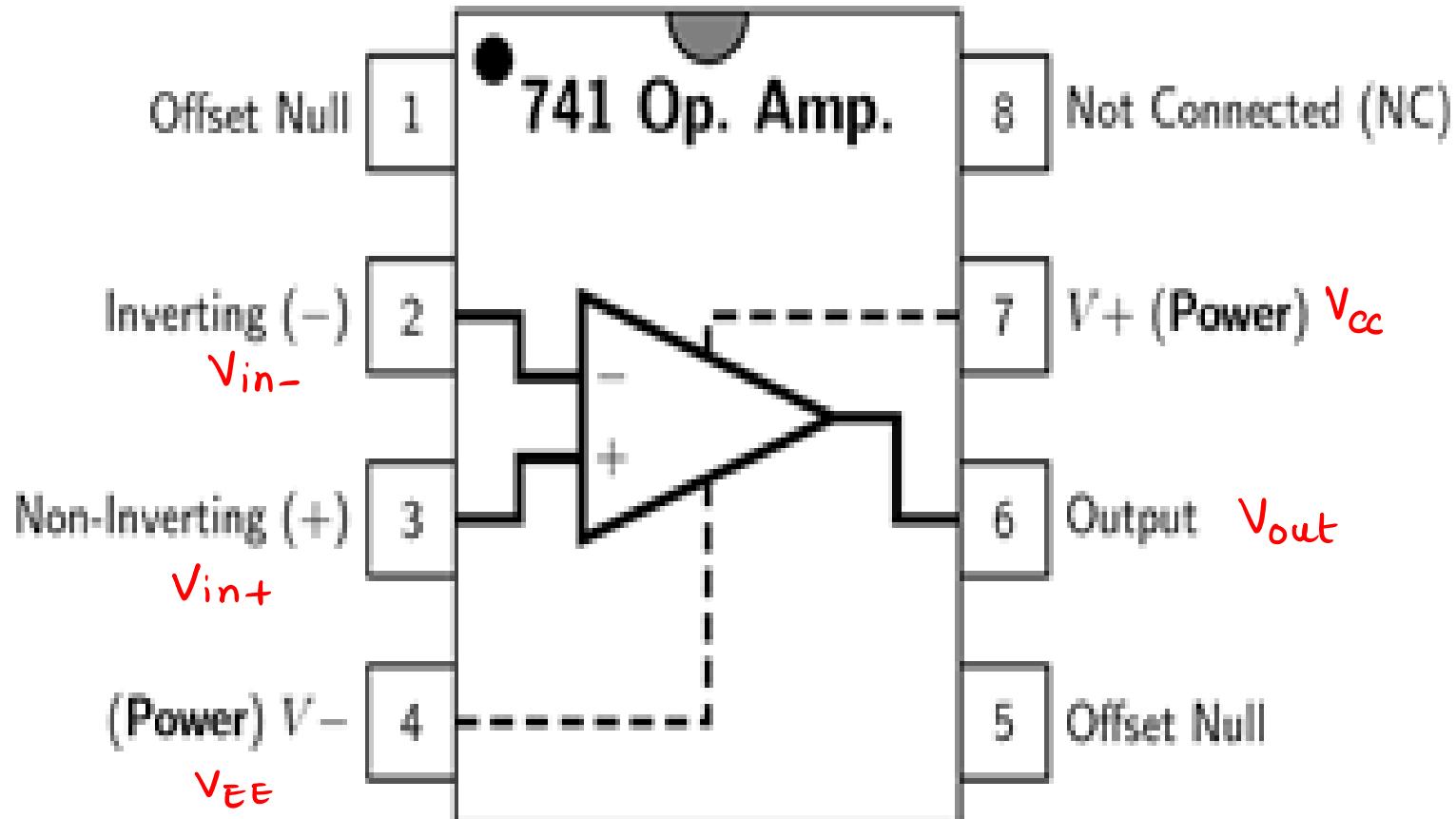

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.

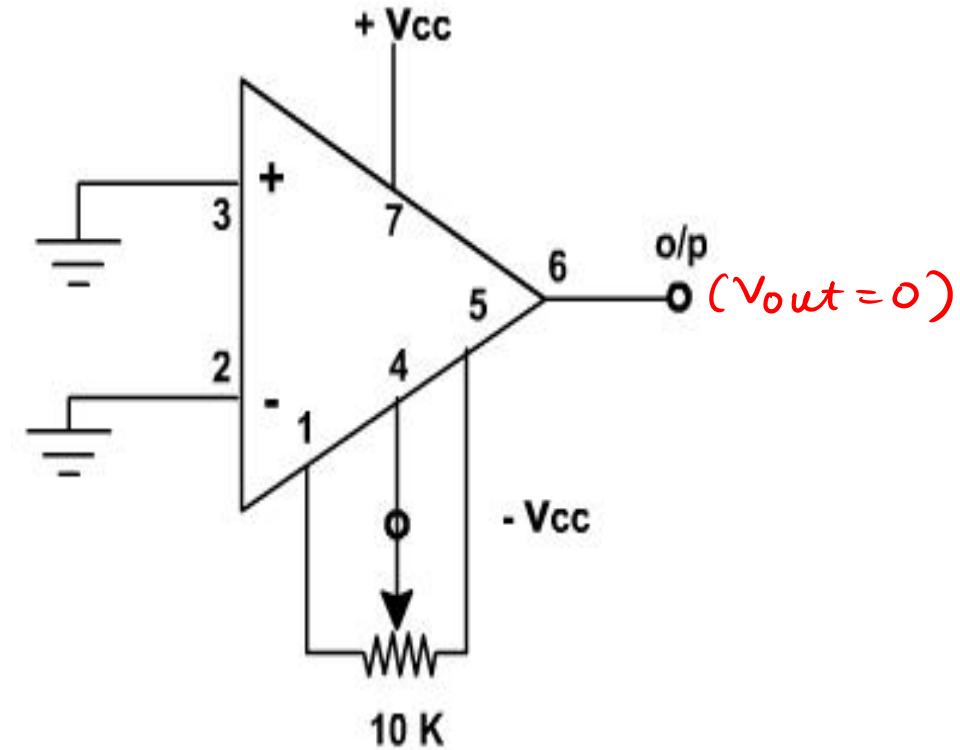
## **Offset Voltage Adjustment:**

- 741 OPAMP have offset voltage null capability. Pins 1 and 5 are marked offset null for this purpose. It can be done by connecting 10 K ohm pot between pins 1 and 5.
- By varying the potentiometer, output offset voltage (with inputs grounded) can be reduced to zero volts. Thus, the offset voltage adjustment range is the range through which the input offset voltage can be adjusted by varying 10 K pot.
- For the 741 IC, the offset voltage adjustment range is  $\pm 15 \text{ mV}$ .



185 : Offset null adjustment  
pins

# Open Loop Configuration of OP-AMP

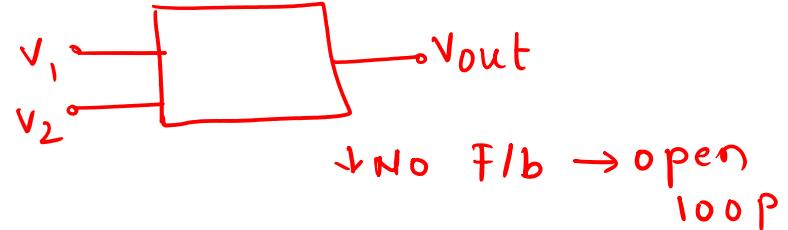

The meaning of open loop operation is that there is absolutely no feedback present from the output to input.

Example:


$$A_v = 10^3$$

$$V_1 = 2V$$

$$V_2 = 1V$$

$$\begin{aligned} V_o &= A_v \cdot V_d \\ &= 10^3 (2 - 1) \\ &= 10^3 V \end{aligned}$$

$$\underline{\underline{V_o = 15V}}$$

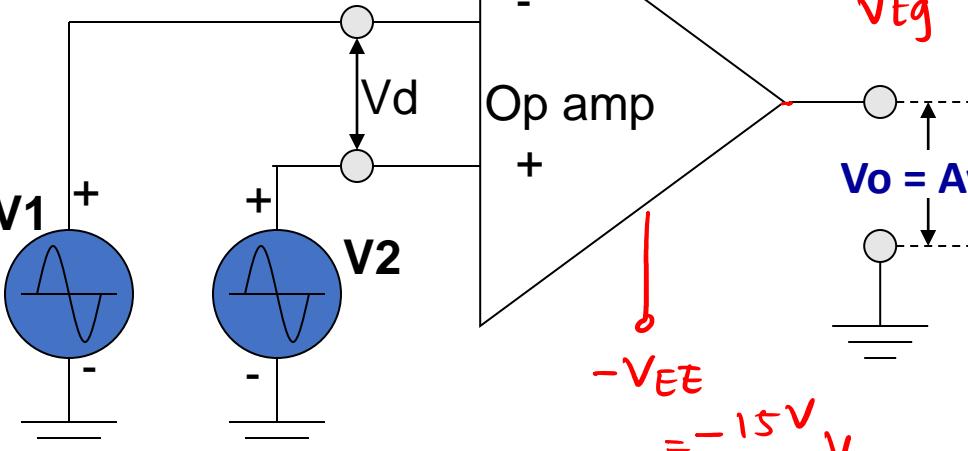

$$V_{CC} = +15V$$

$$Av = \text{open loop}$$

vtg gain of  
op-amp

$$V_o = A_v V_d$$


$$-V_{EE}$$

$$= -15V$$

$$V_{out} = A_v(V_d)$$

$$= A_v(V_1 - V_2) \pm V_{sat} = \pm V_{cc}$$

$V_{csaturation})$

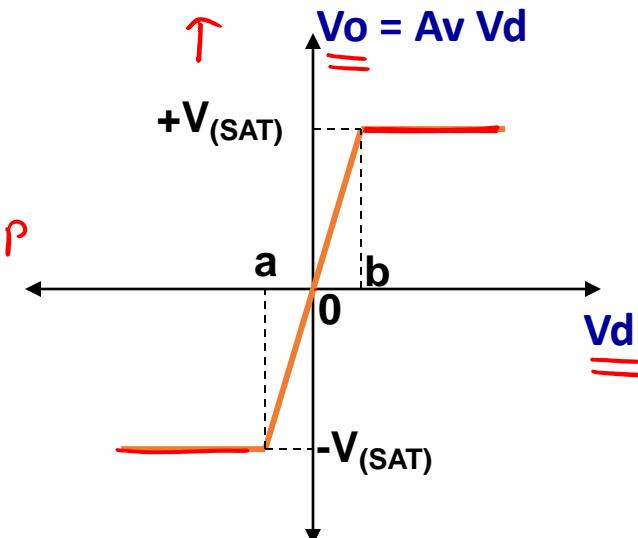

$$V_{sat} = V_{cc} \pm 2V$$

# Open Loop Configuration of OP-AMP


$$\frac{V_1}{V_2} = \frac{30\mu V}{25\mu V}$$

$$A_v = 10^3$$

$$V_o = A_v \cdot V_d$$
$$= 10^3 (5 \times 10^{-6})$$

$$= 5 \times 10^{-3} V$$

$$= 5 mV$$

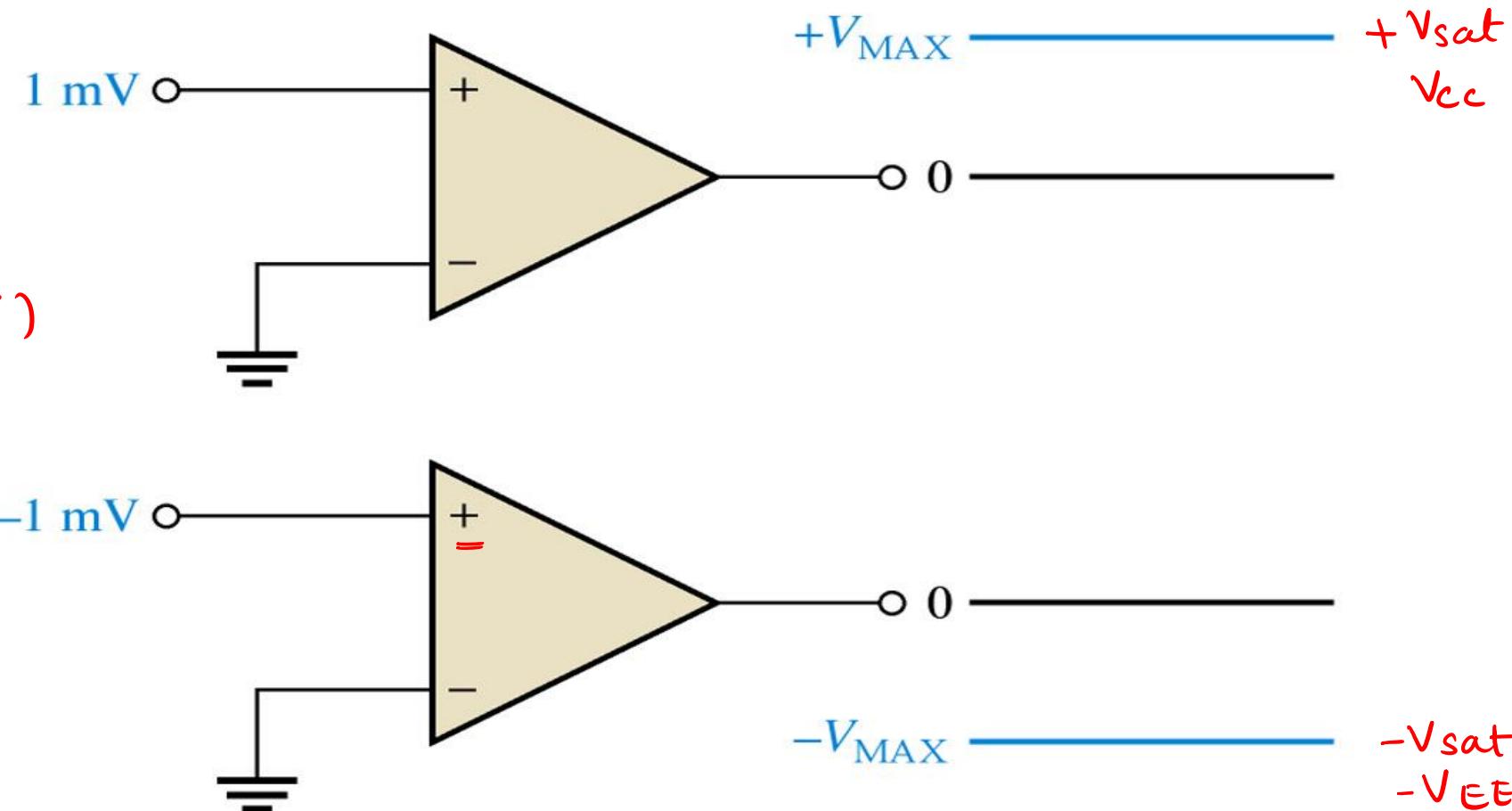

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.

## Why Op-amp not used as an amplifier in the open loop configuration ?

Large Av

(output is limited by supply vtg)

- Due to very large open loop gain, distortion is introduced in the amplified output signal.
  - The open loop gain does not remain constant, it varies with change in temperature and power supply.
  - For this reason, the Op-amp is not used in practice as an amplifier.
  - **However, the Op-amp in open loop configuration is used in application such as comparator.**


# Close Loop Configuration of OP-AMP

- In the closed loop configuration, some kind of “feedback” is introduced in the circuit.
- A part of output is returned back or fed back to the input.

Types of feedback

➤ Positive feedback or Regenerative feedback

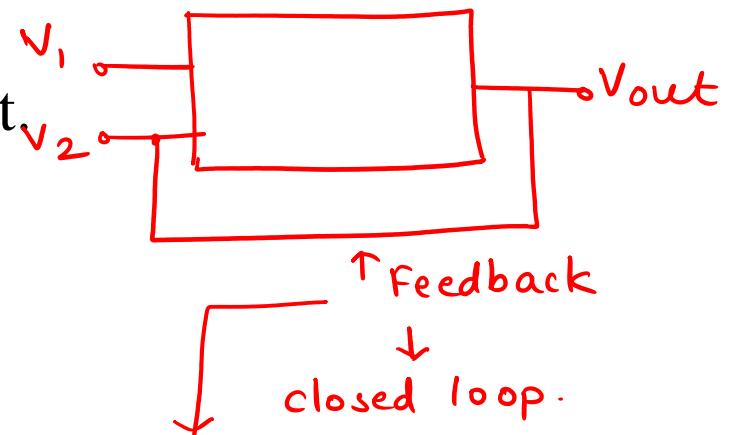➤ Negative feedback or Degenerative feedback.





some part of the o/p is  
fed back to the i/p.
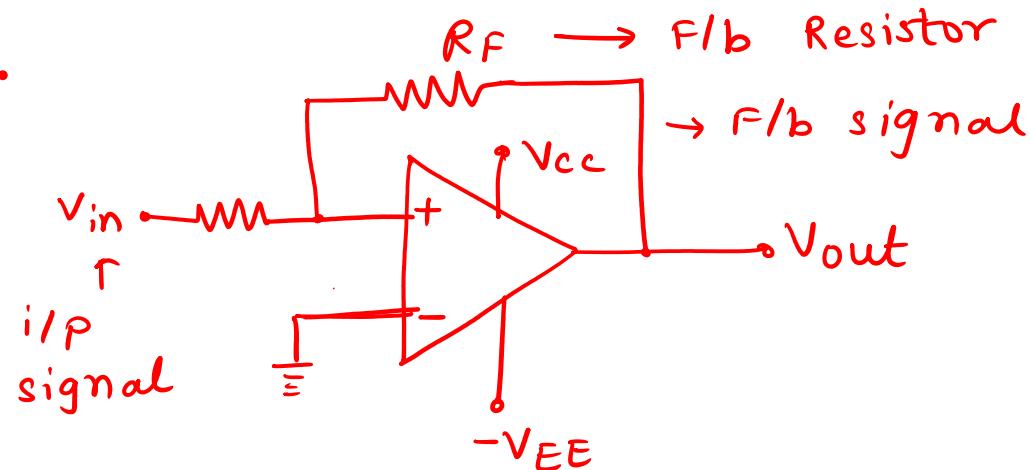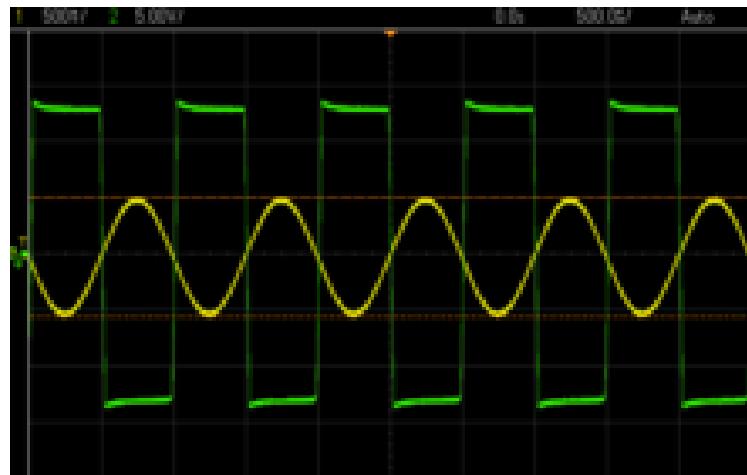
# Positive Feedback or Regenerative Feedback


( $0^\circ$  phase shift)

- If the feedback signal and the original input signal are in phase with each other then it is called as the positive feedback.
- Positive feedback is used in the application such as “**Oscillators**” and **Schmitt triggers or regenerative comparators**.



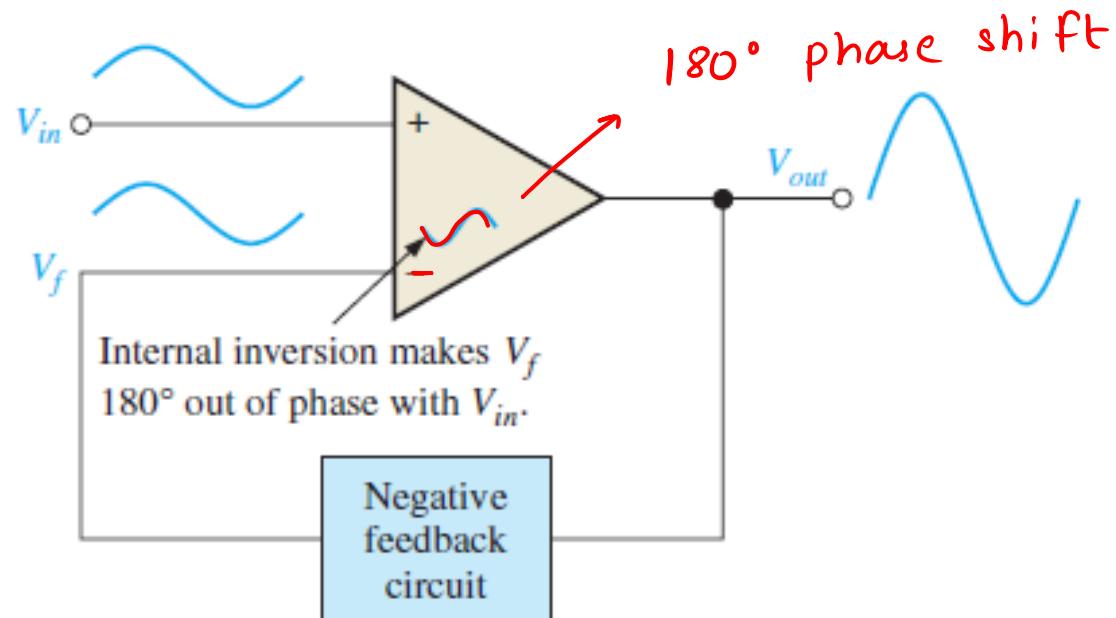
# Negative Feedback or Degenerative Feedback

- If the signal is fed back to the input and the original input signal are 180° out of phase, then it is called as the negative feedback.
- In the application of **Op-amp as an amplifier**, the negative feedback is used.


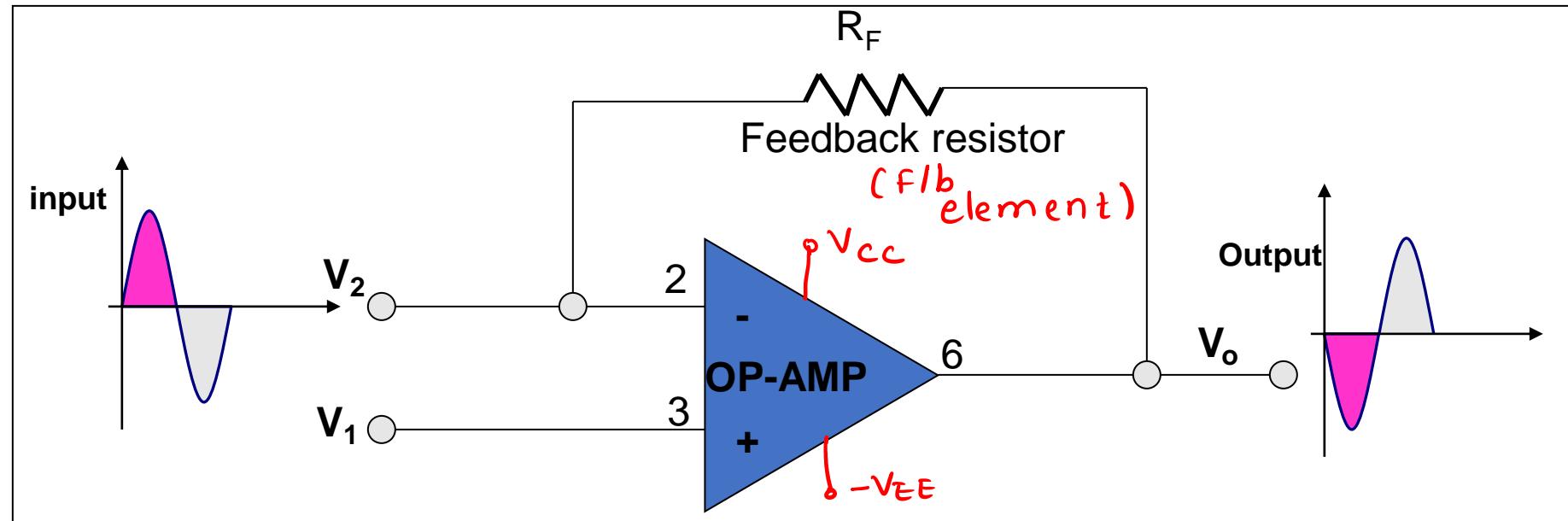
# Negative Feedback or Degenerative Feedback

- In the amplifier circuits using Op-amp, a feedback resistor  $R_F$  is connected between the output and inverting terminal as shown in figure to introduced a negative feedback.
- As the voltages  $V_2$  and  $V_O$  are  $180^\circ$  out of phase, a fraction of output voltage fed back to the input via  $R_F$  will be  $180^\circ$  out of phase with the input.




This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.

# Advantages of Negative Feedback

Negative feedback is used in the amplifier circuits as they provide the following improvements in the operation of an amplifier:

- ✓ It stabilizes the gain. (Reduces open loop gain) → Gain depends on  $R_F$  &  $R_i$  (clip resistor)
- ✓ Reduces the distortion. (Gain is reduced)
- ✓ Increases the bandwidth. (Gain  $\times$  BW product is constant)
- ✓ Reduces the effects of variation in temperature and supply voltage on the output of the Op-amp.

## Virtual Ground / Virtual short :

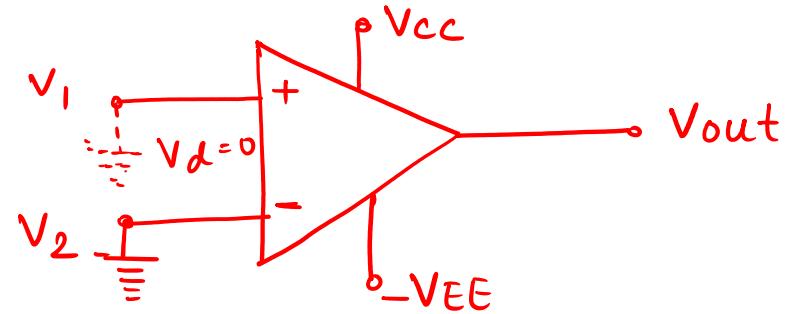

$$V_{out} = Av(V_d) = Av(V_1 - V_2)$$

Ideally,  $Av = \infty$

$$Av = \frac{V_{out}}{V_d}$$

To make  $Av = \infty$ ,

$$V_d = 0$$

$$V_1 - V_2 = 0$$

$$V_1 = V_2$$


IF  $V_2 = 0$

$V_1$  is assumed to be at ground potential.



Both the inputs  $V_1$  and  $V_2$  are considered to be at same potential.  
( $V_d = 0$ ).


# The Inverting Amplifier

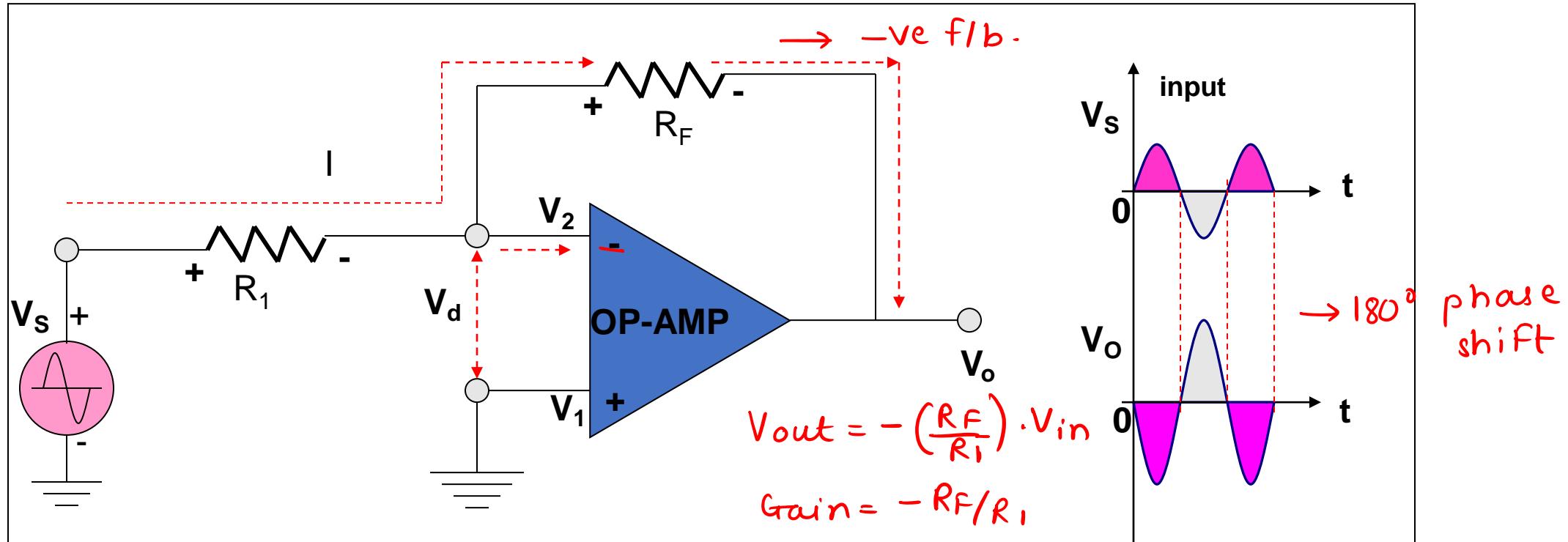

- Expression for the closed loop voltage gain ( $A_{VF}$ )  
$$A_{VF} = - R_F / R_1$$
- The negative sign indicates that there is a phase shift of 180° between the input and output voltages.

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.

## Inverting Amplifier:

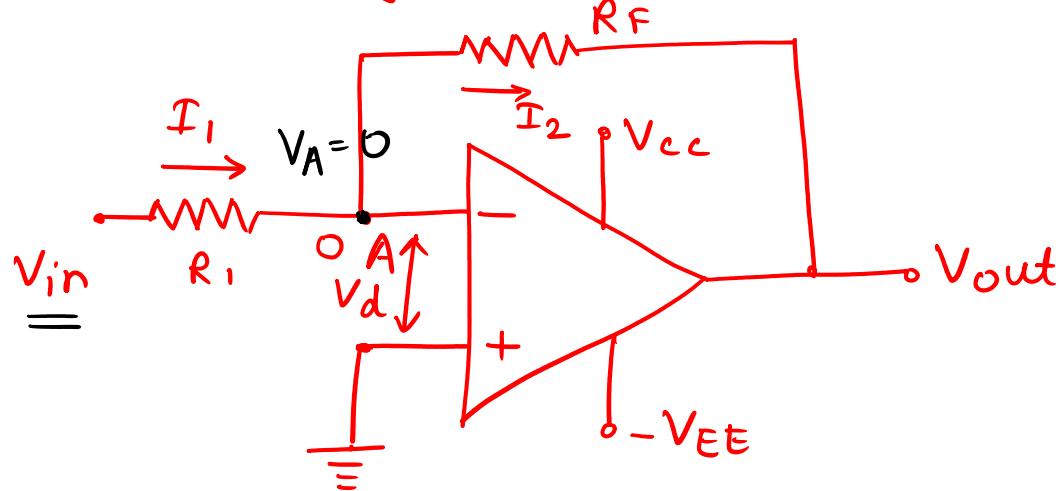


$$V_A = 0 \quad \text{(virtual ground)}$$

$$\frac{V_{in} - 0}{R_1} = \frac{0 - V_{out}}{R_F}$$

$$\frac{V_{in}}{R_1} = -\frac{V_{out}}{R_F}$$

$$V_{out} = -\frac{R_F}{R_1} \cdot V_{in}$$

# The Non-Inverting Amplifier

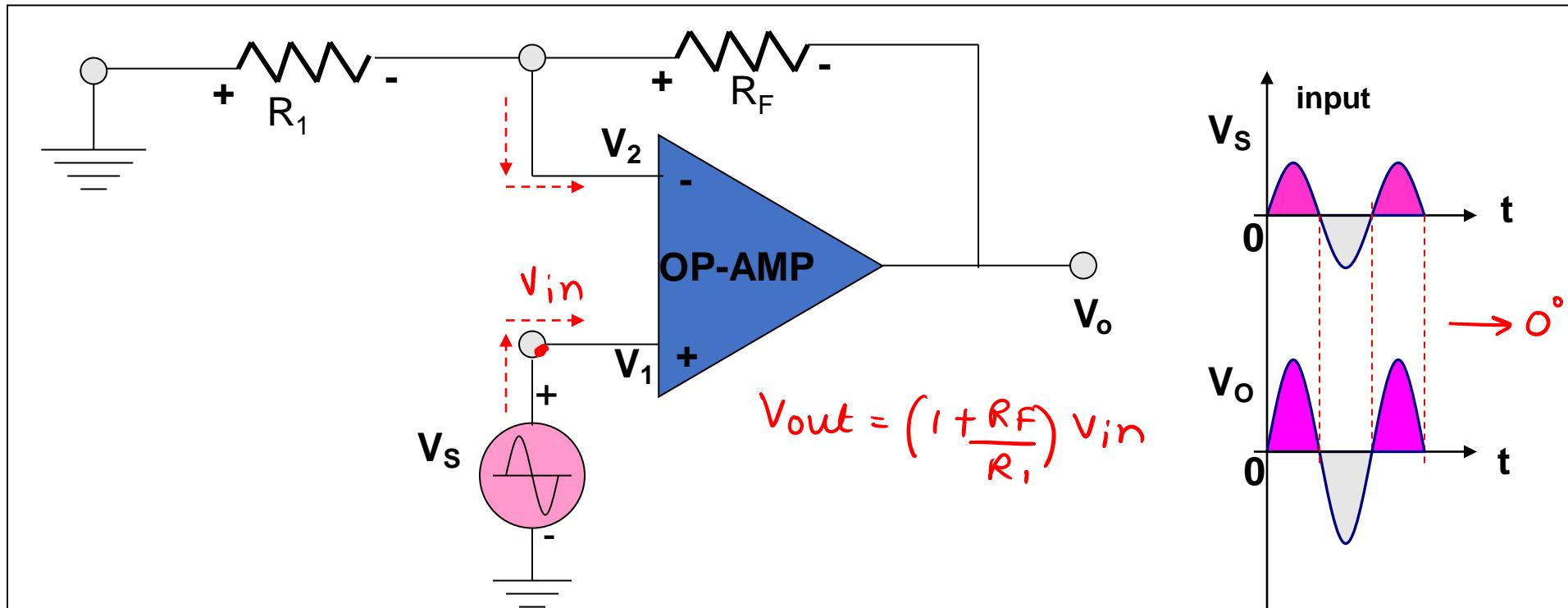


- Expression for the closed loop voltage gain ( $A_{VF}$ )


$$A_{VF} = 1 + \frac{R_F}{R_1}$$

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.

## Non-inverting Amplifier:

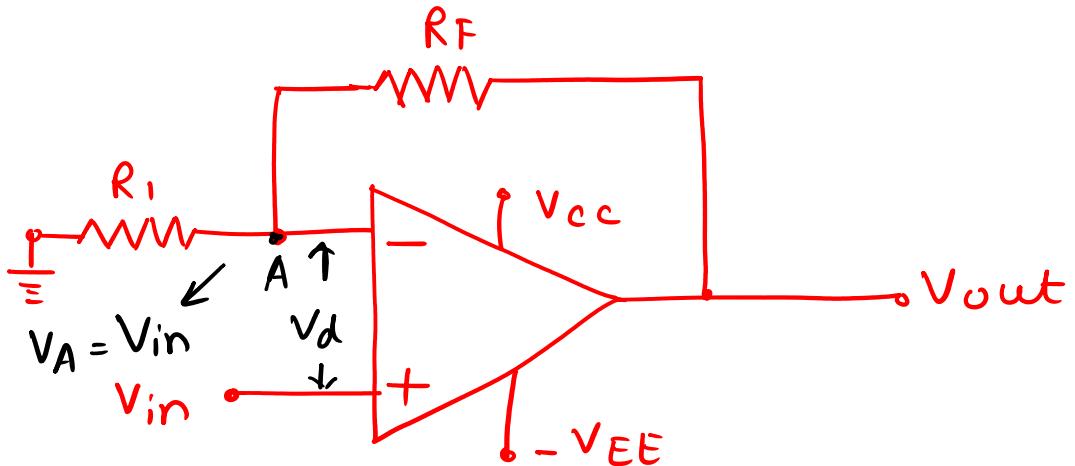

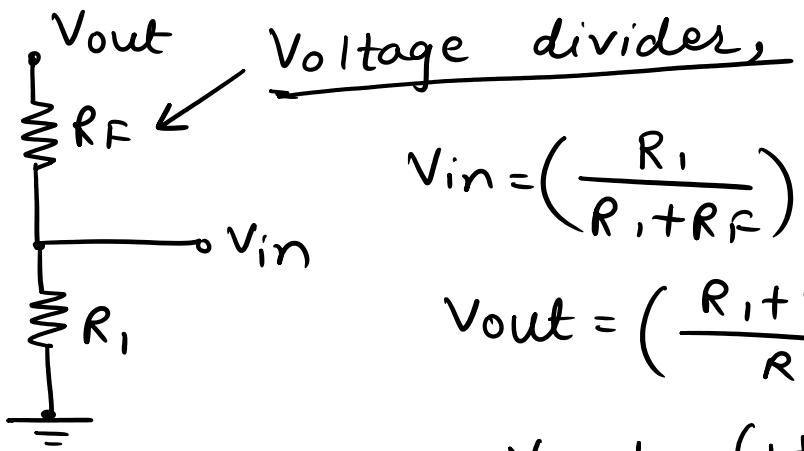According to virtual ground,  
 $V_A = V_{in} \dots (V_d = 0)$



$$V_{in} = \left( \frac{R_i}{R_i + R_F} \right) V_{out}$$

$$V_{out} = \left( \frac{R_i + R_F}{R_i} \right) V_{in}$$

$$V_{out} = \left( 1 + \frac{R_F}{R_i} \right) V_{in}$$


$$\frac{0 - V_{in}}{R_i} = \frac{V_{in} - V_{out}}{R_F}$$

$$\frac{-V_{in}}{R_i} = \frac{V_{in} - V_{out}}{R_F}$$

$$\frac{V_{in}}{R_i} + \frac{V_{in}}{R_F} = \frac{V_{out}}{R_F}$$


$$V_{out} = \left( 1 + \frac{R_F}{R_i} \right) V_{in}$$

### \* Inverting Amplifier:

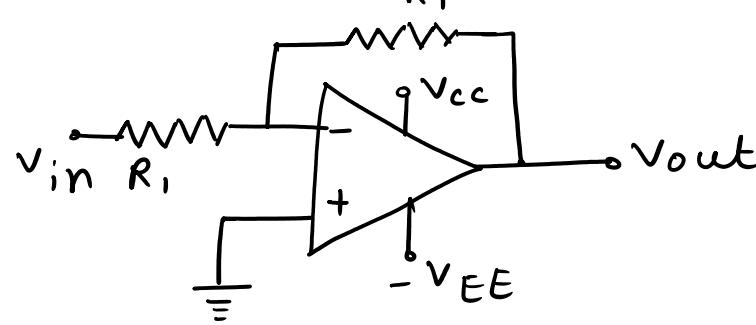


$$V_{out} = -\frac{R_F}{R_1} \cdot V_{in}$$

### \* Non-inverting Amplifier:

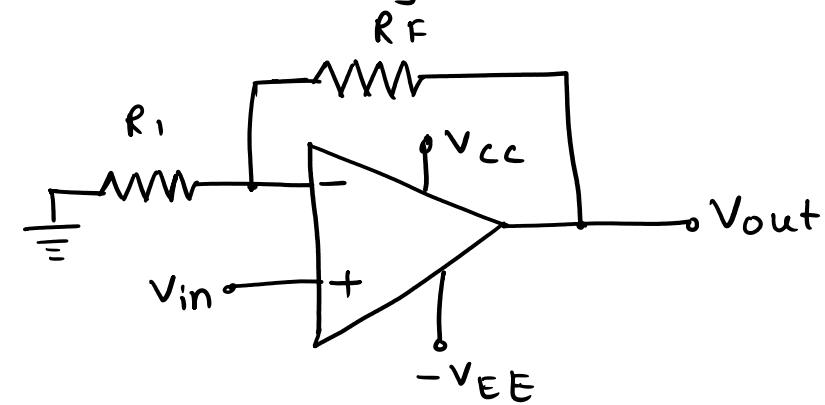

$$V_{out} = \left(1 + \frac{R_F}{R_1}\right) V_{in}$$

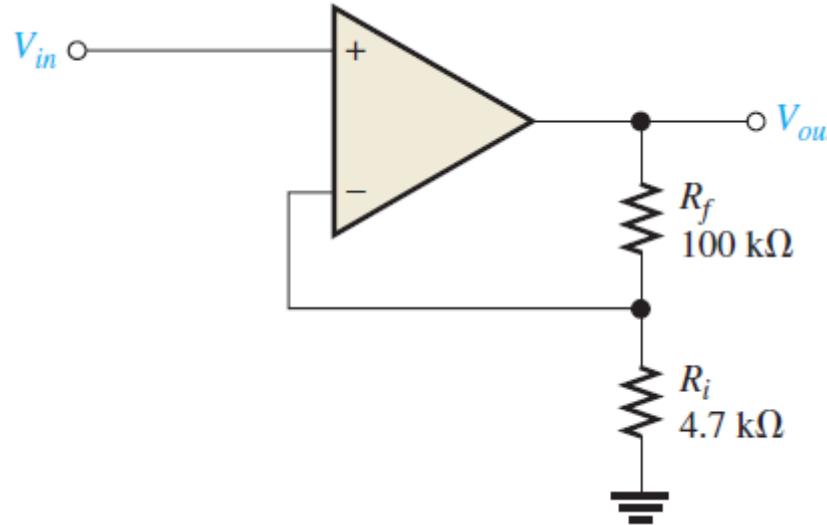1> Determine the closed-loop voltage gain of the amplifier.




$$\rightarrow V_{out} = \left( 1 + \frac{R_f}{R_i} \right) V_{in}$$

$$\begin{aligned} \text{closed loop gain} &= 1 + \frac{R_f}{R_i} \\ &= 1 + \frac{100k}{4.7k} \\ &= 22.3 \end{aligned}$$

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.

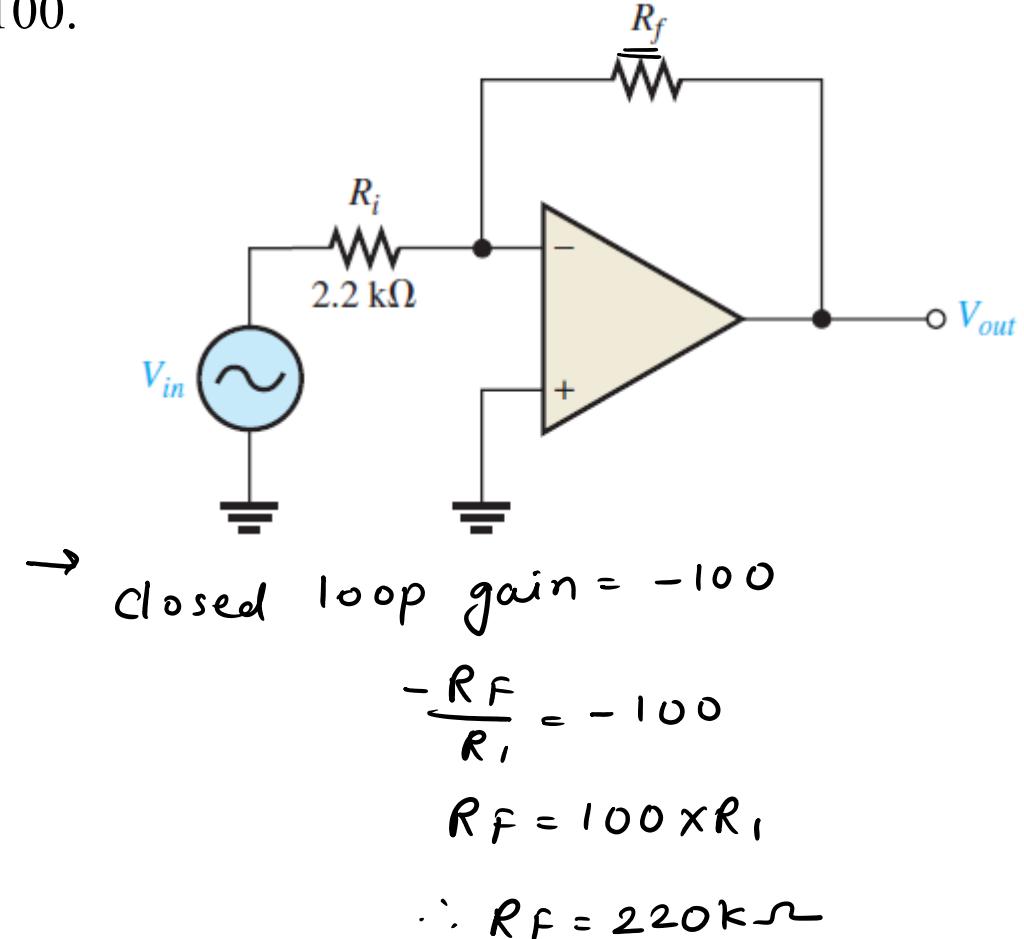2> Given the op-amp configuration in, determine the value of  $R_f$  required to produce a closed-loop voltage gain of -100.



The variable resistance varies from 0 to  $100\text{ k}\Omega$ . Find the maximum and minimum closed loop voltage gain.

Solution:

$$R_1 = 2\text{ k}\Omega, R_f(\min) = 0, R_f(\max) = 100\text{ k}\Omega$$


$$A = (1 + R_f/R_1)$$

$$\underline{A_{\max}} = (1 + 100/2)$$

$$\underline{\underline{A_{\max}}} = 51$$

$$\underline{A_{\min}} = (1 + 0/2)$$

$$\underline{\underline{A_{\min}}} = 1$$

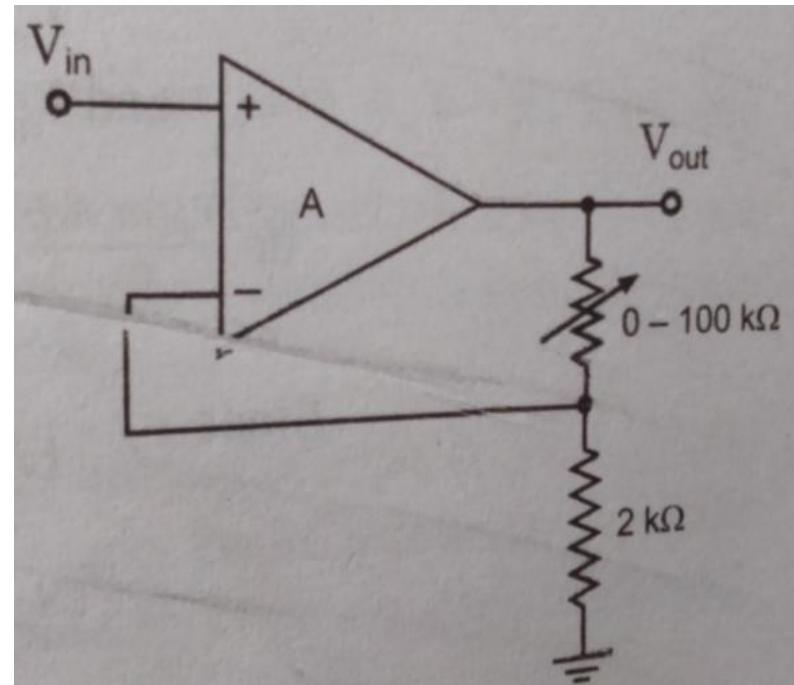

What is the range of the voltage gain adjustment in the given circuit?

Solution:

$$Af = -R_f/R_1$$

$$Af_{min} = -R_f/R_1_{max}$$


$$= -500K/(10K+10K)$$

$$\underline{Af_{min} = -25}$$

$$Af_{max} = -R_f/R_1_{min}$$

$$= -500K/(10K)$$

$$\underline{Af_{max} = -50}$$

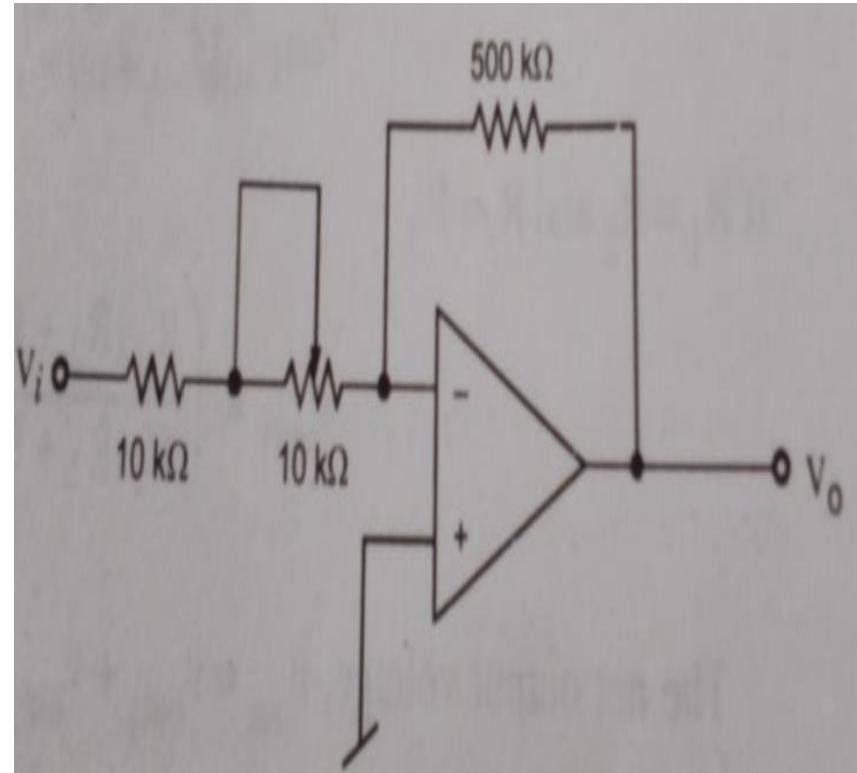

If the differential voltage gain and common mode voltage gain of Op-Amp are 50 dB and 10dB respectively. What is the value of CMRR?

$$\rightarrow A_d = 50 \text{ dB}$$

$$A_c = 10 \text{ dB}$$

$$CMRR = ?$$

$$CMRR = \frac{A_d}{A_c}$$

$$CMRR(\text{dB}) = 20 \log_{10} \left( \frac{A_d}{A_c} \right)$$

$$CMRR(\text{dB}) = A_d(\text{dB}) - A_c(\text{dB})$$


$$= 50 \text{ dB} - 10 \text{ dB}$$

$$= 40 \text{ dB}$$


$$40 \text{ dB} = 20 \log_{10} (CMRR)$$

$$CMRR = 10^{\frac{40}{2}} \\ = 100.$$

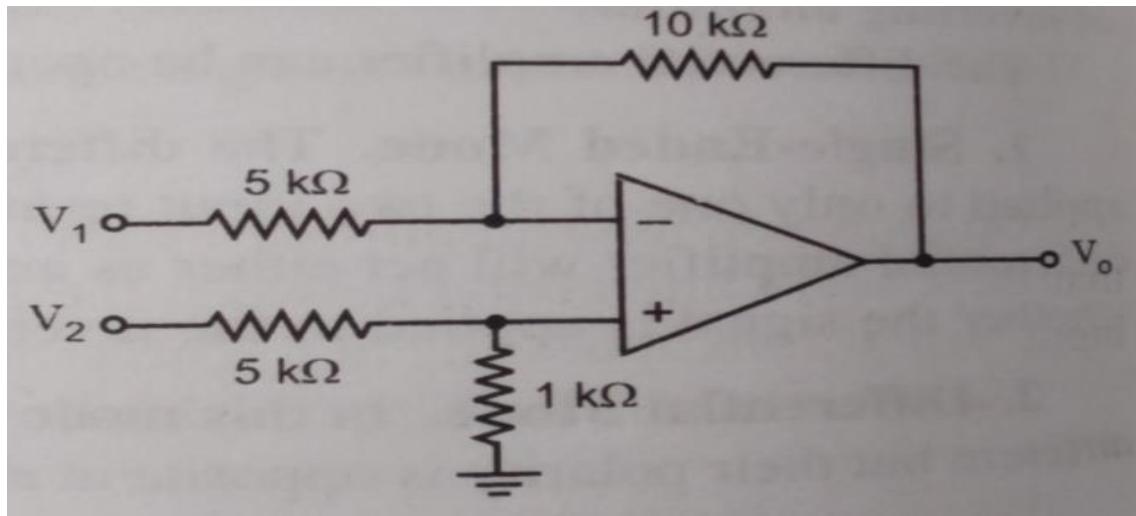Find the output voltage of the op-amp shown in figure.



1) To find  $V_{O1}$ ,  $V_2 = 0$

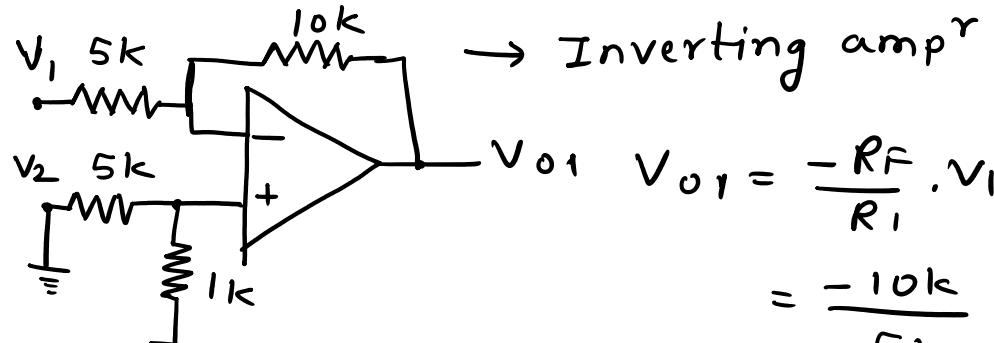


$$V_{O1} \quad V_{O1} = -\frac{R_F}{R_I} \cdot V_1 \\ = -\frac{10k}{5k} \cdot V_1$$

$$\therefore V_{O1} = -2V_1$$

This ppt is created as a reference material (only for the academic purpose) for the students of PICT. It is restricted only for the internal use and any circulation is strictly prohibited.

$$V_{out} = V_{O1} + V_{O2} = -2V_1 + \frac{1}{2}V_2$$

2) To find  $V_{O2}$ ,  $V_1 = 0$

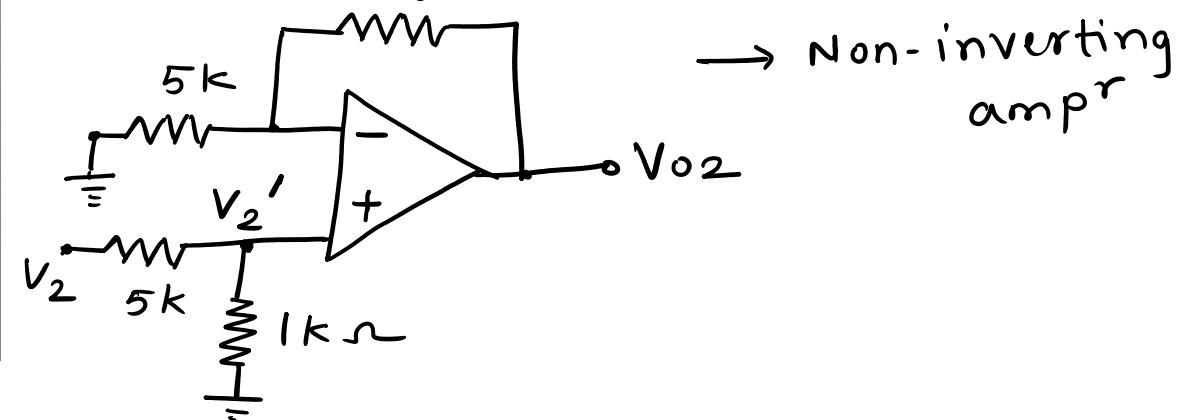


$$V_{O2} = \left(1 + \frac{R_F}{R_I}\right) V_{2'}$$

$$V_{2'} = \left(\frac{1k}{1k+5k}\right) V_2 = \frac{1}{6} V_2$$

$$\therefore V_{O2} = \left(1 + \frac{10k}{5k}\right) \frac{1}{6} \cdot V_2 = \frac{3}{6} V_2 = \frac{1}{2} V_2$$


$$\therefore V_{O2} = \frac{1}{2} V_2$$

## Modes of OP-AMP:

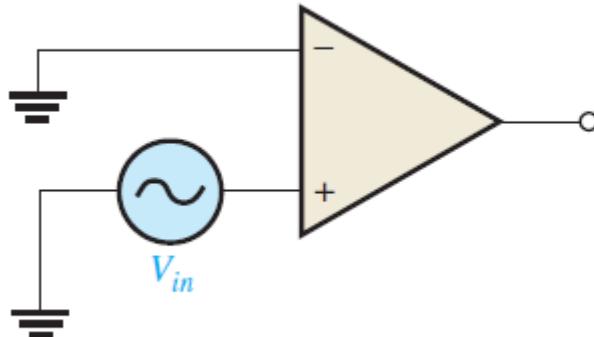


(a)

→ single ended  
input

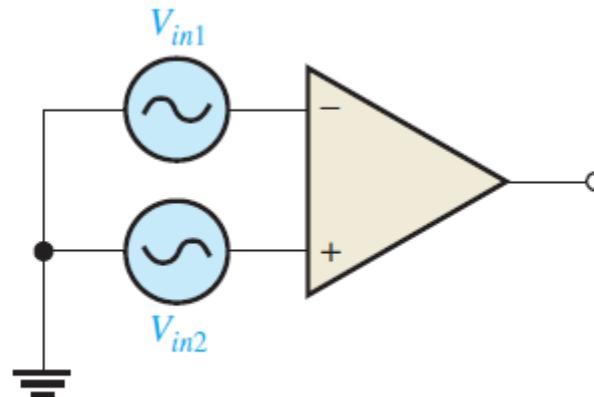

(b)

→ Double ended  
input

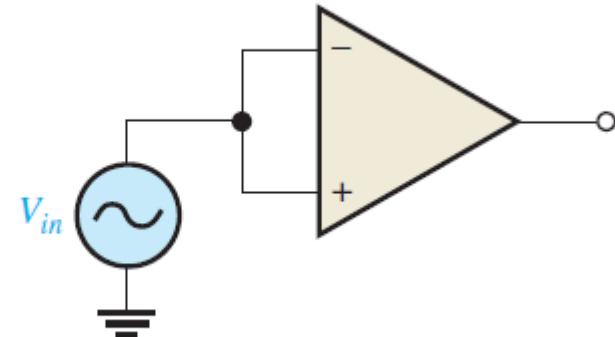

(c)

→ common mode  
input

$$V_1 = 675 \mu V$$

$$V_2 = 665 \mu V$$

$$CMRR = 80 dB$$

$$A_d = 5 \times 10^5$$

$$\rightarrow CMRR = 20 \log_{10} \left( \frac{A_d}{A_c} \right)$$

$$CMRR = 10^4$$

Now,


$$CMRR = \frac{A_d}{A_c}$$

$$10^4 = \frac{5 \times 10^5}{A_c}$$

$$\therefore A_c = 50$$

$$\begin{aligned} V_{out} &= A_d(V_1 - V_2) + A_c \left( \frac{V_1 + V_2}{2} \right) \\ &= 5.0335 V \end{aligned}$$
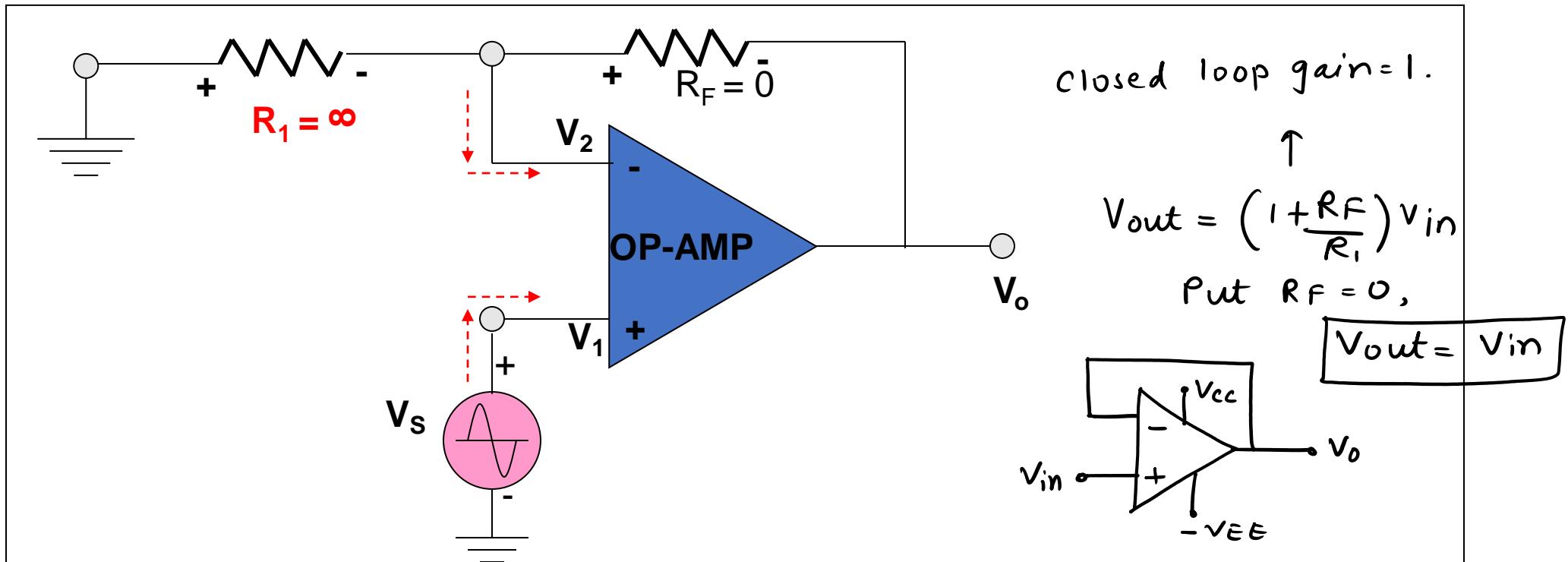
# The Voltage Follower (Unity Gain Buffer)



- When  $R_1$  is infinite and  $R_F = 0$  the non-inverting amplifier gets converted into a voltage follower or unity gain.

# Acknowledgements

1. Electronic Devices, Thomas L. Floyd
2. Web Resources

# **Thank You..**

This ppt is created as a reference material (only for the academic purpose) for the students of PICT.

It is restricted only for the internal use and any circulation is strictly prohibited.