

D-MOSFET



can operate in Depletion and Enhancement Mode
DE-MOSFET

- The drain and source are diffused into the substrate material and then connected by a narrow channel adjacent to the insulated gate. Both n-channel and p-channel devices are shown in the figure.

* Channel is present.

↓
w/o application of V_{GS} , it acts as closed sw.

↓
Normally ON.

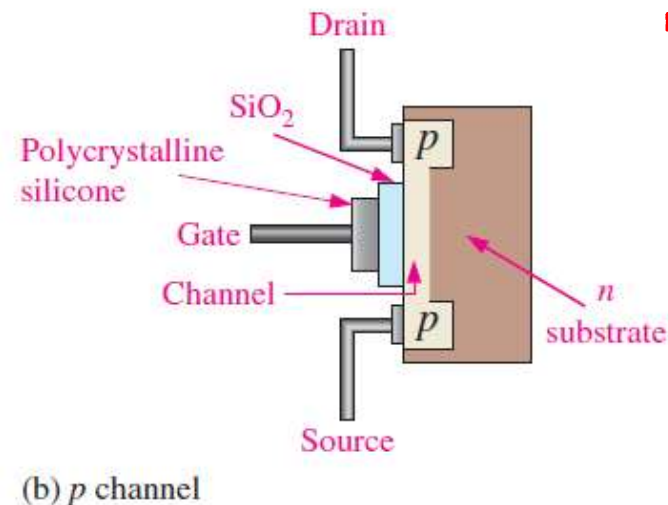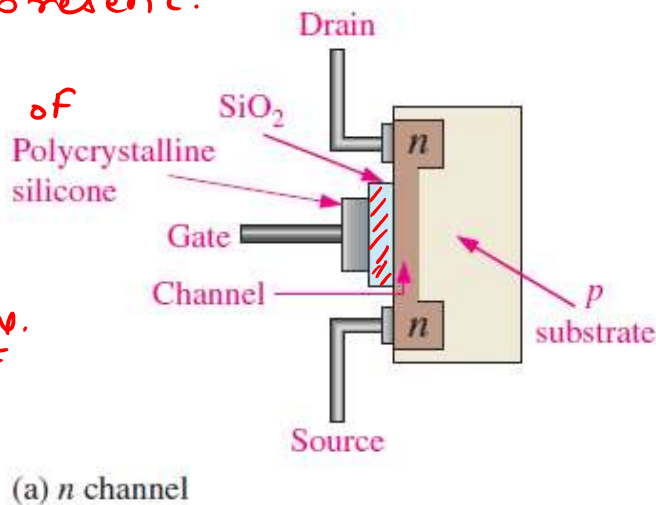

Symbols:

i) n-channel D-MOSFET



ii) p-channel D-MOSFET



D-MOSFET...

(nchannel)


• Biasing..

1) $-V_{GS}$ is applied

↓
Depletion Mode

↓
conductivity of channel is reduced.

↓
 $I_D \downarrow$

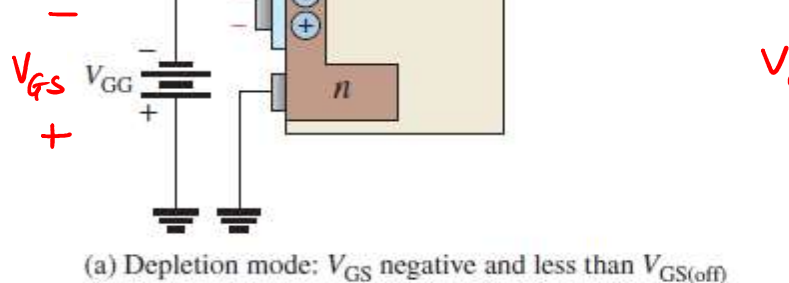


I_D is less

I_D is more

1) $+V_{GS}$ is applied

↓
conductivity of channel is enhanced.
↓
Enhancement Mode

↓
 $I_D \uparrow$

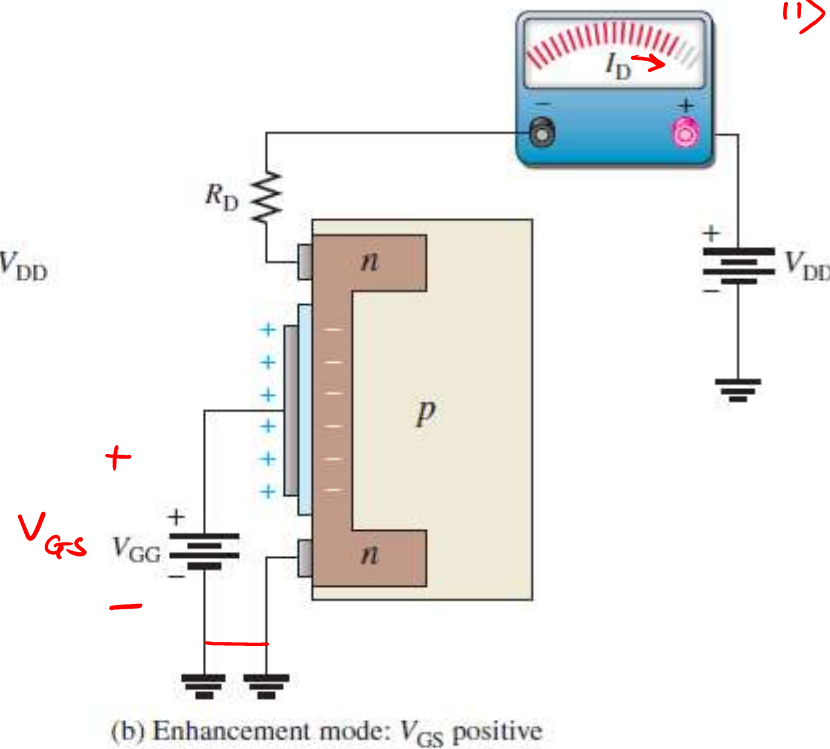

D-MOSFET...

- The D-MOSFET can be operated in either of two modes, the depletion mode or the enhancement mode, and is sometimes called a depletion/enhancement MOSFET.
- Since the gate is insulated from the channel, either a positive or a negative gate voltage can be applied. $+V_{GS} / -V_{GS}$
- The ^{p-}n-channel MOSFET operates in the depletion mode when a negative gate-to-source voltage is applied and in the enhancement mode when a positive gate-to-source voltage is applied.
- These devices are generally operated in the depletion mode.

Depletion Mode

- Visualize the gate as one plate of a parallel-plate capacitor and the channel as the other plate. The silicon dioxide insulating layer is the dielectric.
- With a negative gate voltage, the negative charges on the gate repel conduction electrons from the channel, leaving positive ions in their place. Thereby, the n channel is depleted of some of its electrons, thus decreasing the channel conductivity.
- The greater the negative voltage on the gate, the greater the depletion of n-channel electrons. At a sufficiently negative gate-to-source voltage, $V_{GS(off)}$, the channel is totally depleted, and the drain current is zero.

$$V_{GS(off)} = V_{GS} \Big|_{I_D=0}$$

Enhancement Mode

- With a positive gate voltage, more conduction electrons are attracted into the channel, thus increasing (enhancing) the channel conductivity.

*	n-channel D-MOSFET	p-channel D-MOSFET
Depletion Mode	$-V_{GS}$	$+V_{GS}$
Enhancement Mode	$+V_{GS}$	$-V_{GS}$


D-MOSFET characteristics

- D-MOSFET can operate with either positive or negative gate voltages.


$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}} \right)^2$$

I_{DSS} → Drain to Source Saturation Current

$$I_{DSS} = I_D \big|_{V_{GS}=0}$$

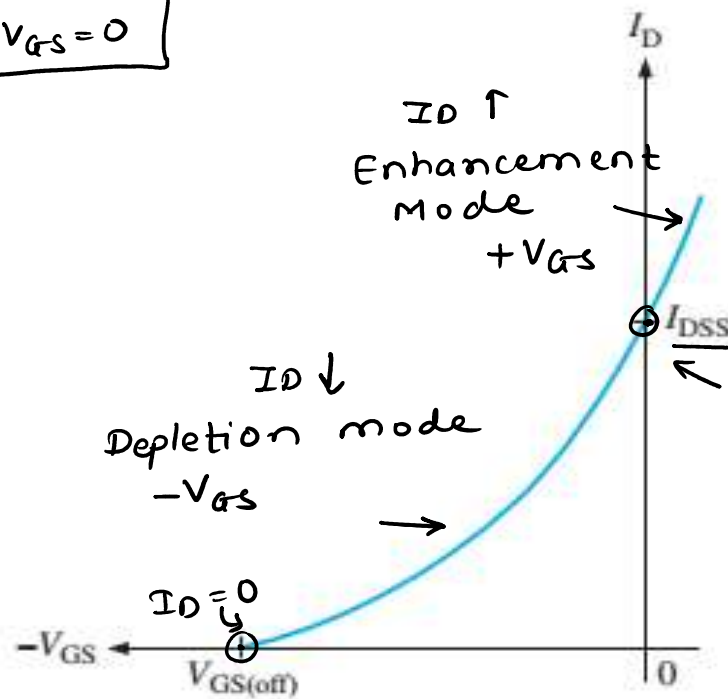

(a) n channel

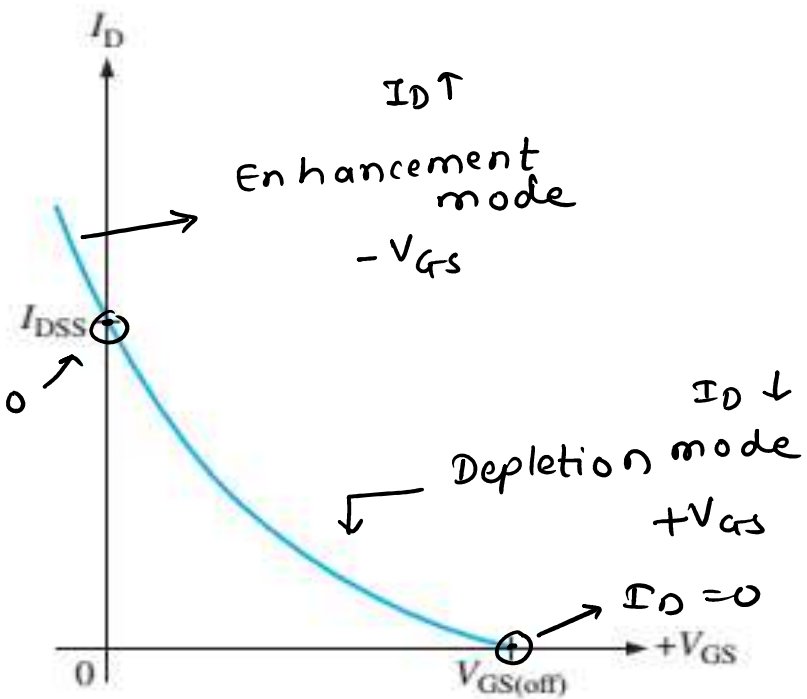

(b) p channel

D-MOSFET characteristics...

- This is indicated on the general transfer characteristic curves in for both n-channel and p-channel MOSFETs.
- The point on the curves where $V_{GS}=0$ corresponds to I_{DSS} . The point where, $I_D=0$ corresponds to $V_{GS(off)}$.

$$V_{GS(off)} = -V_P.$$

\hookrightarrow Pinch off voltage

Numerical Problem

- For a certain D-MOSFET, I_{DSS} 10 mA and $V_{GS(off)} = -8$ V.

(a) Is this an n-channel or a p-channel?

(b) Calculate I_D at $V_{GS} -3$ V

(c) Calculate I_D at $V_{GS} 3$ V


a) The device has a negative $V_{GS(off)}$; therefore, it is an **n-channel** MOSFET.

$$b) I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_{GS(off)}}\right)^2 = (10mA) \left(1 - \frac{-3V}{-8V}\right)^2 = \underline{3.91mA}$$

$$c) I_D = (10mA) \left(1 - \frac{+3V}{-8V}\right)^2 = \underline{18.9mA}$$

BJT	MOSFET
It is a current controlled device.	It is a voltage controlled device.
It is a bipolar device (Current flows due to both majority & minority carriers).	It is a unipolar device (Current flows due to only majority carriers).
Thermal Runaway can damage the BJT	Thermal Runaway does not take place
Input resistance (R_i) is very low .	Output resistance (R_o) is very high .
Transfer characteristics are linear in nature.	Transfer characteristics are non-linear in nature.
BJT is More sensitive than MOSFET	MOSFET is less Sensitive
AC Voltage Gain is HIGH	AC Voltage Gain is Less
Bigger in size.	Smaller in size.
Regions of operation: Saturation – ON Switch , Cut off – OFF Switch Active – Amplifier	Regions of operation: Ohmic – ON Switch , Saturation – Amplifier , Cut off – OFF Switch
Switching speed is less.	Switching speed is high.
Symbol	Symbol

MOSFET as a Switch

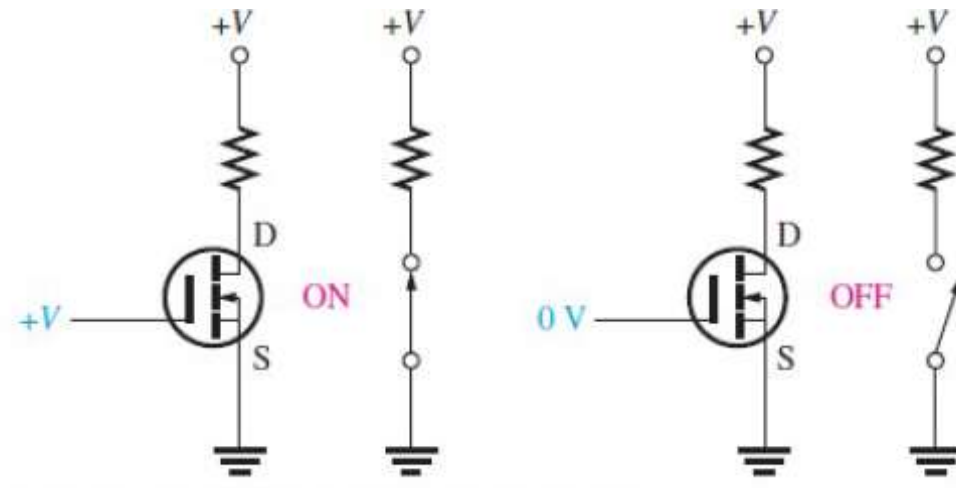

- Enhancement mode type N-channel MOSFET device. As shown, the MOSFET is switched ON when positive voltage is applied as V_{GS} .
- When zero voltage is applied to the device at V_{GS} , it will be powered OFF.

MOSFET as an Amplifier → Single stage RC coupled small signal amplifier

n-channel E-MOSFET

1) $V_{GS} > V_{GS(TH)}$

2) Bias the MOSFET in saturation region.


* Amplification Factor

$$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$$


g_m = Transconductance of MOSFET
Unit = mA/V
= mS

- * Common source
- * common Gate
- * common Drain

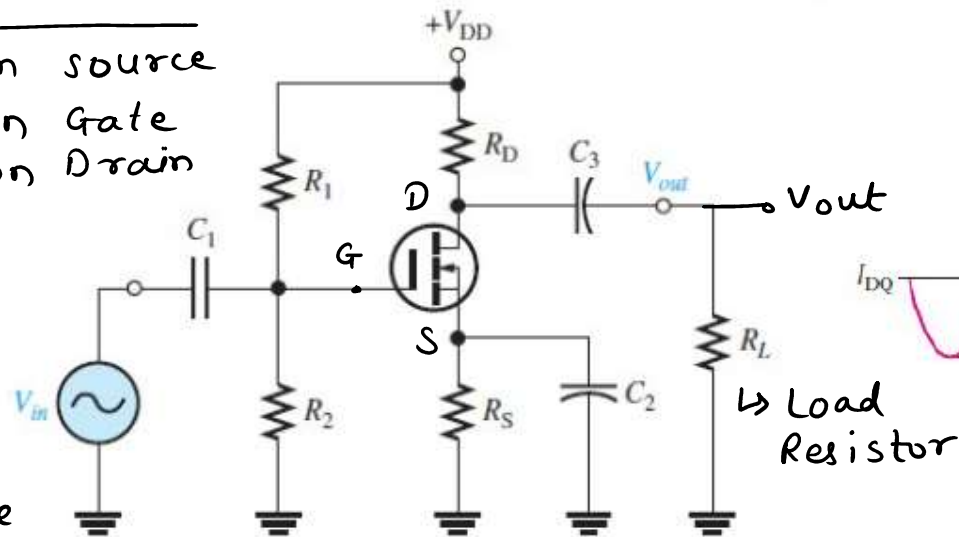Input: Gate & source
Output: Drain & source



↳ Load Resistor

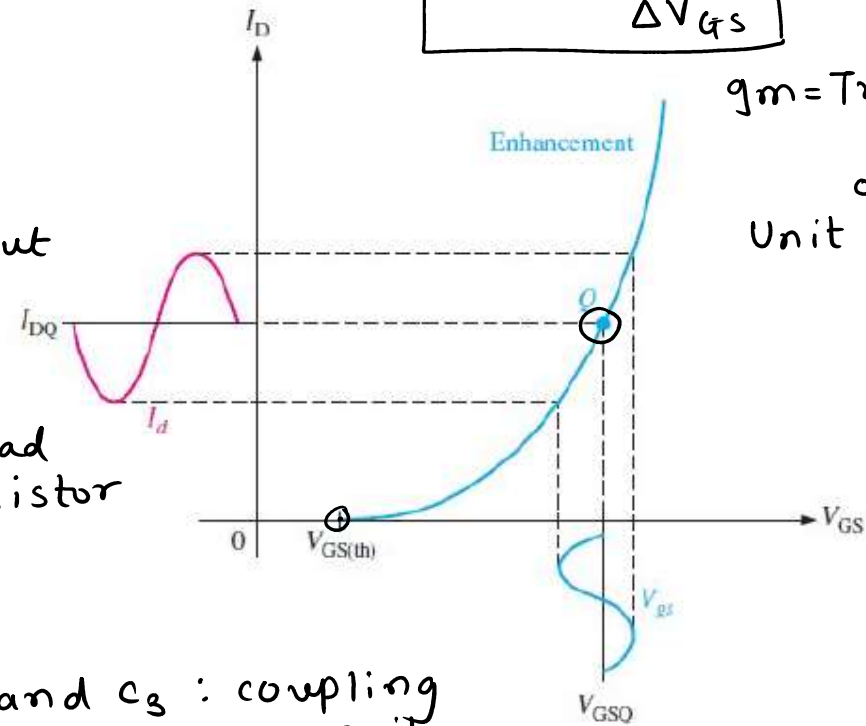

Common Source

R_1 and R_2 → Biasing resistors
→ Voltage divider bias
↳ Q point stability

C_1 and C_3 : coupling capacitors
 C_2 : Bypass capacitor

$$I_C = \beta_{dc} I_B$$

↳ A.F.

MOSFET as an Amplifier

- The gate is biased with a positive voltage such that $V_{GS} > V_{GS(TH)}$
- The signal voltage produces a swing in V_{GS} above and below its Q-point value, V_{GSQ} .
- This, in turn, causes a swing in I_D above and below its Q-point value, I_{DQ} , as illustrated in Figure
- Operation is entirely in the enhancement mode.

Acknowledgements

1. Electronic Devices, Thomas L. Floyd
2. Web Resources

This ppt is created as a reference material (only for the academic purpose) for the students of PICT.
It is restricted only for the internal use and any circulation is strictly prohibited.

Thank You..

This ppt is created as a reference material (only for the academic purpose) for the students of PICT.
It is restricted only for the internal use and any circulation is strictly prohibited.